



GN001 Application Guide

Design with GaN Enhancement mode HEMT

Updated on April 12, 2018
GaN Systems Inc.




- [Basics](#)
- [Gate Drive Design considerations](#)
- [Design examples](#)
- [PCB Layout](#)
- [Switching Testing results](#)

Please visit <http://gansystems.com/design-center/application-notes/> for the latest version of this document

GaN Enhancement mode High Electron Mobility Transistor (E-HEMT)

- A lateral 2-dimensional electron gas (2DEG) channel formed on AlGaIn/GaN hetero-epitaxy structure provides very high charge density and mobility
- For enhancement mode operation, a gate is implemented to deplete the 2DEG underneath at 0V or negative bias. A positive gate bias turns on the 2DEG channel
- It works just like MOSFET except better switching performance

I_{DS} vs. V_{DS} characteristics

   


Common with Si MOSFET

- True E-mode, normally off
- Voltage driven - driver charges/discharges C_{ISS}
- Supply Gate leakage I_{GSS} only
- Easy slew rate control by R_G

Differences

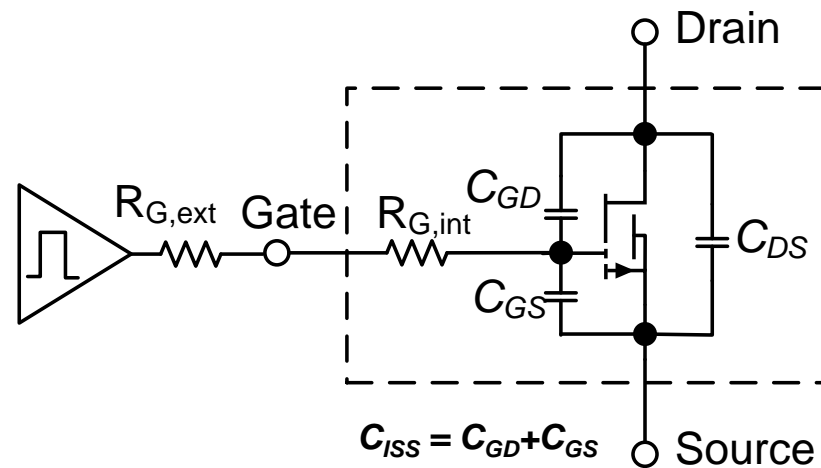
- Much Lower Q_G : Lower drive loss; faster switching
- Higher gain and lower V_{GS} : +5-6V gate bias to turn on
- Lower $V_{G(th)}$: typ. 1.5V



Versus other e-mode GaN

- More robust gate: +7/-10V DC max rating
- No DC gate holding current required
- No complicated gate diode / PN junction

Gate Bias Level	GaN Systems GaN E-HEMT	Si MOSFET	IGBT	SIC MOSFET
Maximum rating	-10/+7V	+/-20V	+/-20V	-8/+20V
Typical gate bias values	0 or -3/+5-6V	0/+10-12V	0 or -9/+15V	-4/+15-20V

 


	Gate	GaN E-HEMT	MOSFET	Si IGBT
A	ON	$R_{DS(ON)}$		
B	ON	$R_{DS(ON)}$		
C	OFF	$V_{th} + V_{GS(OFF)}$ $R_{DS(REV)}$		

- No body diode, but 2DEG can conduct in 3rd quadrant – **No need for anti-parallel diode**
- When gate is OFF (during dead time), 2DEG exhibits like a diode with $V_F = V_{th} + V_{GS(off)}$
- Reduce dead time loss: 1) minimize dead time; 2) Use smaller or avoid negative V_{GS} if possible


Reverse Recovery charge Q_{RR} :

- GaN has zero Q_{RR} making it suitable for **half bridge hard switching** – Replace IGBT
- Si MOSFET can't be used for any half bridge hard-switch circuit due to Q_{RR}
- Excellent reverse recovery of GaN enables new topologies such as bridgeless totem pole PFC


Half bridge turn-on 400V/20A – SJ MOSFET

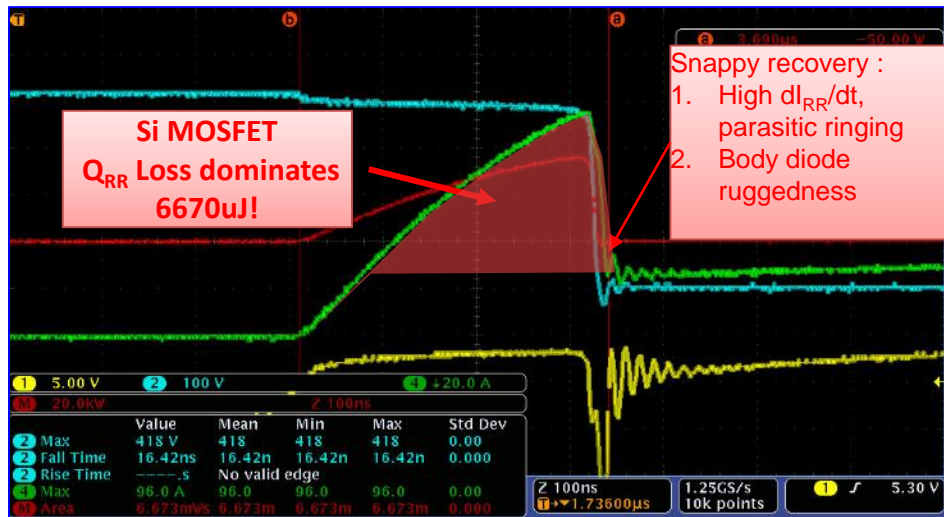

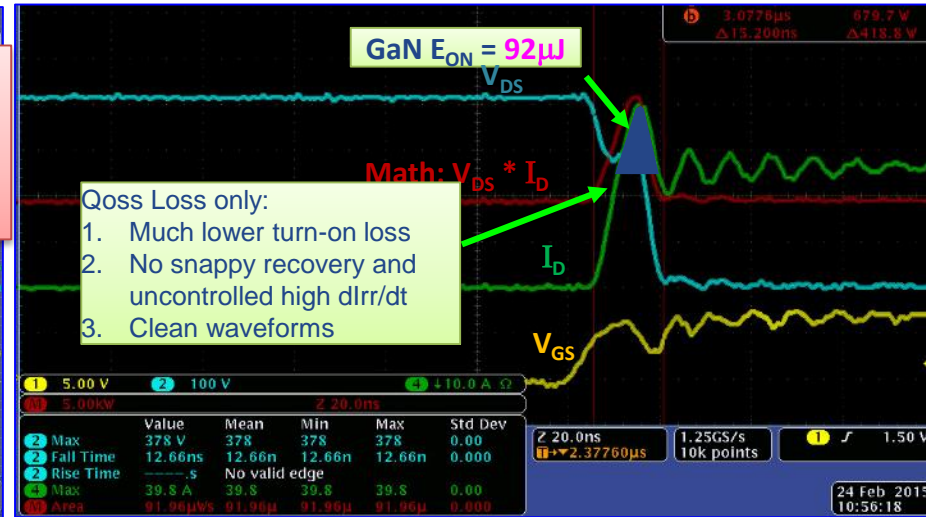Half bridge turn-on 400V/20A – GaN E-HEMT





- For hard switching: t_{d_pwm} must be $> t_{delay_skew} + (t_{d(off)} - t_{d(on)})$:
- Gate turn-on/off delay difference varies with R_G : typical $\pm 5ns$ range (GS66508)
- High/low side gate driver delay skew (worst case delay mismatch) usually dominates:
 - Example Silab Si8261 isolated gate driver $t_{delay_skew_max} = 25ns$. In this case the dead time must be set $> 30ns$ as minimum
 - However in practical circuit safety margin must be considered: for GS66508 typical **50-100ns** is chosen for dead time
- For soft switching dead time needs to be chosen for achieving ZVS transition
- For 100V: smaller can be used (10-20NS) as 100V driver has better delay matching

 

- [Basics](#)
- [Gate Drive Design considerations](#)
- [Design examples](#)
- [PCB Layout](#)
- [Switching Testing results](#)

GaN switches faster than Si/SiC MOSFETs with $dv/dt > 100V/ns$

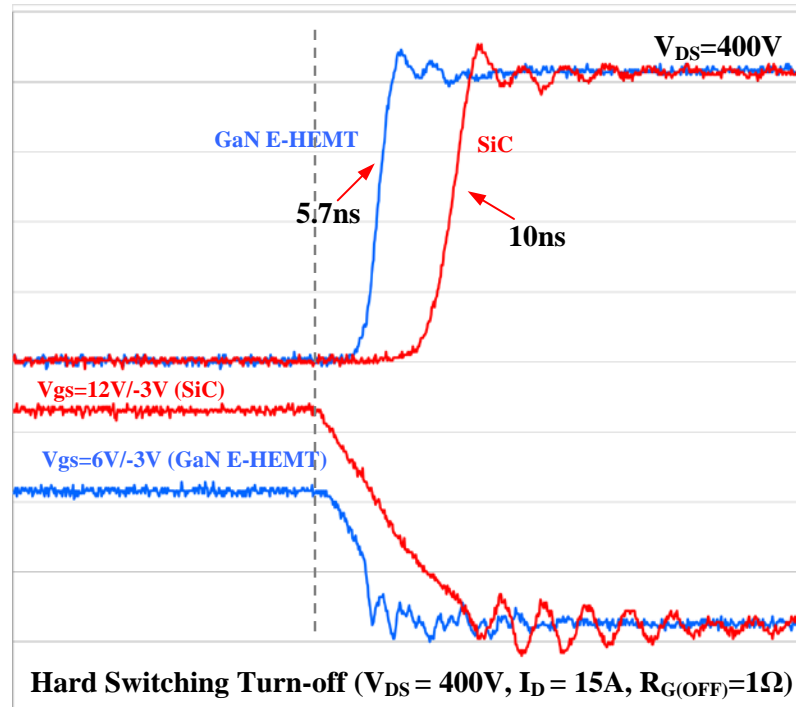 - GaN has a 4x faster turn-on and $\sim 2x$ faster off time than state of art SiC MOSFET with similar $R_{ds(on)}$



Design considerations for driving high speed GaN E-HEMTs:

Controlling noise coupling from power to gate drive loop should be the first priority:

- High dv/dt and di/dt combined with low C_{ISS} and $V_{G(th)}$ → Need to protect gate spikes from going above threshold or maximum rating under miller effect for safe operation
- Gate ringing or sustained oscillation may occur if the design is not done properly and may lead to device failure. We will discuss how to mitigate that in this section
- On the other hand, the switching performance of GaN should not be compromised too much
- This is more critical for 650V hard switching half bridge application as very high dv/dt could occur at hard turn-on.
- Single end topology has less concern with miller effect, and for resonant ZVS topology the dv/dt and di/dt are lower so their design requirement may be relaxed.


In this section we will walk through the design tips on how to control miller effect and mitigate gate ringing/oscillation, followed by gate driver recommendations

Gate drive impedance (R_G and L_G) is critical for turn-off, but less at turn-on

Basic rule: the gate needs to be held down as strong as possible with minimum impedance


Miller effect is more prominent at 650V than 100V design due to the higher dv/dt

Positive dv/dt

 




- Prevent false turn-on
- Strong pull-down (low R_G/R_{OL})
- Low L_G to avoid ringing
- Use negative gate bias, -2 to -3V is recommended

Negative dv/dt

 


- Occurs at turn-on of the complementary switch in half bridge
- Keep V_{GS_pk} within -10V
- Strong pull-down (low R_G/R_{OL}) and low L_G for lower ringing
- V_{GS} may bounce back $>0V$ (LC ringing): ensure $V_{GS+_pk} < V_{G(TH)}$ to avoid false turn-on or gate oscillation

- For negative dv/dt , it is important to have a low-Z path for the reverse miller current to reduce the negative V_{GS} spike (and the ringing afterwards caused by LC resonance)
 - Pay attention to the V_{GS} spike around $V_{DS} < 50V$ due to the change of non-linear C_{ISS}/C_{RSS} ratio
 - A clamping diode is recommended for gate drive with single output. For gate drive with separate sink output the diode may not be needed depending on the R_G and L_G in the circuit
 - For bipolar gate bias, use a TVS diode in series with the clamping diode (or two back to back)
 - C_{GS} may not help in some cases, be careful! (induce LC resonance with L_{gate} and L_{CS})
 - Negative gate bias can help to prevent false turn-on, but ensure worst case V_{gs_pk} within $-10V$

 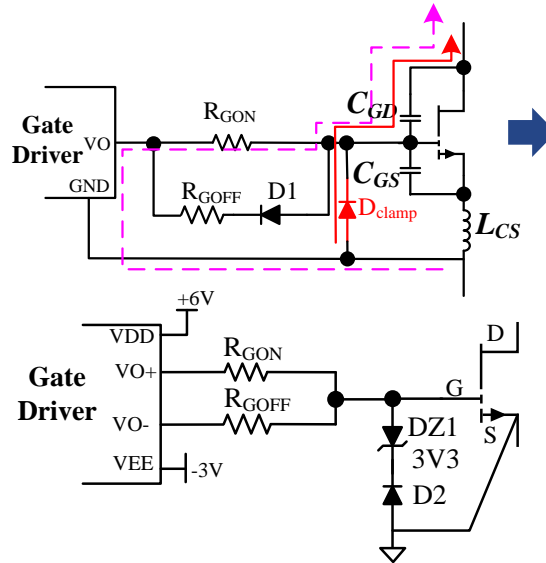 


Select right gate resistor

- GaN E-HEMT speed can be easily controlled by gate resistors
- Critical to choose the right $R_{G(ON)}/R_{G(OFF)}$ ratio for performance and drive stability
- Separate R_G for turn-on and off is recommended
- Recommend $R_{G(ON)}/R_{G(OFF)} \geq \mathbf{5-10}$ ratio for controlling the miller effect
- GaN has extremely low Q_g and drive loss: most cases 0402/0603 SMD resistors can be used
- Turn on $R_{G(ON)}$:
 - Control the turn-on dv/dt slew rate
 - Too high $R_{G(ON)}$ slows down switching and increases loss
 - Too small $R_{G(ON)}$: High dv/dt -> Higher switching loss due to the miller turn-on and potential gate oscillation
 - For GS66508: recommend to start with $R_{G(ON)} = \mathbf{10-20\Omega}$
- Turn off $R_{G(OFF)}$:
 - Typical starting value range is $\mathbf{1-2\Omega}$
 - Provide strong and fast pull-down for robust gate drive

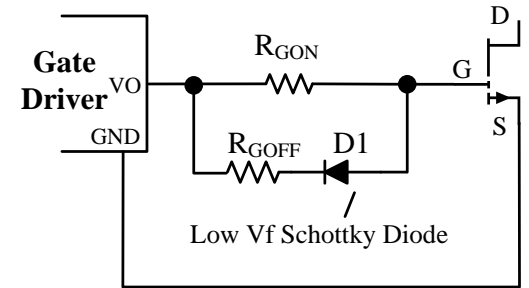


Gate driver w/ single output

 

Gate driver w/ separate outputs
(Preferred)



What causes the gate ringing/oscillation?

 - Gate over/undershoot and ringing caused by high L_G
- Common Source Inductance L_{CS} Feedback path from power to gate loop (di/dt)
- Capacitive coupling via miller capacitor C_{GD} (dv/dt)
- Noise coupling via test probe




What to do if gate ringing/oscillation occurs?

- First improve the layout by reducing L_G , L_{CS} and external G-D coupling:
 - Locate driver as close to gate as possible
 - Low inductance wide PCB trace and polygon
 - Use kelvin source connection to minimize L_{CS}
- Select right R_G to tune turn-on slew rate
- Try negative gate bias (-3V) for turn-off
- At last resort try circuits below to damp the high frequency LC ringing & overshoot:
 - Use a ferrite bead with $Z=10-20\Omega@100\text{MHz}$ in series with gate. (ferrite bead may increase L_G but damp the high frequency gate current ringing)
 - RC snubber across G-S: example $R=3.3/C=200-470\text{pF}$

  


High side gate drive



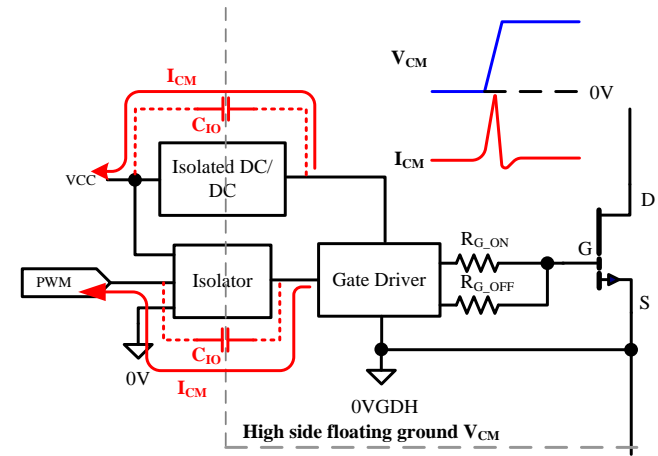



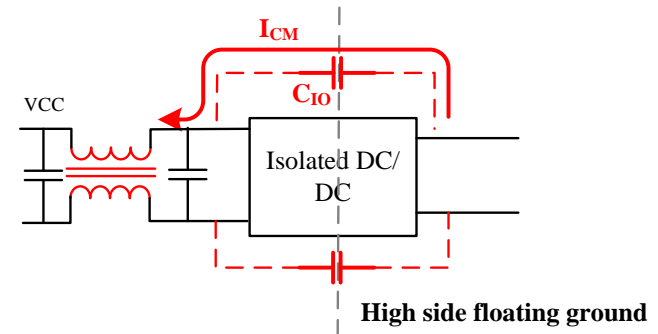












- **GaN enables fast switching $dv/dt > 100kV/us$:**
 - Minimize Coupling capacitance C_{IO}
 - CM current via C_{IO} limits CMTI
 - Use isolator/isolated gate driver with high CMTI
- **Full Isolated gate drive:**
 - Best performance
 - Isolation power supply – Minimize inter-winding Capacitance
- **Bootstrap:**
 - Common for lower voltage 100V half bridge design
 - Lower cost and simpler circuit
 - **Choose the bootstrap diode with low C_j and fast recovery time. Watch for bootstrap diode power loss limit and recovery time for high-frequency operation.**
 - Post-regulation or voltage clamping may be required after bootstrap



Optional common mode choke at input side to suppress CM noise



The following drivers have been verified by GaN Systems and are recommended for use with our GaN E-HEMTs:

Configurations	Gate Driver/Controller IC	Design resources
650V Half/Full Bridge: 1. DC/DC: LLC, PSFB, Sync Boost/Buck 2. AC/DC: Totem pole PFC, Active Clamp Flyback 3. Inverter, motor drive	 Si8271 – Single; Si8273/4/5 – HB/Dual -GB (0-6V) or -AB (-3/+6V)	 Si827x Datasheet  Si8271 demo board (GS66508T)  IMS evaluation board User Guide
	 ADuM4121ARIZ (0-6V Drive) ADuM4121BRIZ (-3/+6V Drive)	 ADuM4121 Datasheet
	 ACPL-P346 Use -4/+6V gate drive	 ACPL-P346 Datasheet  ACPL-P346 Evaluation Board with GS66508T
80-100V Half/Full bridge 1. 48V DC/DC 2. 48V POL 3. Sync. Buck/Boost 4. Class D Audio 5. Wireless Power Transfer	 LM5113(NRND) : 100V, max 5MHz LMG1205 : 80V/5A HB Driver	 LM5113 Datasheet  LMG1205 Datasheet
	 PE29101 : 100V, 48V DC/DC, 33MHz PE29102 : 60V, Class D Audio, WPT, 40MHz	 PE29100 Datasheet  PE20102 Datasheet  PE29102 Demo board (GS61004B)
	 UPI Semi GaN FET drivers: uP1966A : Dual-Channel GaN driver	 uP1966A GaN Driver  Ultra High Speed 80V HB Driver for GaN Application

Configurations	Gate Driver/Controller IC	Design resources
Low side non-isolated driver for 650V/100V GaN*: 1. Flyback, Push-pull 2. Forward 3. Boost PFC 4. Secondary SR 5. Class E P/A	LM5114/UCC27511: Single Channel, 4A, 5-6V drive UCC27611: w/ internal LDO (5V)	LM5114 Datasheet UCC2751x Datasheet
	uP1964: Internal LDO for 6V drive	uP1964 Datasheet
	Other GaN compatible drivers IXD609SI: Single, 6V drive, high drive current (9A) FAN3122/TC4422: Single, 6V drive, high drive current (9A) FAN3223/4/5: Dual 4A, 6V drive, for push-pull or SR application	
Sync Buck DC/DC (100V GaN): 1. 48V-12V DC/DC	LTC7800: 60V, Sync. Step-Down Controller (up to 2.2MHz, w/ integrated GaN compatible drivers)	LTC7800 Datasheet
Secondary side Rectification (100V GaN): 1. High frequency LLC 2. Flyback	NCP4305A: 5V gate drive clamp, 1MHz max	NCP4305 Datasheet
	SRK2001: Adaptive SR controller for LLC, 5-6V drive for GaN, 500KHz max	SRK2001 Datasheet

[*] Low side non-isolated drivers can also be used on high side / half bridge configurations by combining with level-shift / signal isolators, see [page 29](#) for design example.

- ❑ [Basics](#)
- ❑ [Gate Drive Design considerations](#)
- ❑ [Design examples](#)
- ❑ [PCB Layout](#)
- ❑ [Switching Testing results](#)

650V Isolated Driver Design #1 – 0-6V drive

VDD: 5/9 or 12V depending on system power rail

Optional CM Choke for better noise immunity against dv/dt

Choose isolated DC/DC PS1:

- 5/9/12V to 9V, 1W, 3kV isolation
- Low C_{IO} preferred for dv/dt immunity
- Verified/Recommended P/N:
 - RECOM R1S-xx09/HP
 - Mornsun Fxx09XT-1WR2

PWM Input:


- 3.3V or 5V logic from controller
- Optional RC filter for noise filtering
- Consider driver w/ deglitcher (-IS1 suffix) for noisy environment

Enable:

- Direct tie to VDDI if not used
- **Recommend filter cap (100nF) close to EN pin to prevent false triggering**

Si8271-based isolated driver (0-6V drive)

6V LDO for tight V_{DRV} regulation

 

Keep this loop routing as tight as possible



Gate resistors:

1. Turn-on R_{GATE} R2: typ. 10-20 Ω
2. Turn-off R_{GATE} R3: typ. 1-2 Ω


Recommended for high-frequency ZVS application

Bootstrap Half bridge gate driver

 
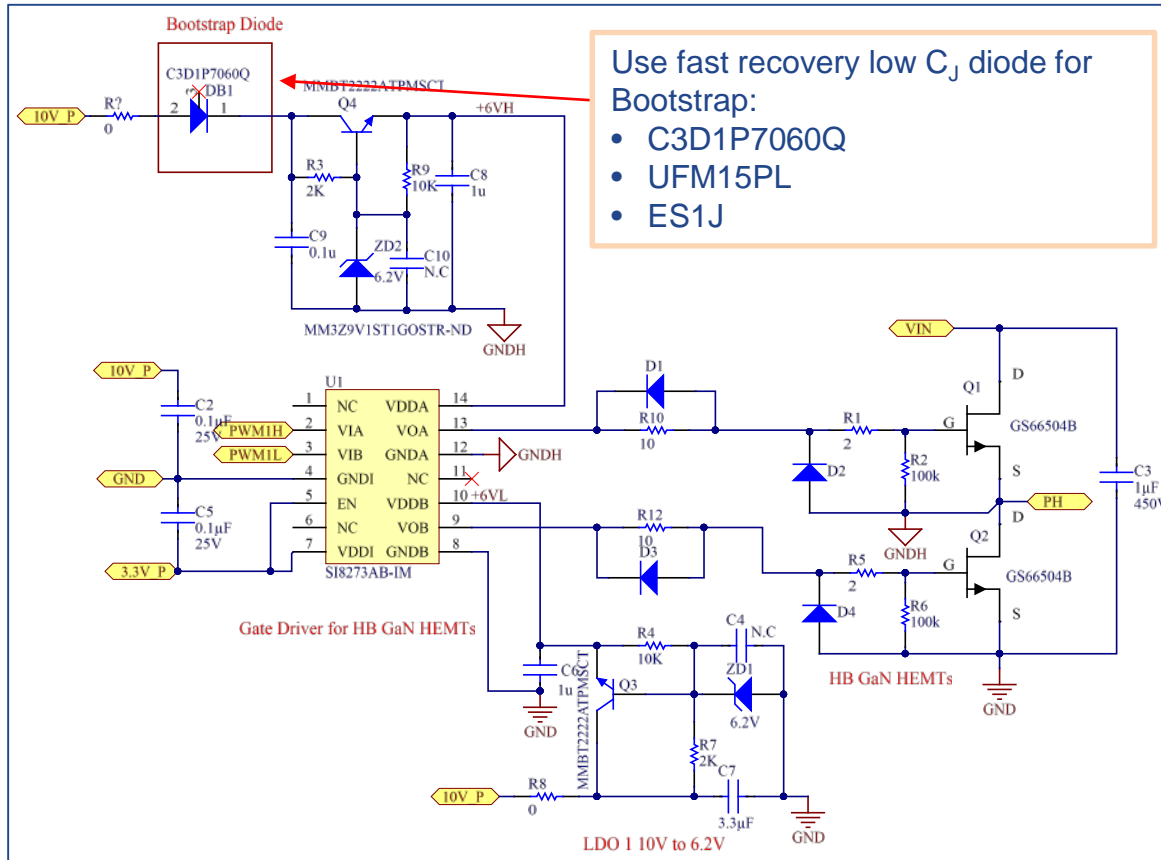
Recommended for low cost high frequency soft switch half bridge circuit (ACF, LLC etc)



LLC test waveform (400V/1.3A 600kHz)

 

 
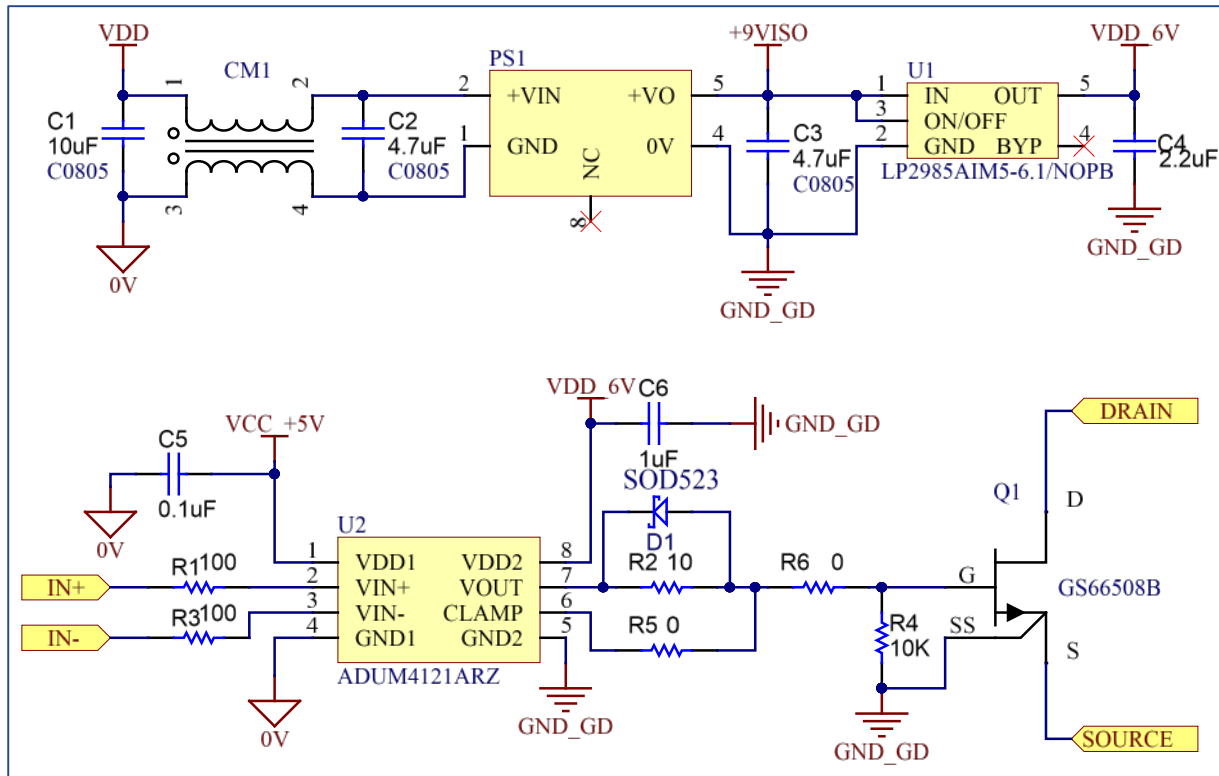
ADuM4121ARZ-based isolated gate driver for GaN HEMT (0-6V drive)



100V half bridge GaN driver – PE29101

- 80V HB driver for GaN
- Support 6V gate drive
- 48V DC/DC application
- High frequency (>5MHz)
- Dead time adjustable
- Small low inductance Pkg

PE29101

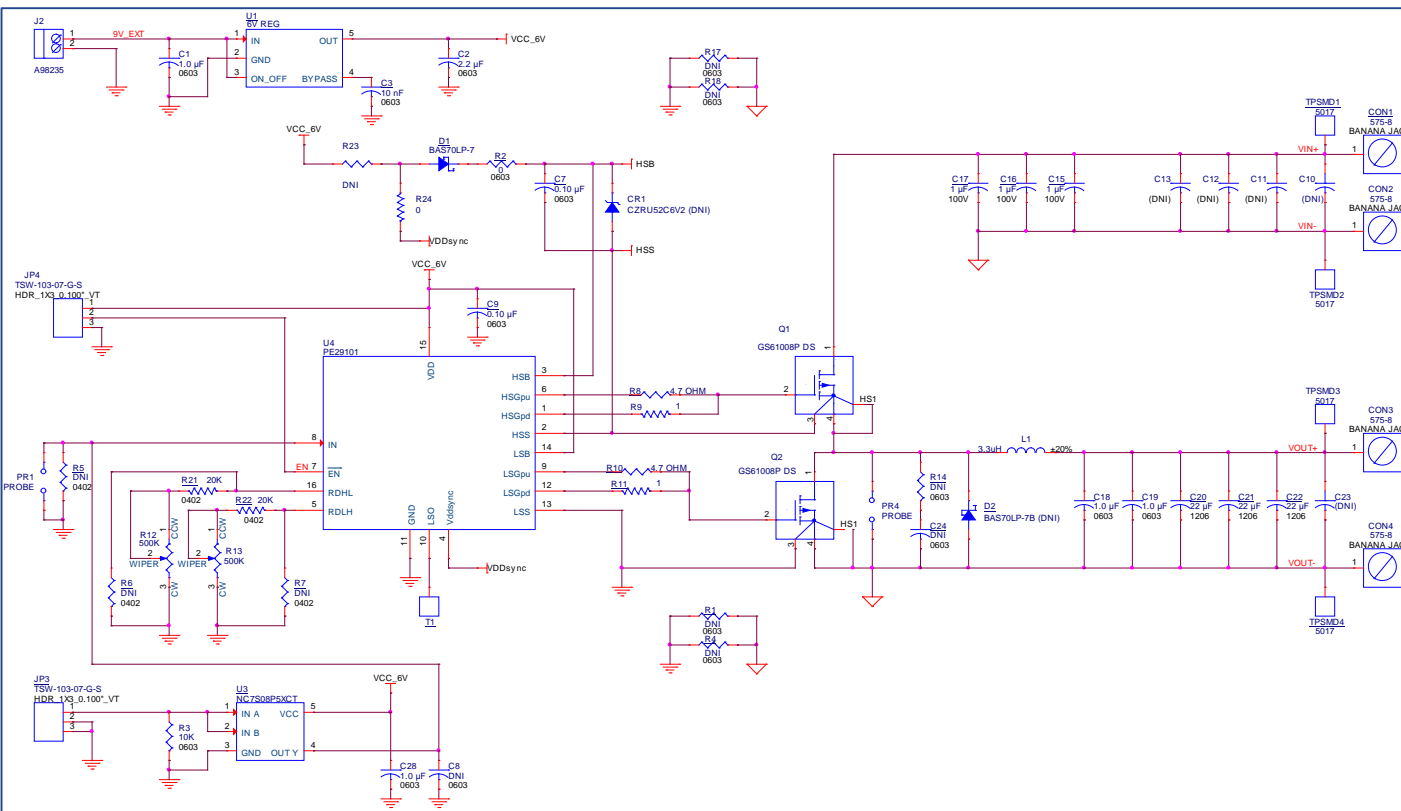 


<http://www.psemi.com/newsroom/new-products/666336-pe29100-gan-fet-driver>


100V half bridge GaN driver – PE29102

PE29102 - 60V Half Bridge GaN driver, optimized for high frequency applications:

- Class D Audio, DC/DC, wireless power charging

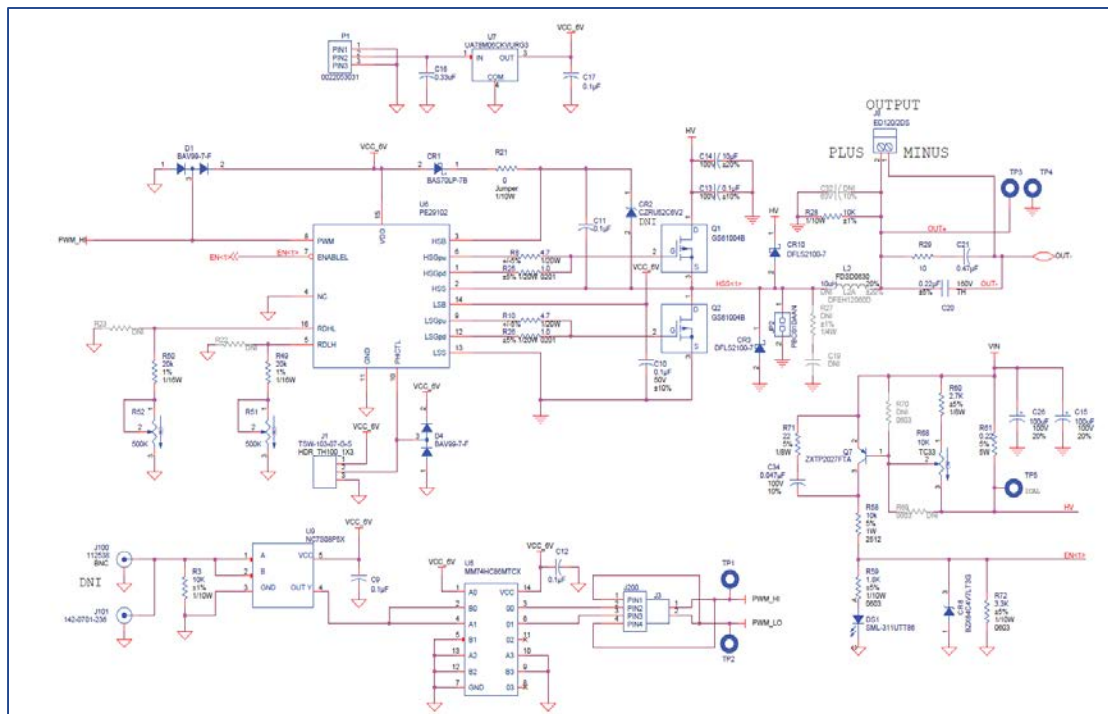

GS61004B-EVBCD

 


100V GaN E-HEMT Full Bridge Evaluation Board, optimized for Class D Amplifiers

For more details on the GS61004B-EVBCD evaluation board, visit: <http://gansystems.com/design-center/evaluation-boards/>

Non-isolated low side driver for GaN

- For single-ended applications (Class E, Flyback, Push-pull etc), or
- Used to adapt MOSFET gate drive bias to 5-6V drive for GaN (low or high side)



LM5114 low side driver

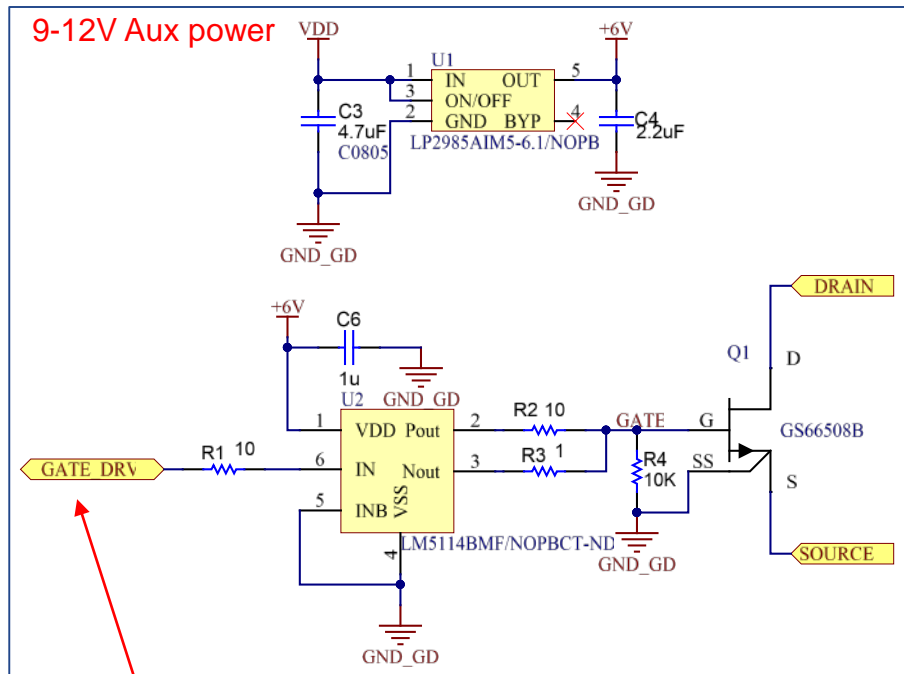

From controller logic signal (3.3/5V) or MOSFET driver output (up to 14V)



uP1964 GaN Driver

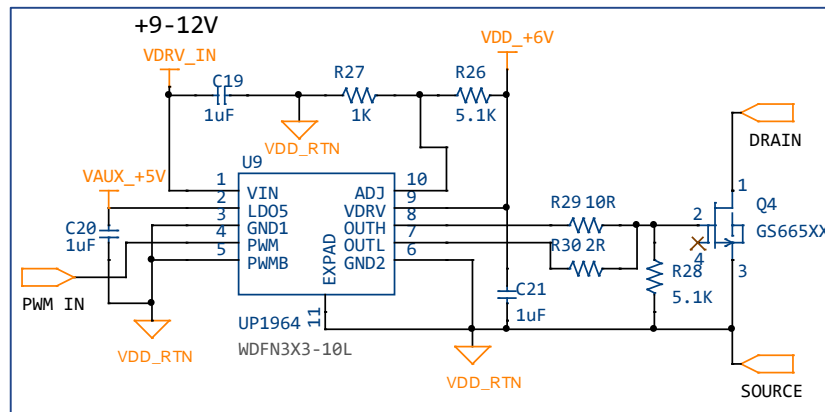 - integrated regulator for 6V bias
- 5V LDO
-



- ❑ [Basics](#)
- ❑ [Gate Drive Design considerations](#)
- ❑ [Design examples](#)
- ❑ [PCB Layout](#)
- ❑ [Switching Testing results](#)


Traditional PQFN + Wire Bond

  

Embedded GaN_{PX}[®] package

Innovative packaging for high speed GaN device:

 - Ultra-low inductance: high frequency switching
- Near chip-scale embedded packaging
- No wire bonding: high reliability
- Better C_{TE} match to PCB: Temp cycle reliability*
- Low thermal resistance $R_{\theta JC}$



- High dV/dt
- Low V_{DS} overshoot
- Better EMI


[*] GaN_{PX}[®] package passed 1000hr IPC9701 solder joint reliability test, condition: 12-Layer 2.5mm PCB, 5oz inner copper and 2oz outer copper.

Design for GaN^{PX}® embedded package

- GaN^{PX}® package bottom-side cooled (B, P)
- GaN^{PX}® package Top-side cooled (T)
- Thermal design

Minimize layout parasitics in the following order:




 
1. Common source / mutual inductance L_{CS}
2. Gate loop inductance L_G
3. Power Loop inductance L_{loop}
4. Drain to gate loop capacitance C_{GD_ext}
5. Isolation coupling capacitance C_{ISO}



GaN_{PX}[®] package: Bottom-side cooled family (B)

- Embedded package with extremely low inductance
- GS66508B includes dedicated kelvin source pin (Source sense - SS)
- PCB cooling using thermal pad (S) and vias or metal core PCB for high power application

GS66508B (650V, 30A, 50mΩ)

  
 
 


Use SS pin for gate return

GS66504B/GS66502B (650V, 15/7A, 100/200mΩ)





GS61004B (100V/45A, 15mΩ)

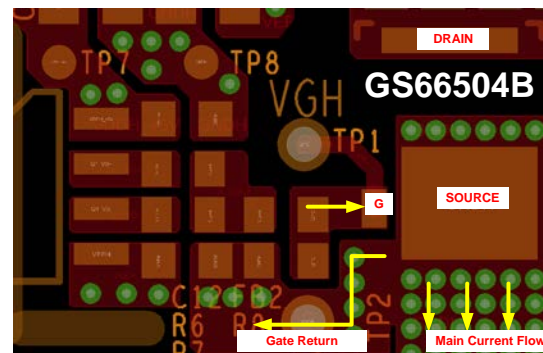  


Create Kelvin source on PCB

- Similar to B type except substrate (thermal pad) is floating on the package
- Use SS pin for kelvin source connection
- **The thermal pad must be always connected to its source pin on PCB**


GS61008P (100V/90A, 7.5mΩ)

  

- 1 Use/create kelvin source to separate drive return and power ground (low L_{CS}). Physically separate high current loop and drive loop areas to minimize noise coupling
- 2 Minimize pull-down loop (Gate \rightarrow R3 \rightarrow U1 \rightarrow C2 \rightarrow GS_RTN, locate U1 and C2 close)
- 3 Minimize turn-on (pull-up) loop (locate C1 close)
- 4 Isolate and avoid overlap between gate drive and Drain copper pour
- 5 Isolate and avoid overlap from Drain/Source to the control grounds (CMTI, dv/dt)

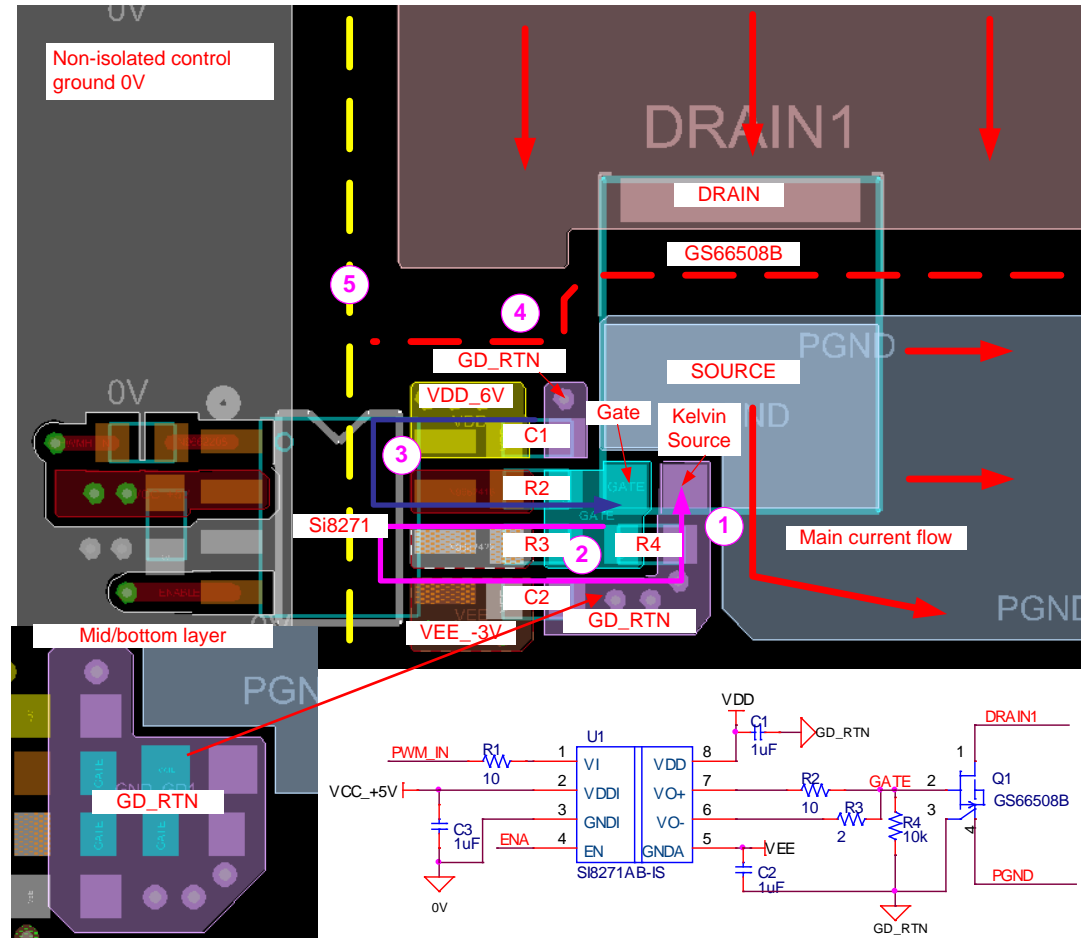

- 1 Keep out area: Avoid placing traces or vias on the top layer of the PCB, directly underneath the top-side cooled package. This is to prevent potential electro-migration and solder mask isolation issues during high temperature or/and voltage operation.
- 2 Symmetrical dual gates are provided for flexible layout and easy paralleling. Either gate drive can be used. If the second gate is not used, it should be left floating.
- 3 A separate Source Sense pin is not provided on our top-side products because of the ultra-low inductance of our GaN_{PX}[®] packaging. The Source Sense pin functionality can be implemented by routing a Kelvin connection at the side of the Source pad. This can be done at either side of the source pad for layout optimization.

 



Design the half bridge power stage with tight loop and low inductance

Layout guidance

- Recommend to use 4-Layer PCB
- Use 2nd layer as ground return
- Use SMD MLCC decoupling caps and locate them close to GaN
- Use multiple decoupling caps to reduce ESR/ESL and create balanced power loop
- Locate drivers close to the gate
- Use kelvin source for driver return



Half bridge design 1

  Use layer 2 as ground return (4-layer PCB)




Half bridge design 2

Only use top layer for power loop

  

 - ❑ [Basics](#)
- ❑ [Gate Drive Design considerations](#)
- ❑ [Design examples](#)
- ❑ [PCB Layout](#)
- ❑ [Switching Testing results](#)




PWM Signal/+5V VCC connector

VDC-


VDC+

VSW


GS66508B-EVBDB PCB Layout

 


Top Layer

 

Mid layer 1

 



Mid layer 2

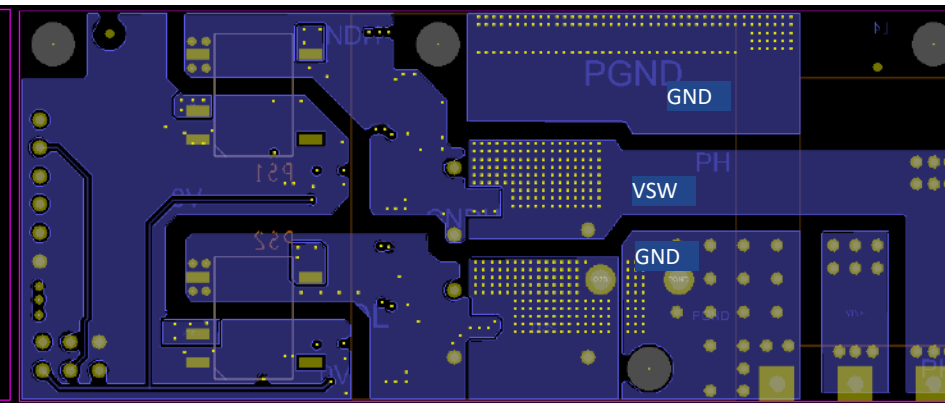

Bottom Layer

Double pulse switching test



- GS66508B hard switched up to 400V/30A

  

GS66508 Double pulse switching test

$V_{DS}=400V, I_D=30A$ Hard Switching Turn-on

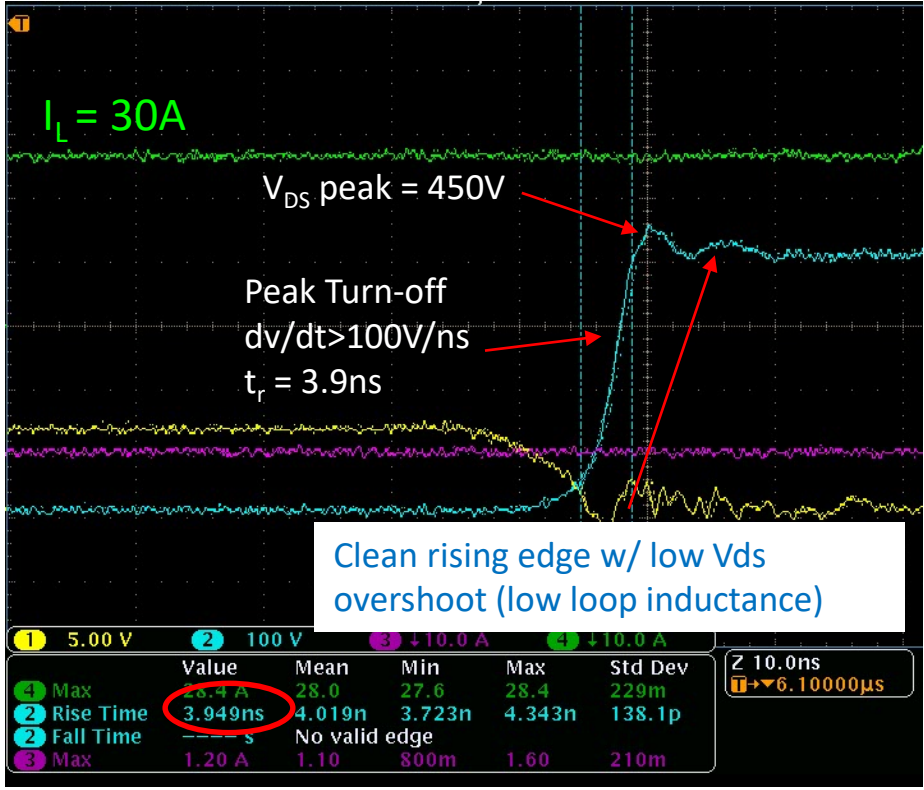 $V_{DS}=400V, I_D=30A$ Hard Switching Turn-off




- This application guide summarized the key design considerations for GaN Systems GaN E-HEMTs. We started with the fundamental aspects of GaN E-HEMTs and then the gate drive design considerations were discussed. A list of recommended drivers and several gate drive reference designs were provided.
- The second part of this guide focused on the PCB layout and discussed the layout best practice by using GaN Systems embedded GaN_{PX}[®] packages.
- At last a real half bridge evaluation board design following the design recommendations in this document was built and its switching performance was tested.
- The switching test results showed fast and clean hard switching waveforms up to full rated current 400V/30A with minimum ringing/overshoot. This concluded that with optimum gate drive and board layout combined with low GaN_{PX}[®] package inductance, GaN E-HEMTs exhibit optimum switching performance

- **Datasheets, spice models:** <http://www.gansystems.com/transistors.php>
- **Evaluation boards:** <http://www.gansystems.com/eval-boards.php>
- **Application notes:** <http://gansystems.com/design-center/application-notes/>
- **PCB Footprint libraries:** <http://www.gansystems.com/transistors.php>
- **FAQ:** <http://gansystems.com/gan-transistors/faq/>
- **Papers and Presentations:** <http://gansystems.com/design-center/papers/>

Tomorrow's power today™

GaN Systems

 

GaN Systems

www.gansystems.com • North America • Europe • Asia