



Highly Efficient High Power PA Design for Resonant WPT

March 2018

- Brief company overview
- WPT applications
- MHz vs kHz
- Tx topologies for WPT
- High power PA design for WPT with GaN Systems devices
 - 300W Class EF2 PA with GS66508B
 - 100W Class FE2 PA with GS61008P
- GaN Systems offering for WPT application

GaN Systems company overview



Market leader for gallium nitride (GaN) power transistors



- GaN-on-Silicon power transistors for the power conversion market
- Industry's most extensive & highest-performance product line
 - Enhancement mode devices
 - 100V & 650V devices; industry-best performance

Global company with decades of experience in GaN

- HQ and R&D in Ottawa, Canada
- Sales & App. Eng. in Germany, Japan, China, Taiwan, Korea, USA
- World-class fabless manufacturing and advanced packaging
- Parts shipping overnight from Mouser since 2014



A complete GaN product portfolio

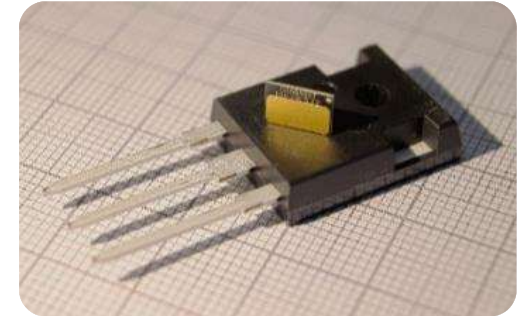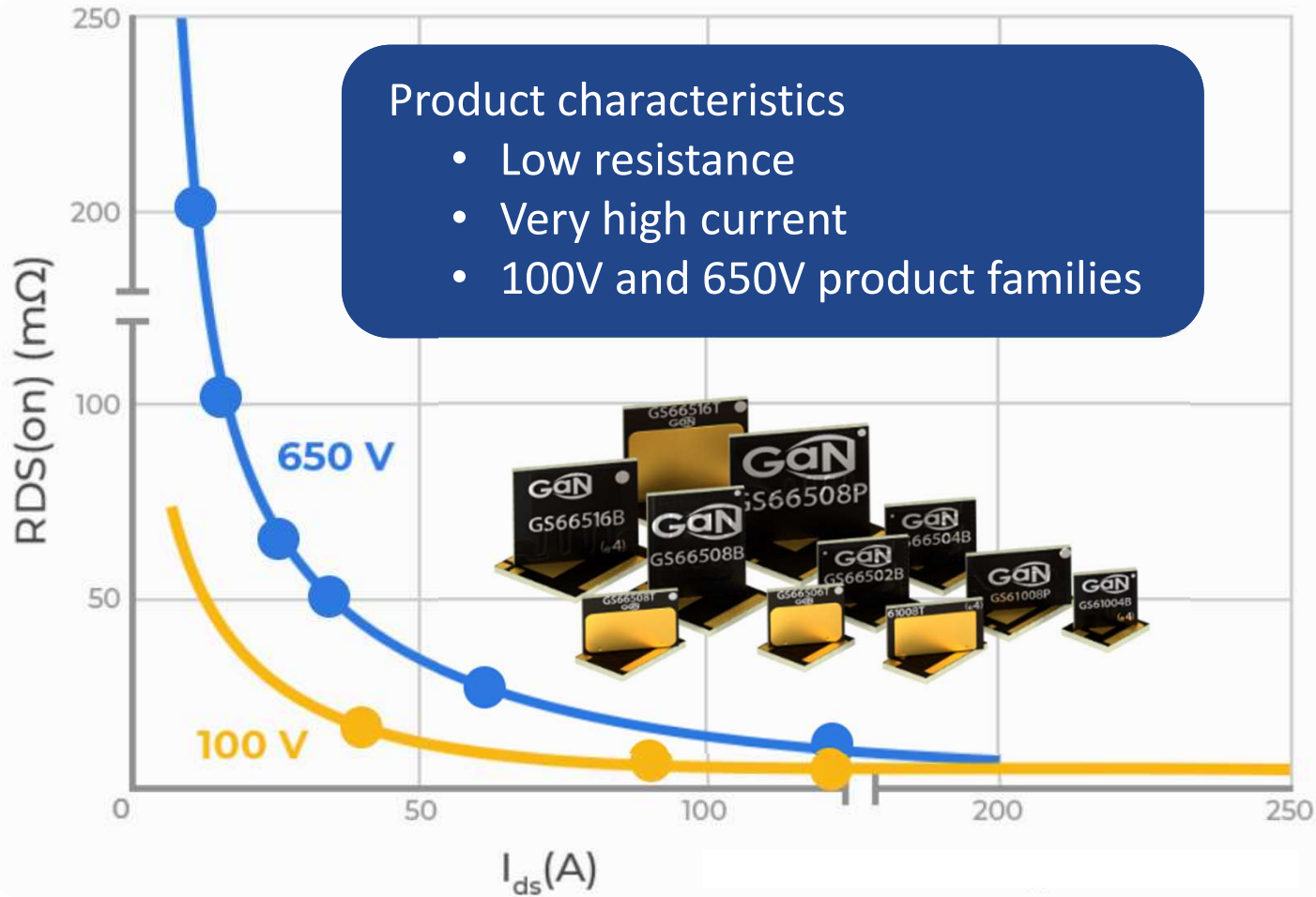

GaN Systems device on a traditional TO-247 package

Everything. Applications for Cutting the Cord

- Laptops
- Phones
- Power Tools
- Home appliances
- eBikes
- Drones
- Robots
-





30W



65W



180W



1000 to
2500W



6000 to
22000W

Trends

- Fast charge, variable Tx/Rx spacing, increasing power levels

Technology Drivers

- High switching frequency, high current, high voltage

Standard organization	Wireless Power Consortium (Qi)	AirFuel Alliance (Rezence)
Method	Inductive	Resonant
Frequency range	80 to 300 kHz	6.78 MHz
Max. Xfr range	5 mm	50 mm
No. charging devices	One	Multiple ok.
Communications system	Load modulation	Bluetooth


- **WPC**
 - Formerly Qi
 - Primarily inductive
- **AirFuel**
 - Formerly PMA, AW4P, Rezence
 - Primarily resonant

GaN compatible with all standards

MHz vs kHz frequencies – Inverter


kHz WPT systems

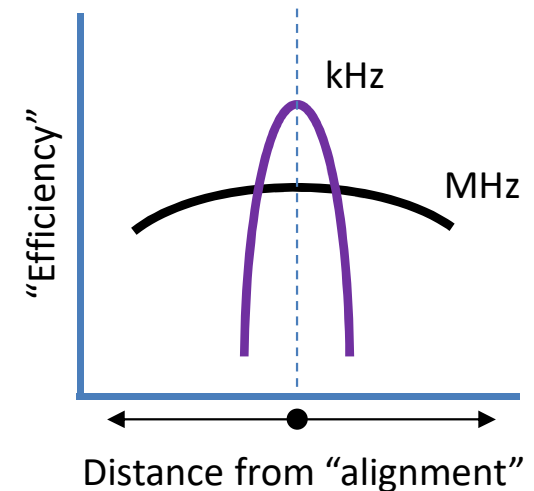- Good efficiency **only** for very low distances, a few millimeters, and **only** when the coils are precisely aligned
- Efficiency drops rapidly as the coils move apart and the induced voltage at the receiver becomes very low and therefore is inefficient to rectify.
- Uses a lot of ferrite to guide the magnetic flux, this limits the position of the receiver to a fixed a position



MHz WPT systems

- High power transfer efficiency across a much greater distance
- Allows for better tolerances to coil misalignment
- The inverter 'sees' more of the receiver, i.e. the reflected resistance (R_{ref}) of the load increases
- Therefore power can be transferred at lower coil currents
- Lower coil currents mean less conduction losses in the inverter, resulting in higher inverter efficiency and higher system efficiency

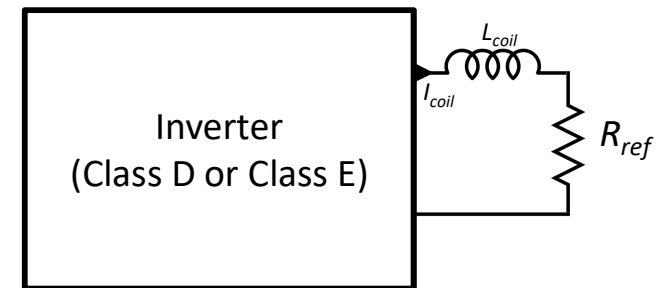




$$R_{ref} = \frac{\omega^2 M^2}{R_{Load}}$$

Source - Transmitter (Tx)

- 1) Amplifier
- 2) Impedance Matching Network
- 3) Tx Coil

Device - Receiver (Rx)

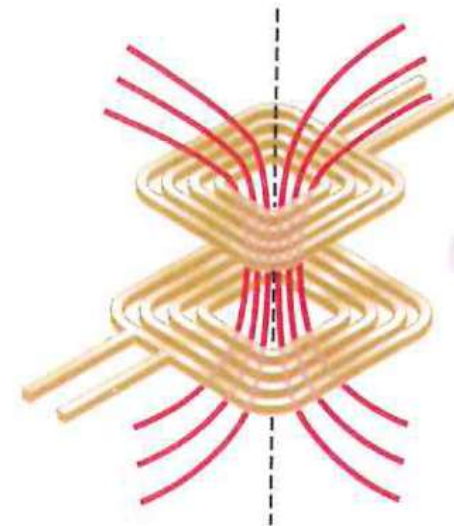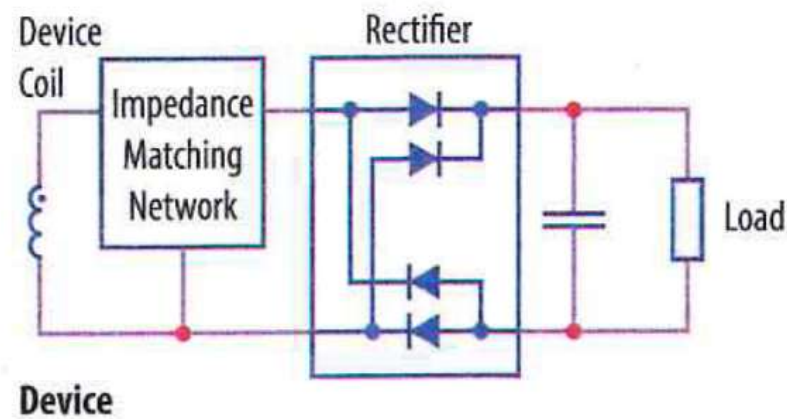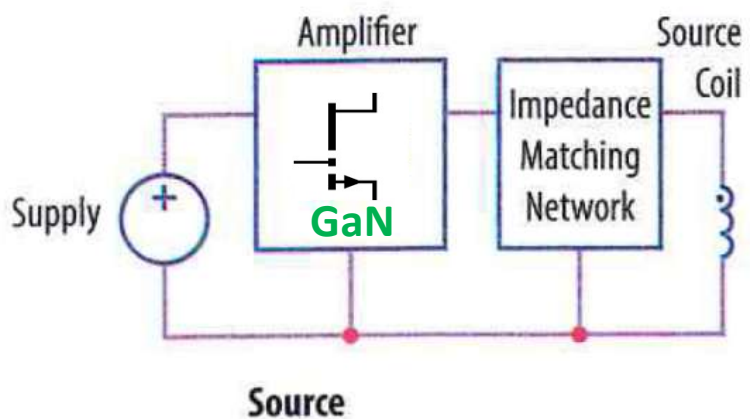- 1) Rx Coil
- 2) Impedance Matching Network
- 3) Rectifier
- 4) Load



GaN FETs are used in the Transmitter Amplifier

Class D/E/EF2 topologies

Class D with ZVS

$$P = \frac{8}{\pi^2} \frac{V_R^2}{R_L} = \frac{8}{\pi^2} \frac{R_L}{(R_L + r_{sat})^2} V_{cc}^2.$$

$$\eta = \frac{P}{P_0} = \frac{8}{\pi^2} \cong 81\%.$$

Class E with shunt C




$$R = \frac{8}{\pi^2 + 4} \frac{V_{cc}^2}{P_{out}} = 0.5768 \frac{V_{cc}^2}{P_{out}}.$$

$$\eta = \frac{P_{out}}{P_0} = \frac{P_0 - P_{sat}}{P_0} = 1 - \frac{P_{sat}}{P_0}.$$

Class EF2


$$P_o = 0.6105 \frac{V_{IN}^2}{R_L}.$$
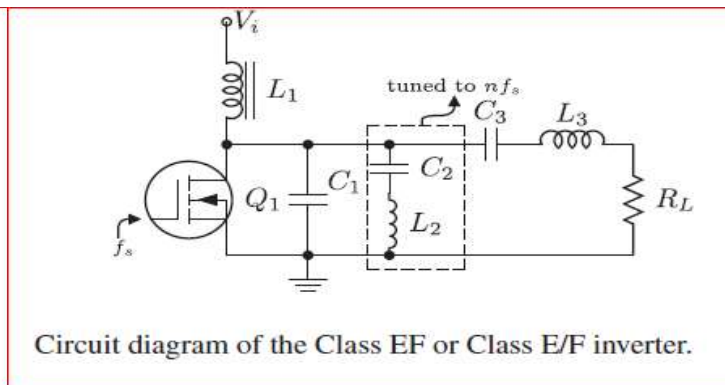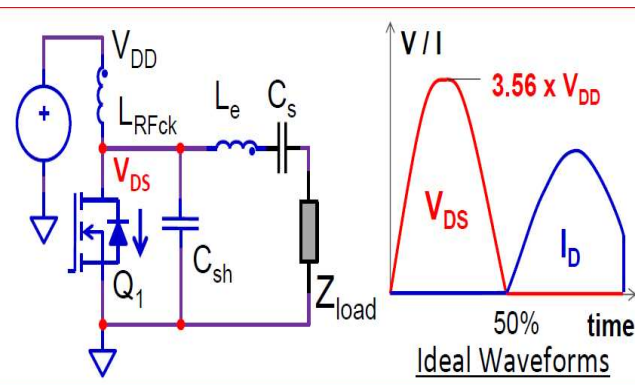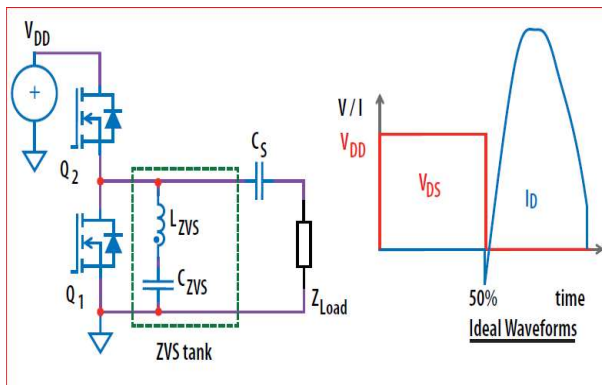
$$\eta = \frac{1}{1 + P_{L1} + P_{DS} + P_{C1} + P_{L2}C_2 + P_{L3}C_3 + P_{t_f}}.$$




- Simulations of MOSFET at 6.78MHz, 25V DC
 - Class D : Max efficiency 82.4%
 - Class E : Max efficiency 93.9%
 - Class EF2 : Max efficiency 93.4%


Class D with ZVS

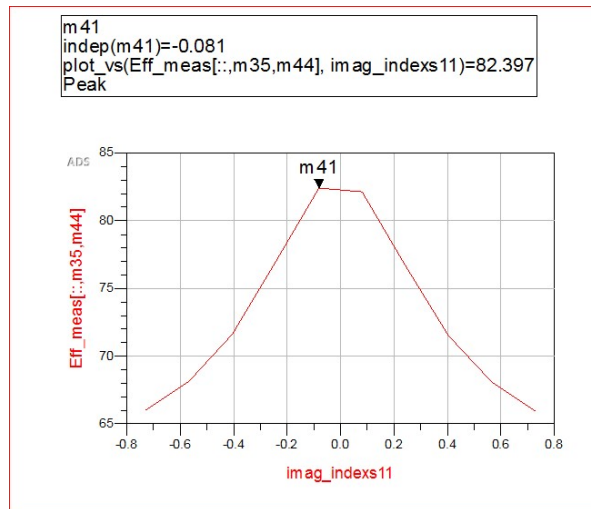

Class E with Cshunt

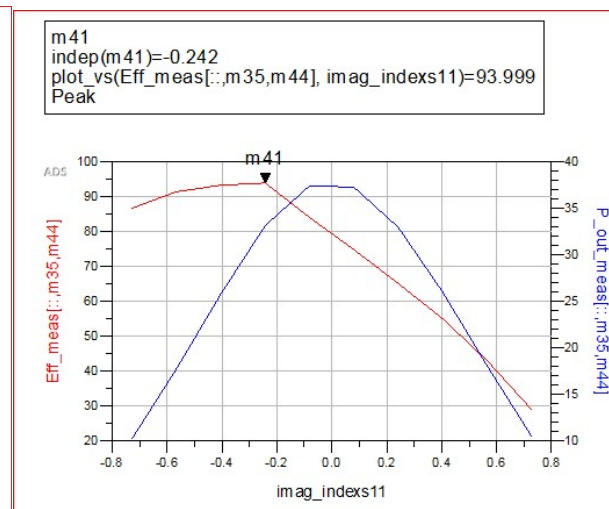


Class EF2

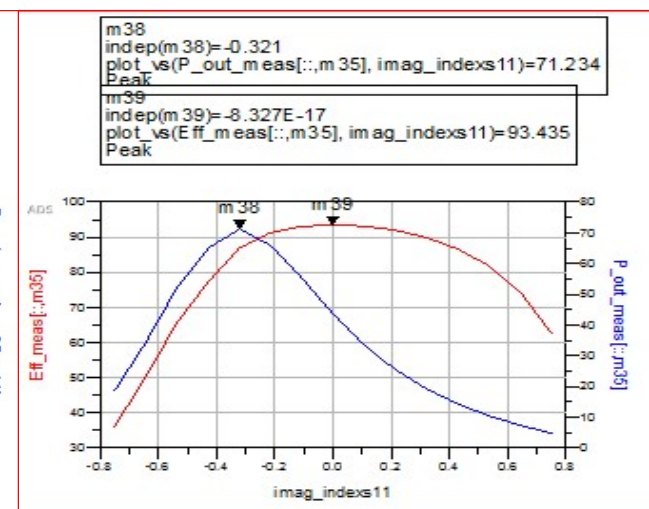


Impedance window comparison typologies Class D/E/EF2

- Single ended configuration at 6.78MHz, 25V DC, red = power, blue = efficiency
 - Class D : low impedance point is point of maximum power and efficiency, power is limited by dissipation power, so PA cannot operate at maximum power and efficiency
 - Class E : low impedance point is the maximum power point, not near its optimum power and efficiency point
 - Class EF2 : both efficiency and power are maximized


Class D with ZVS

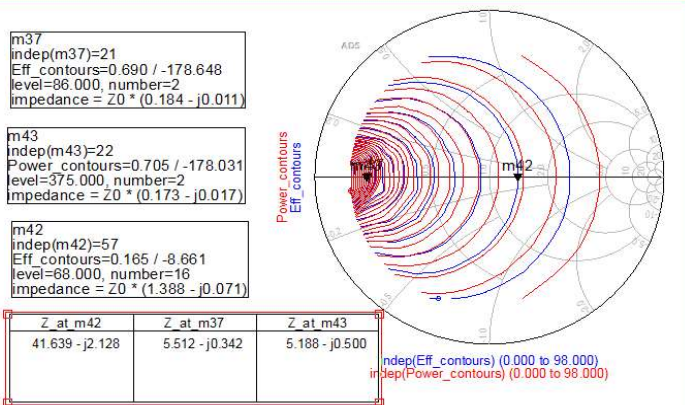

Class E with Cshunt



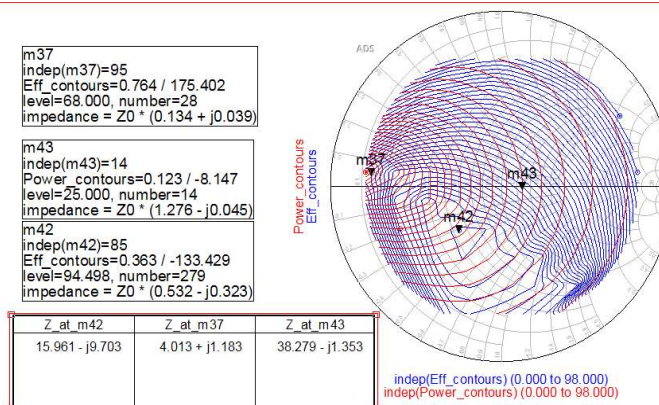


Class EF2

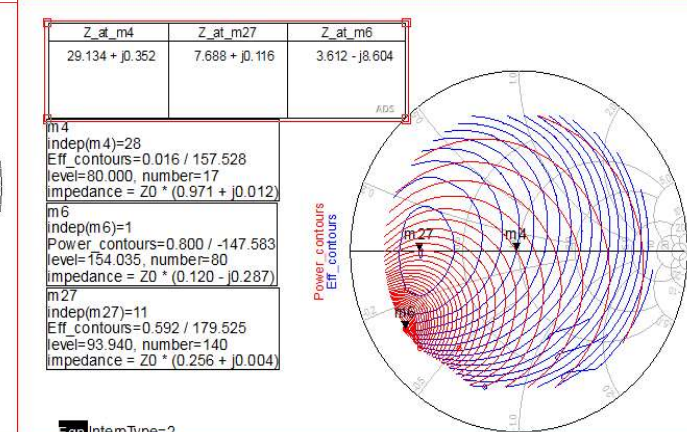

Turn key solution of Class EF2 150W/300W PA for WPT

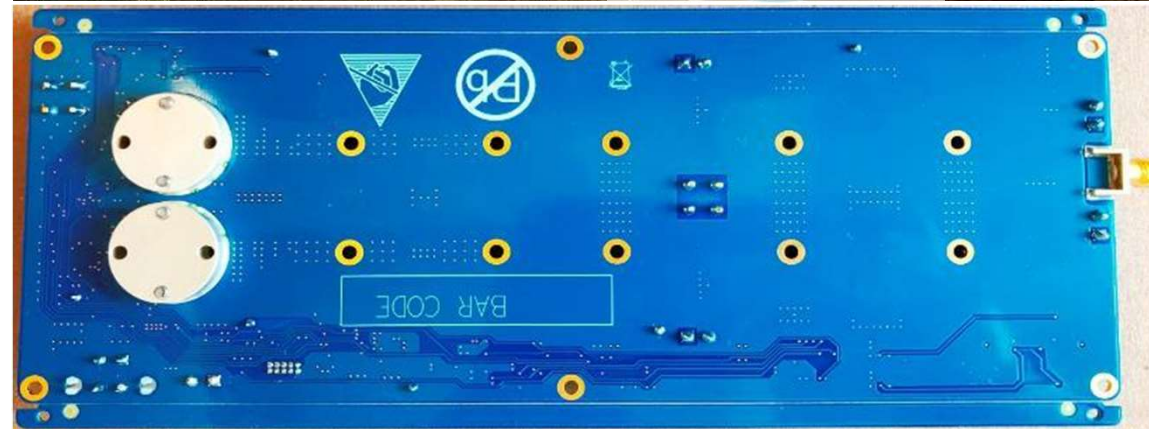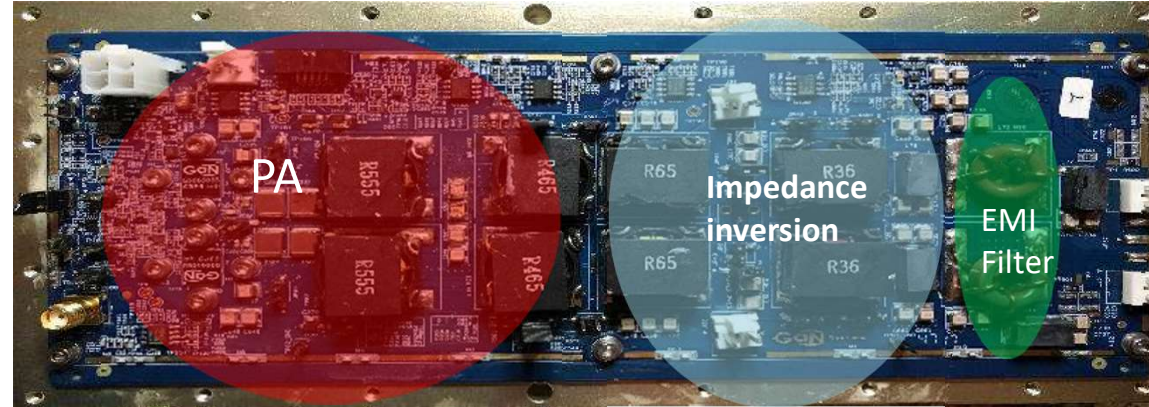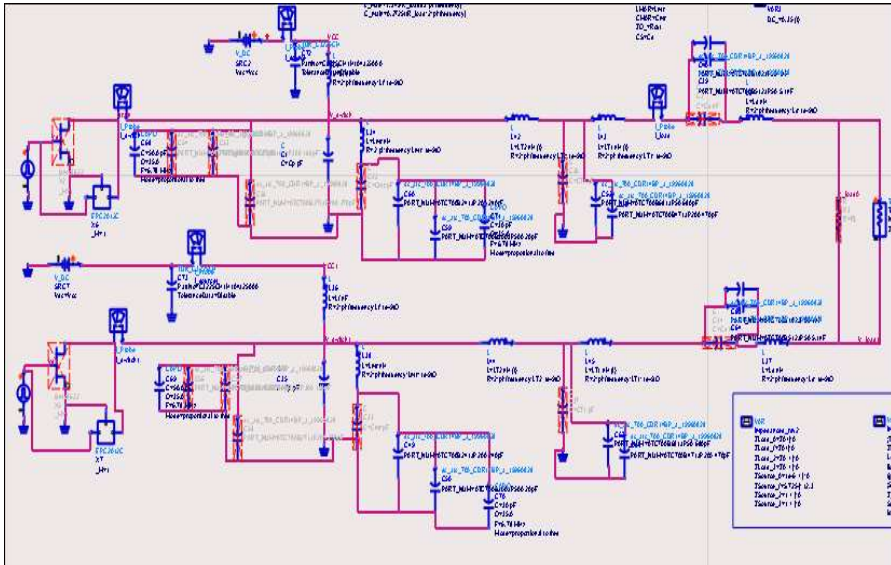
GaN Systems WPT Class EF2 turn key PA solution




- Device 650V, GS66508B, Push Pull
- Thermal solution: copper coins solder down
- Design built in EMI filter
- Unique output filter network design naturally provide constant current

Designed to simultaneously achieve power, efficiency, EMI and constant current behavior.

150W PA Efficiency

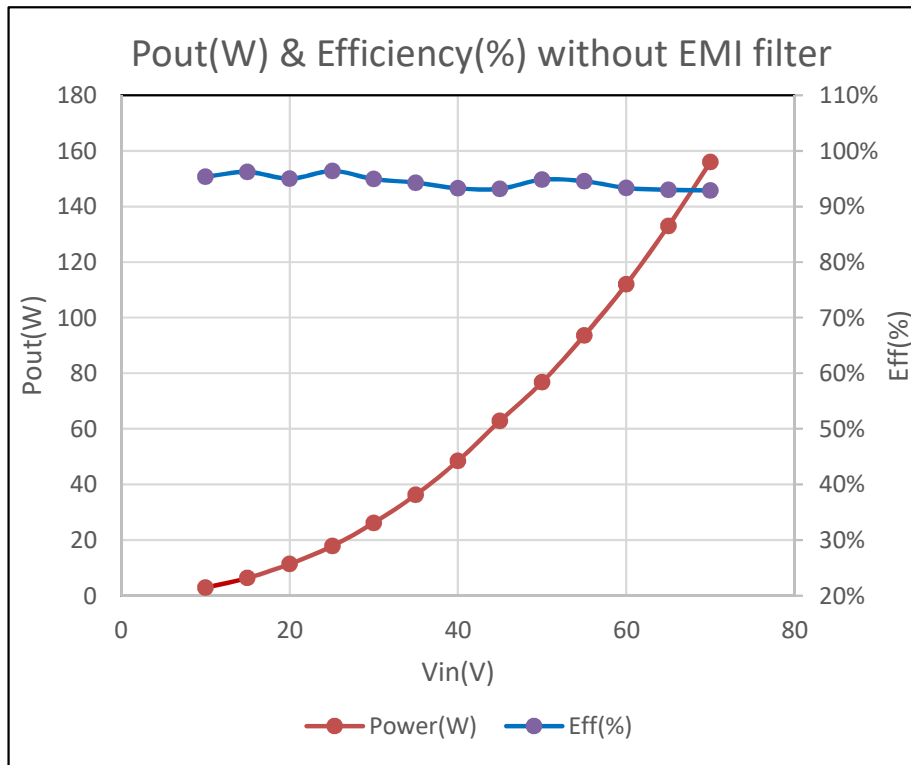


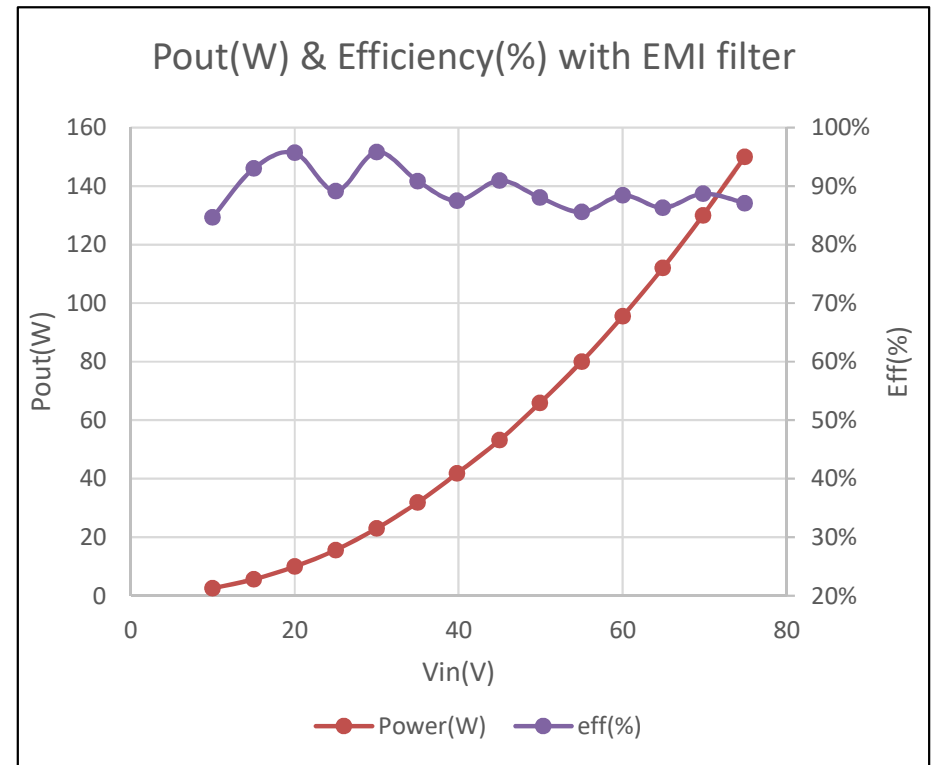
- 50ohm load
- 156W output
- 93% efficiency
- T rise 2 degree at device



- 50ohm load
- 150W output
- 87% efficiency
- T rise 2 degrees at device


Harmonics performance before EMI filter

Harmonics performance with EMI filter

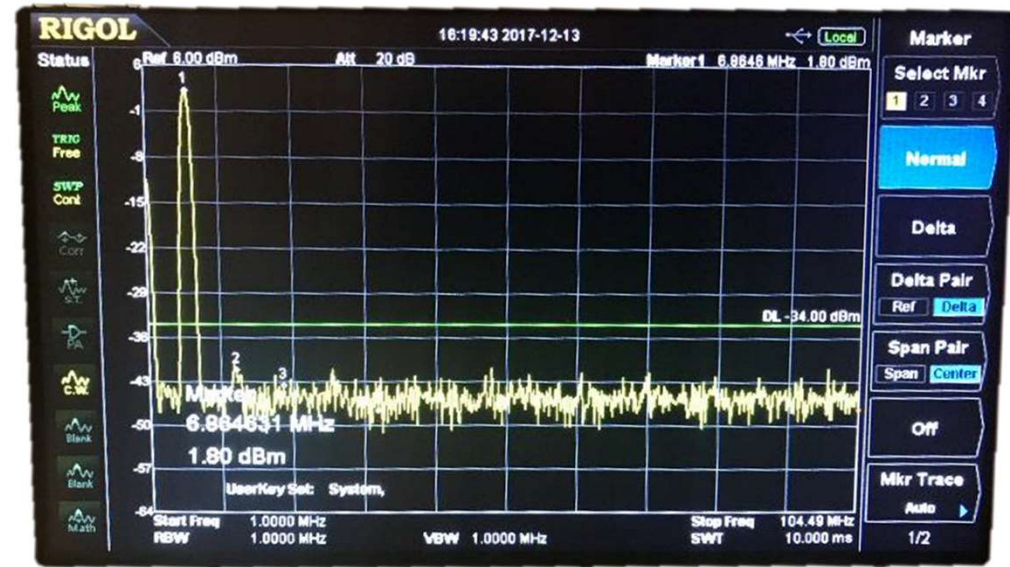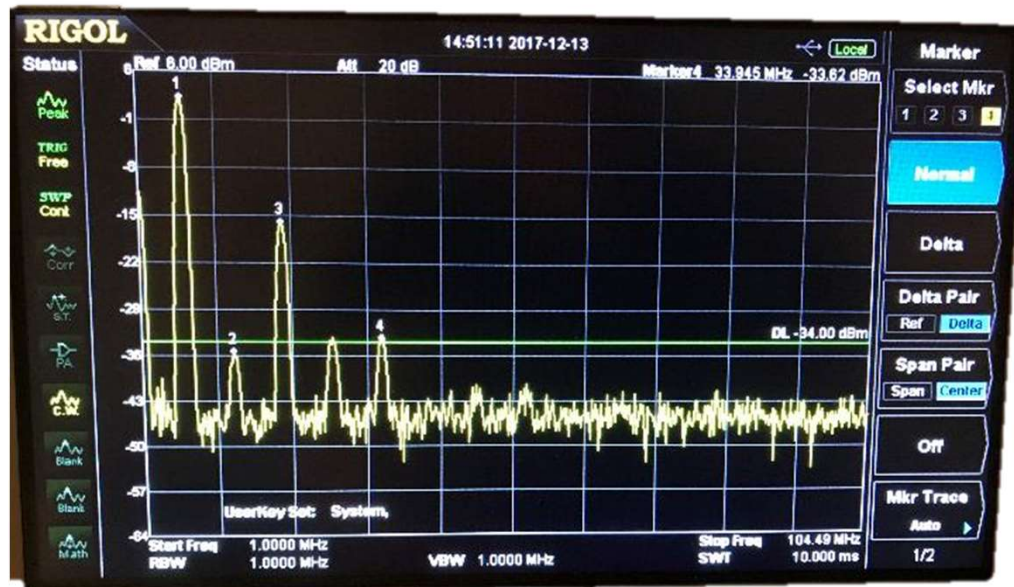


At 150W output power, 3rd harmonic rejection is -42dBc with EMI filter, more than -60dBc rejection on high order harmonics

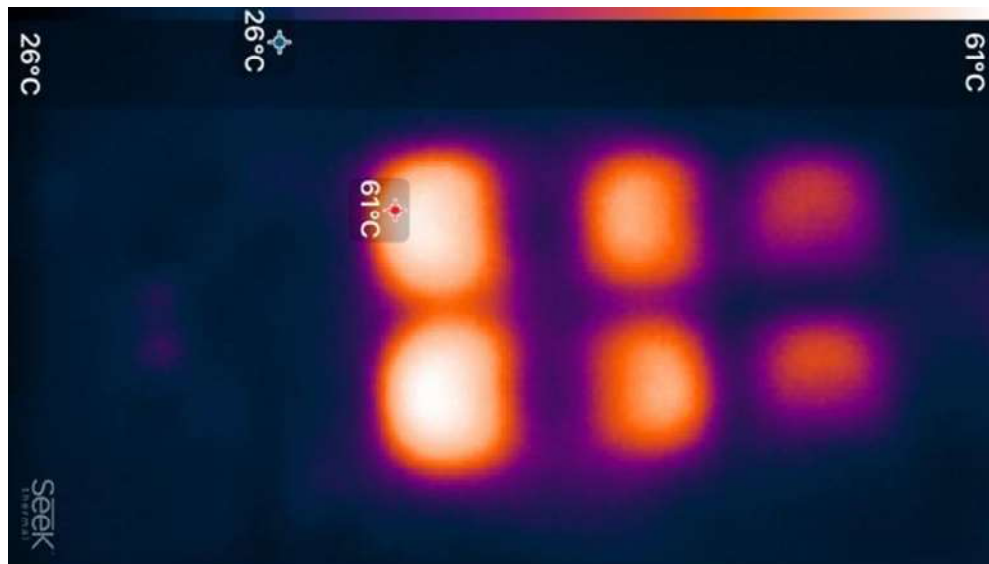Thermal picture without EMI filter at 70V




Thermal picture with EMI filter at 75V

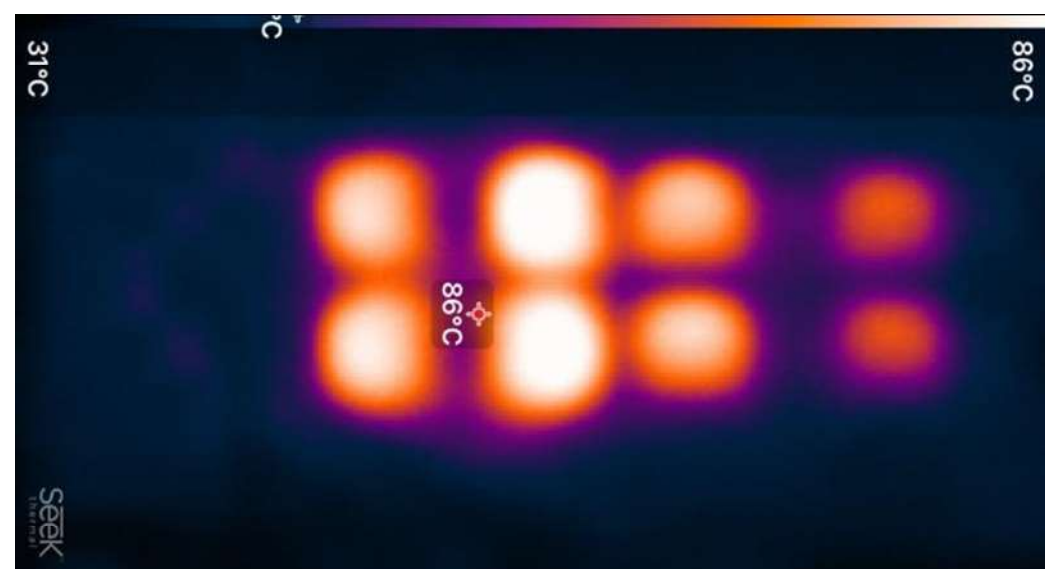

- At 150W output power without EMI filter, hottest point is located at RF choke inductor 61 degree C.
- Hottest point is located at 2nd harmonic shunt inductor, 86 degree C , temperature at device is in control, less than 31 degrees C.


150W PA System Test

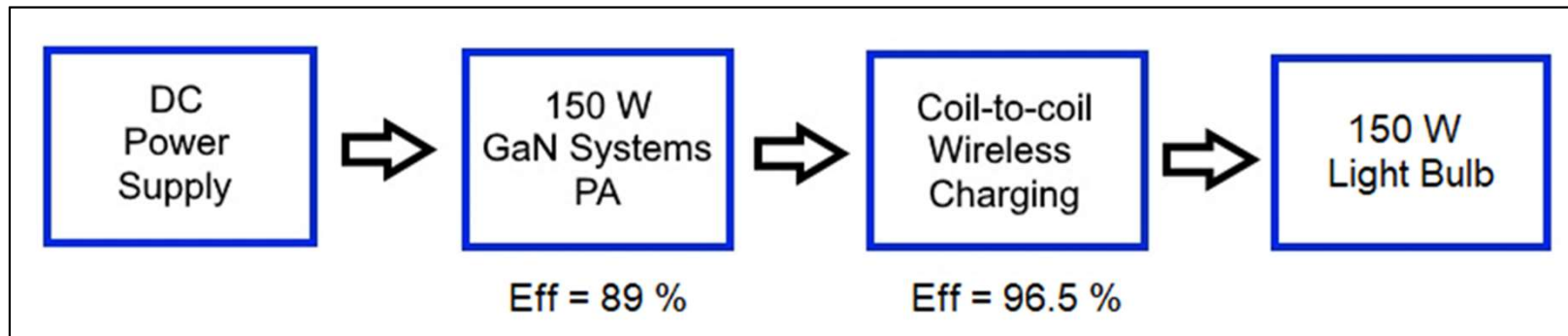

End to end efficiency = 86%



Power Ratings

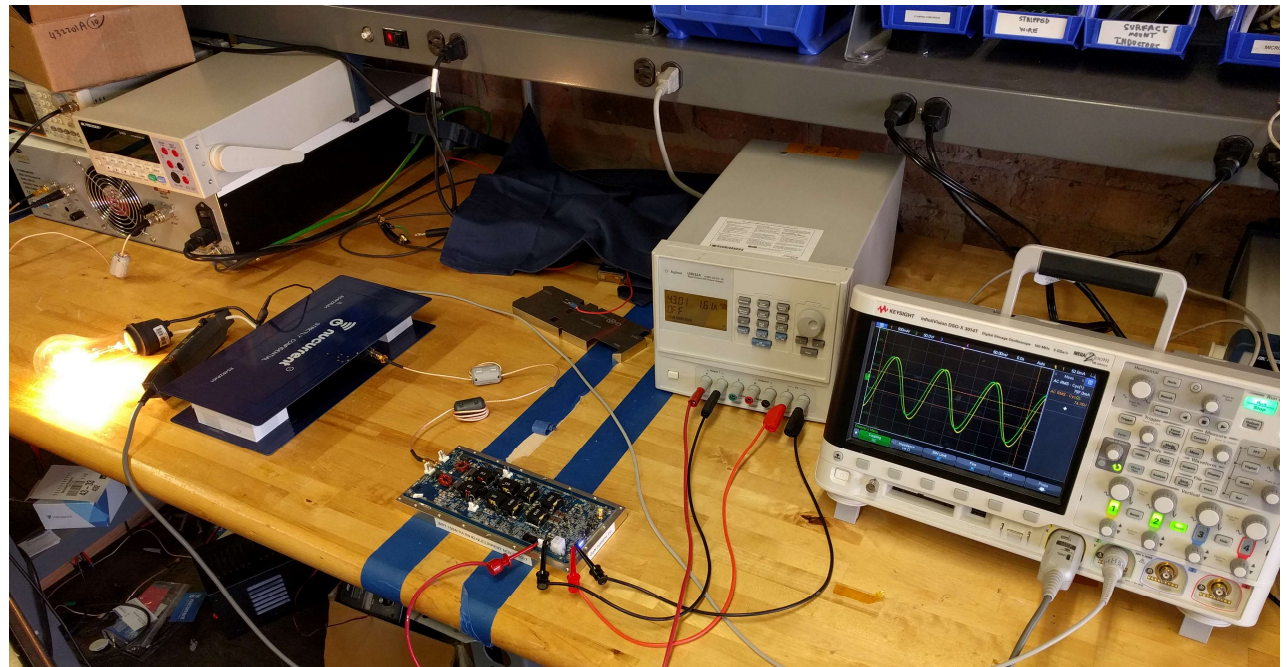- Input Voltage = 43 V (DC)
- Input Current = 1.61 A (DC)
- Output Voltage = 74.8 V (rms)
- Output Current = 0.8 A (rms)



Turn key solution of Class EF2 70W/100W PA for WPT

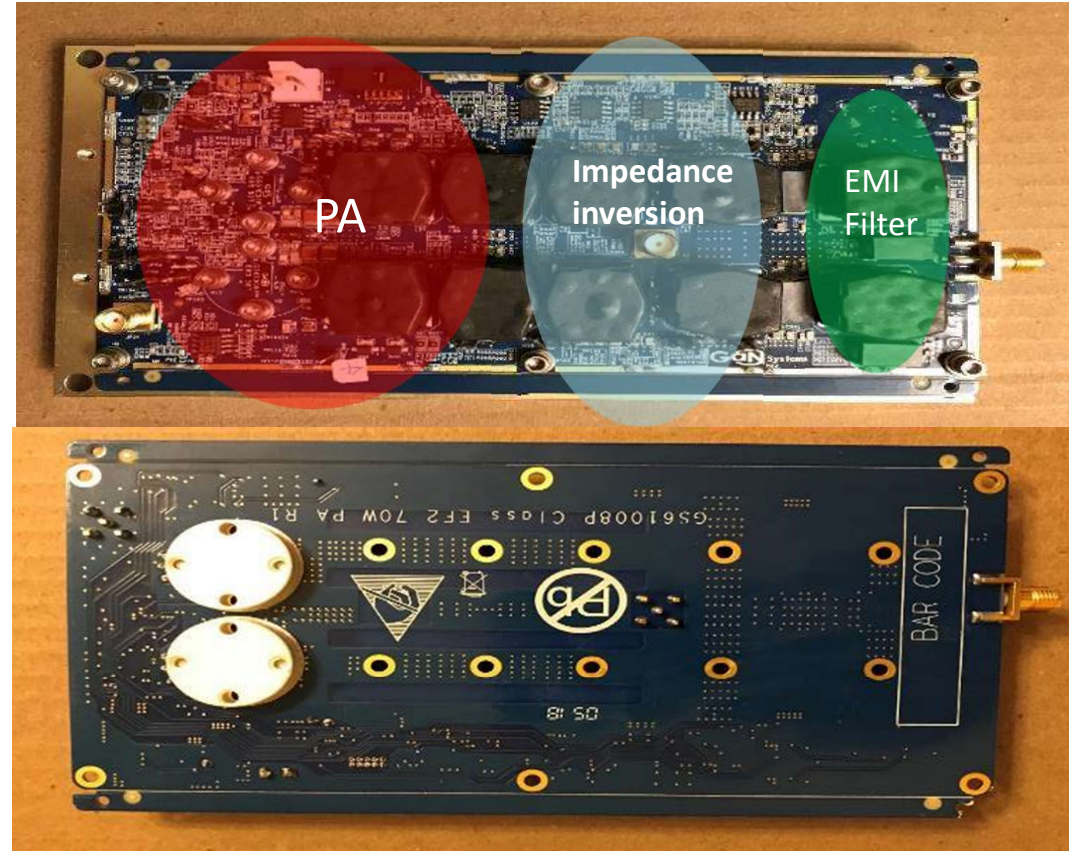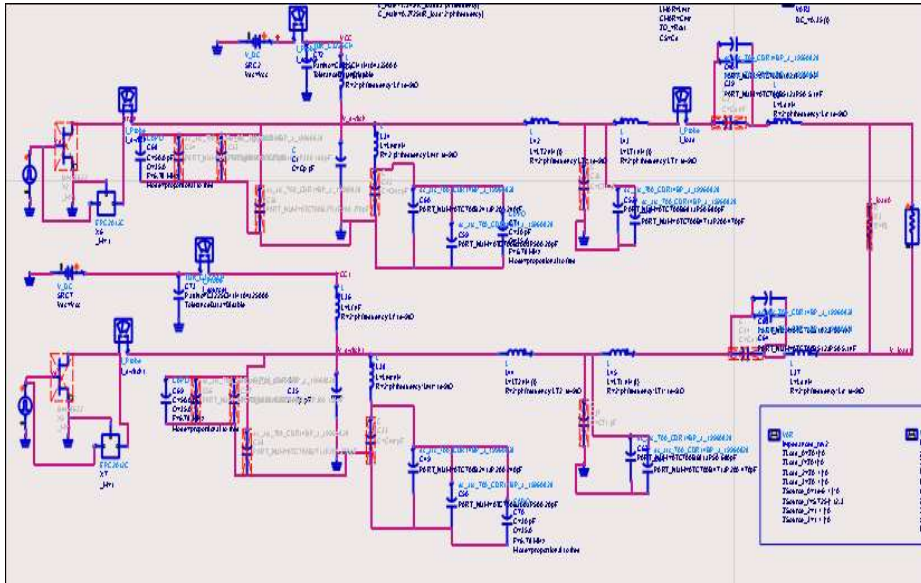
GaN Systems WPT Class EF2 turn key PA solution



- Device 100V, GS61008P, Push Pull
- Thermal solution: copper coins solder down
- Design built in EMI filter
- Unique output filter network design naturally provide constant current


Designed to simultaneously achieve power, efficiency, EMI and constant current behavior.

70W PA Efficiency and Thermals

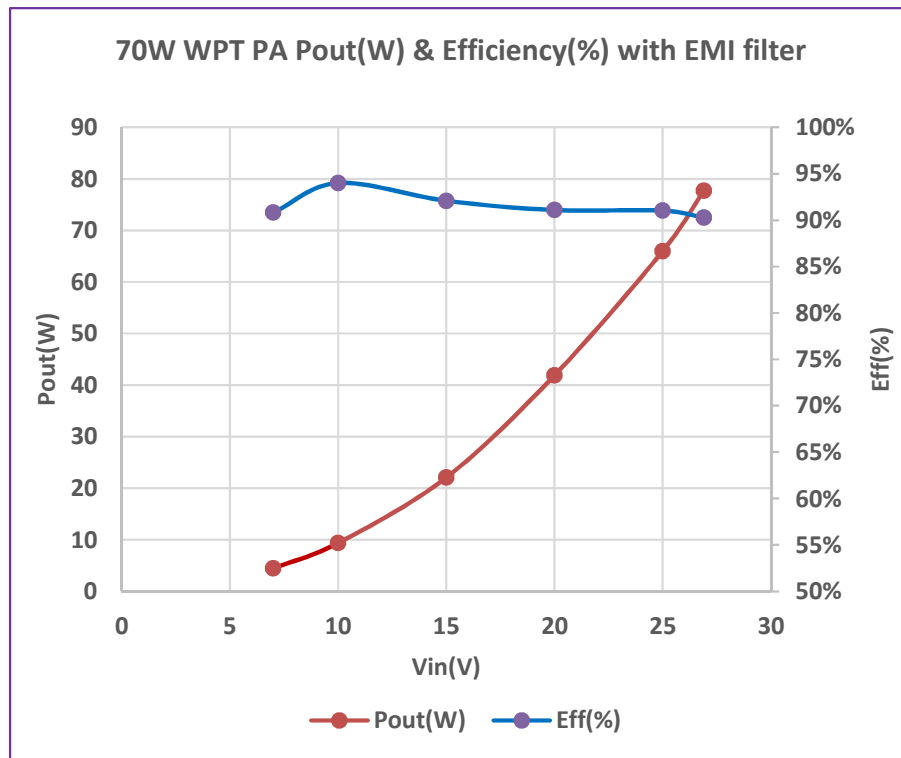


- 50ohm load
- 27V, 78W output
- 90% efficiency
- T rise is 2 degrees at the device

Thermal image with EMI filter at 27V

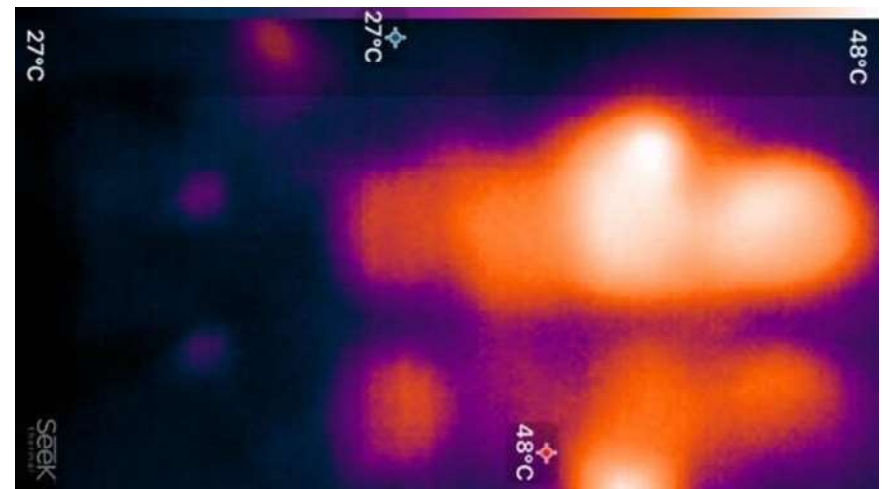


- 77W output power
- Warmest point is at RF choke, 48 deg. C
- Transistor temp is less than 31 deg. C

70W PA Class EF2 without EMI filter

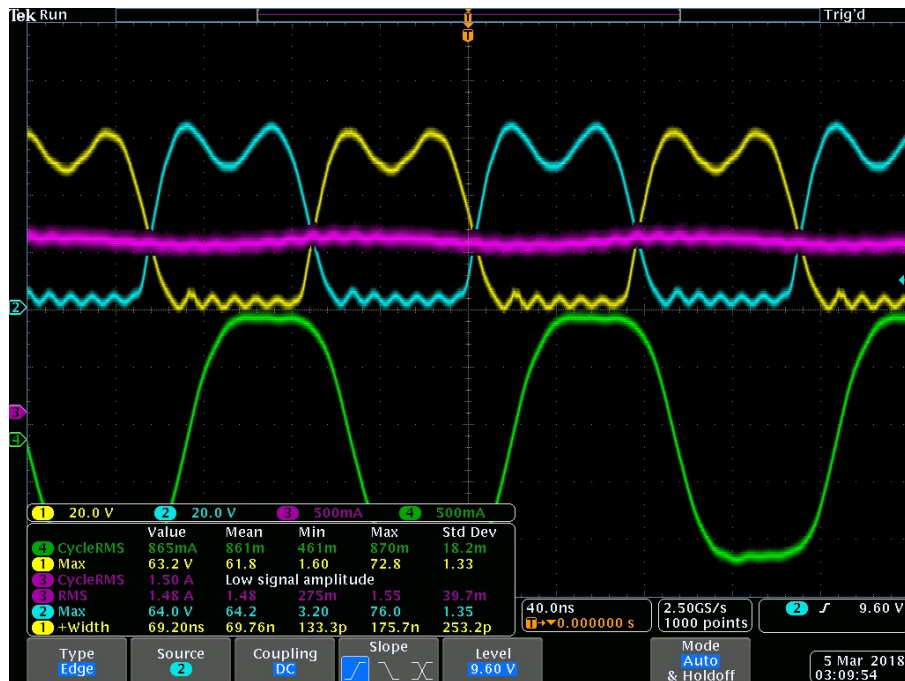

- Low stress voltage wave at both devices at 27V
- $V_{max}/V_{cc} = 2.3$ at 50ohm
- Output current is not a perfect sine wave due to harmonics

70W PA Class EF2 with EMI filter

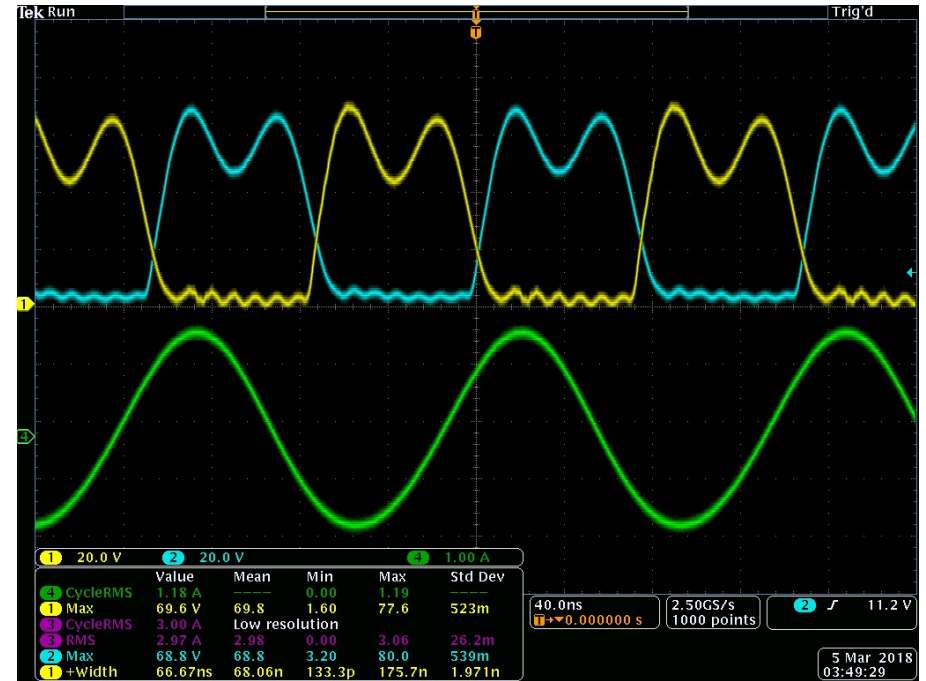

- Low stress voltage wave at both devices at 27V
- $V_{max}/V_{cc} = 2.6$ at 50ohm
- Output current is almost a perfect sine wave

High Power GaN devices for Resonant WPT

GS61004B



- 300W CW at 50V
- 1 kHz – 150 MHz
- 40 dB gain at 10 MHz
- 91% efficiency at 10 MHz
- GaNPX® package
- Handles >10:1 VSWR
- Advanced integrated design provides gate-source voltage range (-10V to +7V) to enhance performance when operating in switching modes such as Class C, E, EFn.

GS61008B



- 600W CW at 50V
- 1 kHz – 120 MHz
- 40 dB gain at 10 MHz
- 90% efficiency at 10 MHz
- GaNPX® package
- Handles >10:1 VSWR
- Advanced integrated design provides gate-source voltage range (-10V to +7V) to enhance performance when operating in in switching modes such as Class C,E,EFn.

GS66508B



- 600W CW at 100V
- 1 kHz – 80 MHz
- 37 dB gain at 10 MHz
- 91% efficiency at 10MHz
- GaNPX® package
- Handles >10:1 VSWR
- Advanced integrated design provides gate-source voltage range (-10V to +7V) to enhance performance when operating in in switching modes such as Class C,E,EFn.


DS66516B



- 1000W CW at 100V
- 1KHz – 80 MHz
- 37 dB gain at 10 MHz
- 90% efficiency at 10MHz
- GaNPX® package
- Handles >10:1 VSWR
- Advanced design integrated provides gate-source voltage range (-10V to +7V) to enhance performance when operating in in switching modes such as Class C,E,EFn.

GaN Systems enables compact, low cost, high power wireless charging

- **WPT is growing in many markets and applications**
 - Need high power, spatial freedom and high efficiency
- **MHz systems are better than kHz**
 - Wireless power is about mobility, you want to be able to charge and power devices without being limited to a fixed position. MHz provides this capability.
- **GaN Systems provides high performance solutions**
 - 100W and 300W PA kits demonstrate high efficiency at high power output
 - The Tx architecture design offers exceptional EMI performance
 - Enable end-to-end efficiency approaching 90%

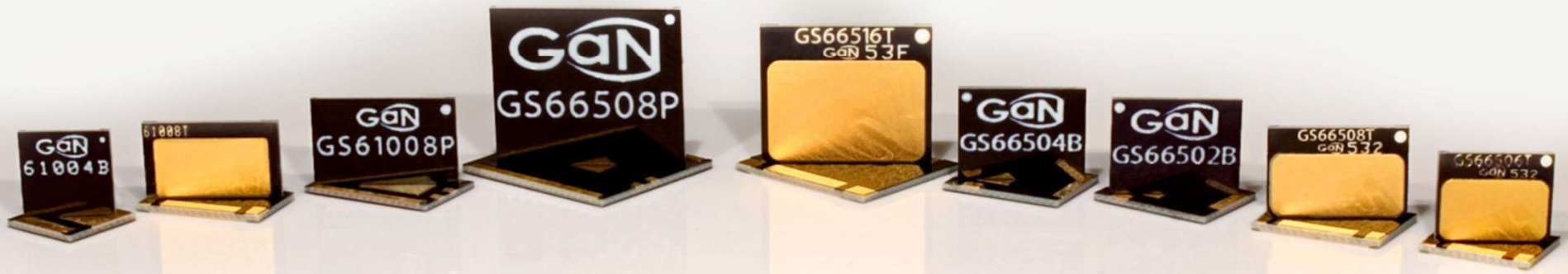

GaN Systems

www.gansystems.com • North America • Europe • Asia