



Systems

Design considerations of Paralleled GaN HEMT-based Half Bridge Power Stage

Last update: Rev.1 Aug-30-2016


- ❑ Paralleling design considerations
- ❑ Layout considerations for paralleling GaN
- ❑ Design example of 4_x paralleled GaN power stage
- ❑ Experimental results

What are key considerations when paralleling power switches:

Design parameters	Effect on paralleling	Desired
$R_{DS(on)}$	Affect static current sharing.	Positive temperature co-efficient for self-balancing
Gate threshold, $V_{GS(th)}$	Impact dynamic current sharing during turn-on and off. Lower V_{th} results in earlier turn-on and higher switching current/loss which creates positive feedback	Tight distribution, temperature independent or positive temperature co-efficient
Trans-conductance, g_m	Impact dynamic current sharing during turn-on and off.	Tight distribution, temperature independent or negative temperature co-efficient
Circuit design and layout	Balanced circuit layout are important for dynamic current sharing and stability of the paralleling operation. This is particularly critical for high speed power switches such as GaN/SiC	Minimize and equalize all layout parasitics to reduce circuit mismatch
Thermal	Affect the device temperature difference. T_j variation may cause dynamic or static current sharing issues depending on device characteristics.	All paralleled devices should have similar thermal resistance and installed on same heatsink for good thermal balance.

- GaN E-HEMT has positive temperature co-efficient $R_{DS(on)}$
- Compared to SiC, strong temperature dependency of $R_{DS(on)}$ of GaN helps the current sharing in parallel operation

GaN E-HEMT $R_{DS(on)}$ vs T_J

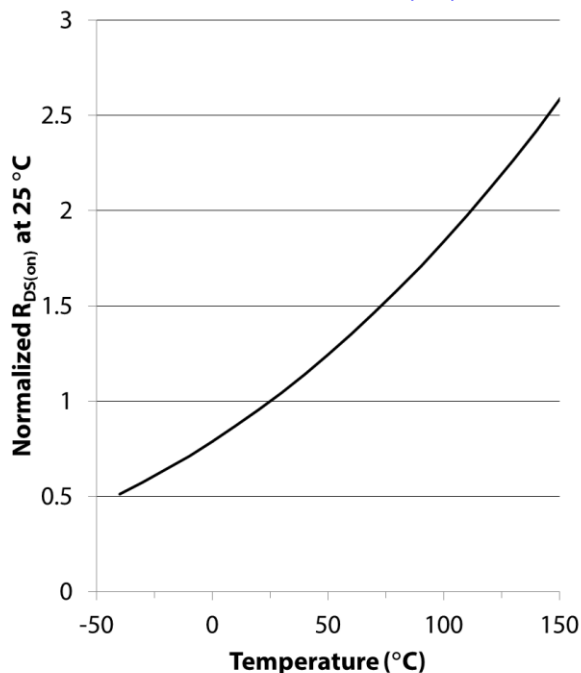

SiC $R_{DS(on)}$ vs T_J


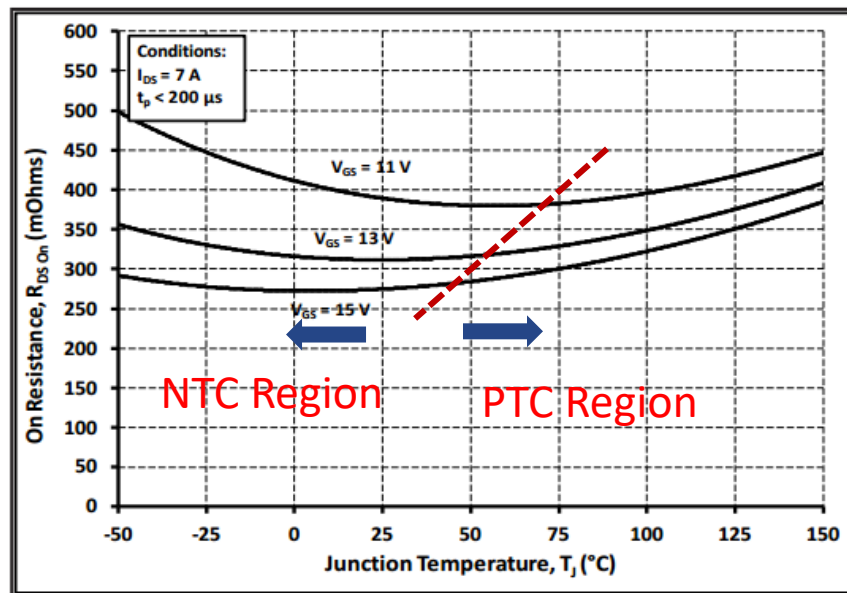



Figure 6. On-Resistance vs. Temperature
For Various Gate Voltage

- GaN E-HEMT has stable gate threshold over the temperature range
- Si/SiC MOSFET $V_{GS(th)}$ decreases with temperature:
 - *Hotter drive turn-on earlier – positive feedback*

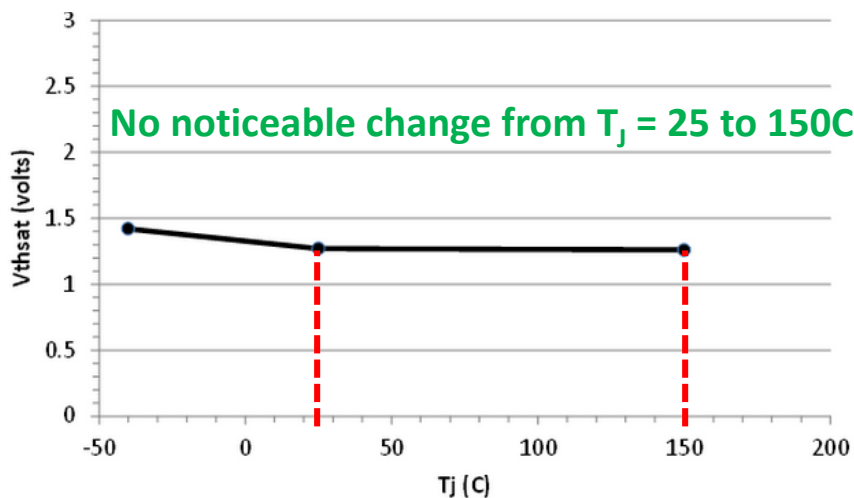GaN E-HEMT $V_{GS(th)}$ is stable over T_J range



SiC $V_{GS(th)}$ decreases with T_J

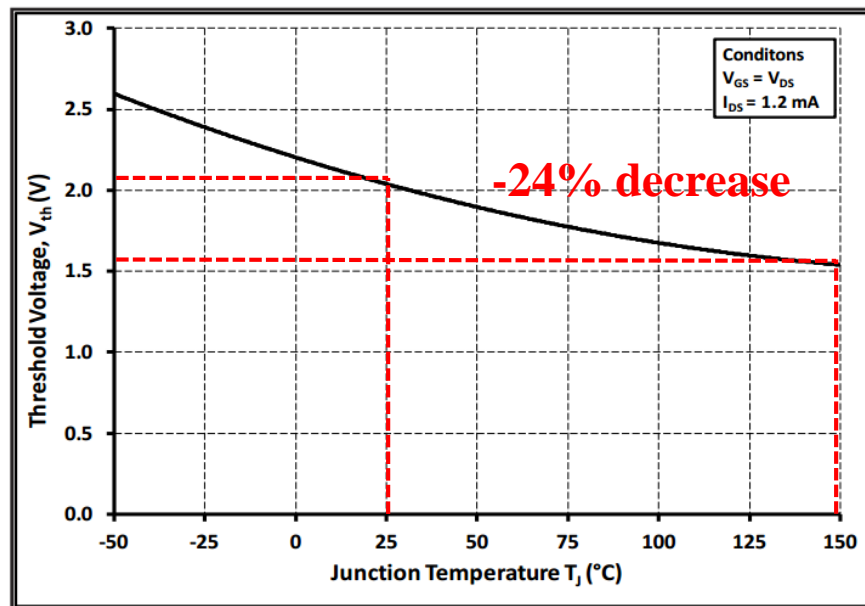

Trans-conductance, g_m vs T_j

- GaN E-HEMT Trans-conductance g_m decreases with temperature, good for paralleling
- This characteristics, together with stable $V_{GS(th)}$, helps with dynamic current sharing and self-balancing

GaN HEMT


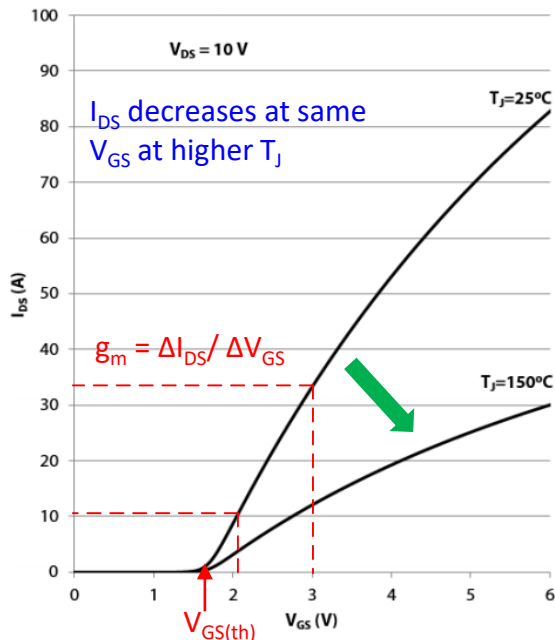


Figure 10 : Typical I_{DS} vs. V_{GS}


SiC MOSFET

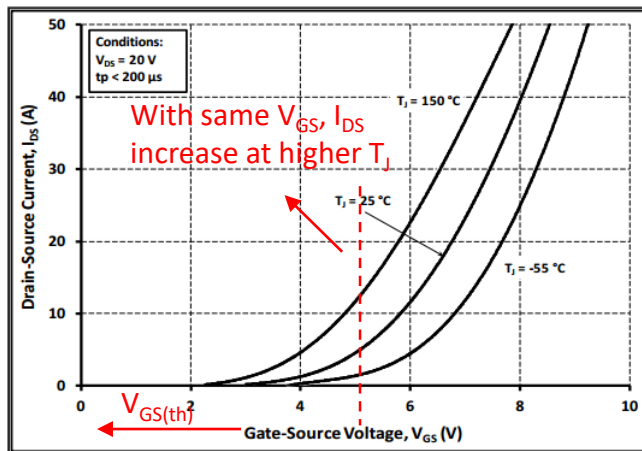

SiC: $V_{GS(th)}$ drops and g_m slightly increases:

- Hotter device tends to have higher switching current -> higher switching loss
- Positive feedback, potential thermal runaway if not designed properly

SJ MOSFET

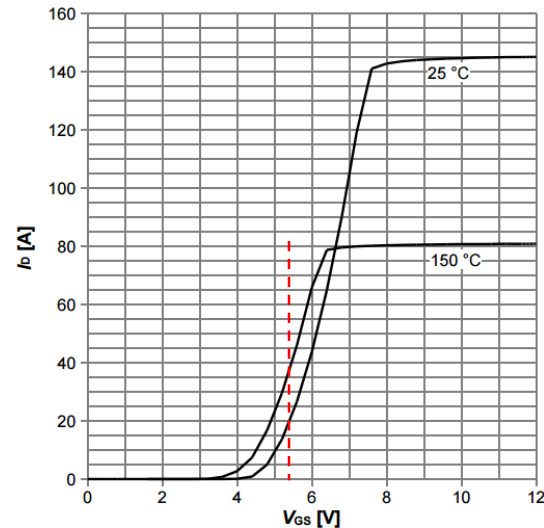


Si: V_{th} decreases and g_m remain constant:

- Slightly positive feedback with T_J

Effect of g_m on switching transient

- Negative feedback for self balancing in parallel:

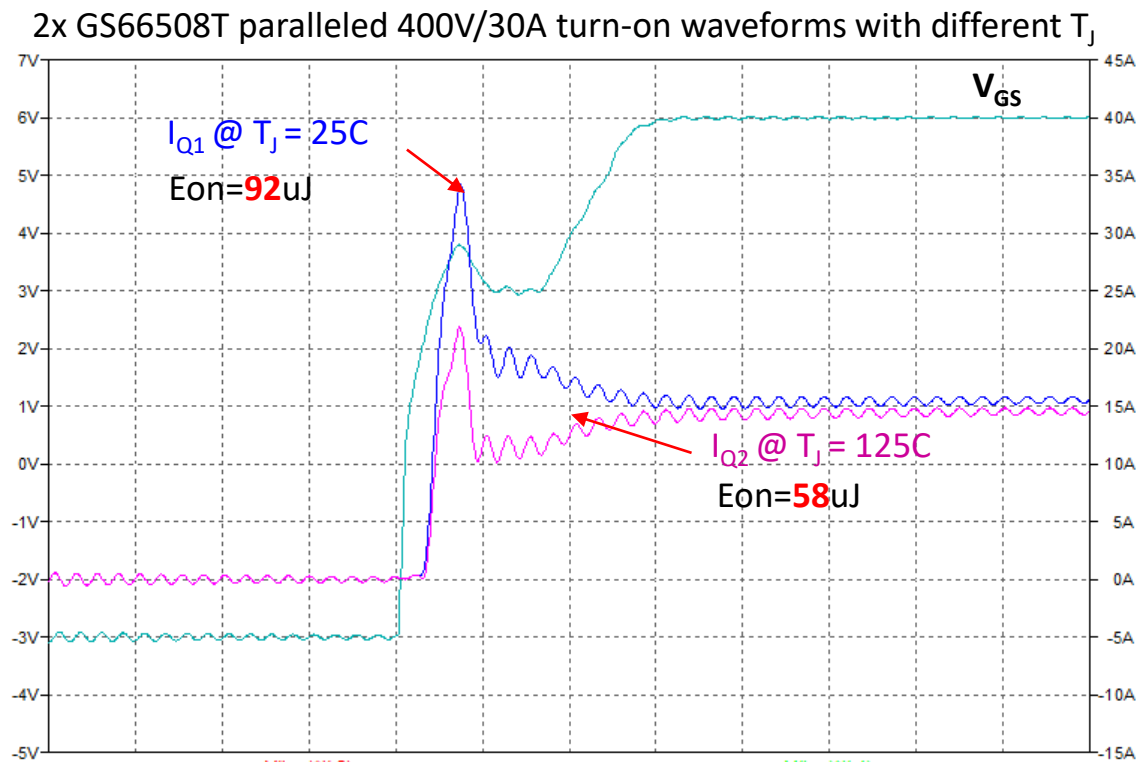
- $T_J \uparrow - g_m \downarrow - I_{D@switching} \downarrow - E_{on} \downarrow - T_J \downarrow$




GaNPX™ Package improves the paralleling performance and stability

- Traditional package has high source inductance that impacts paralleling performance
- GaNPX has ultra low Ls compared to traditional package
- Top-cooled T package features symmetric dual gate pads for easier layout


GaNPX T Package
GS66516T (650V/25mΩ)

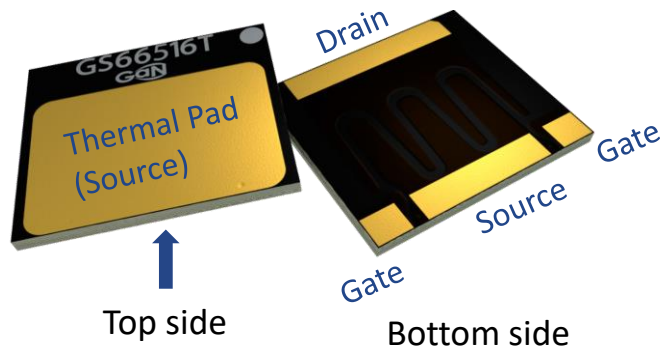

Ansys Q3D 3D modeling of GS66516T

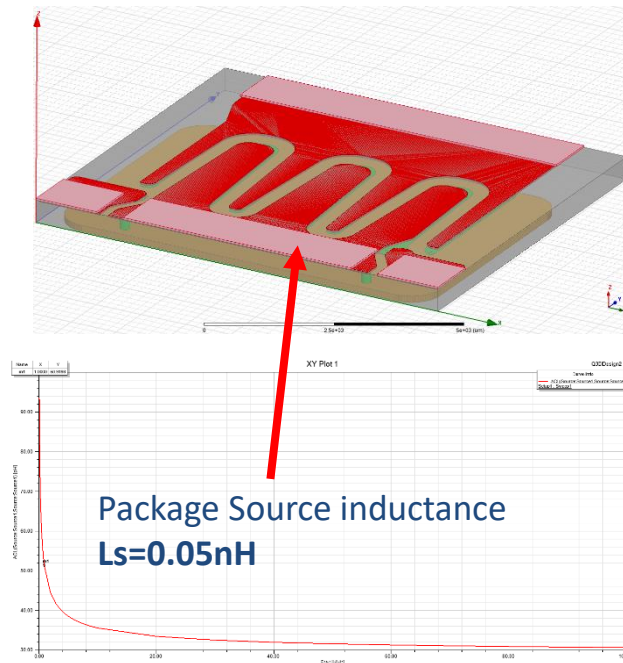


TO-247 Package inductance

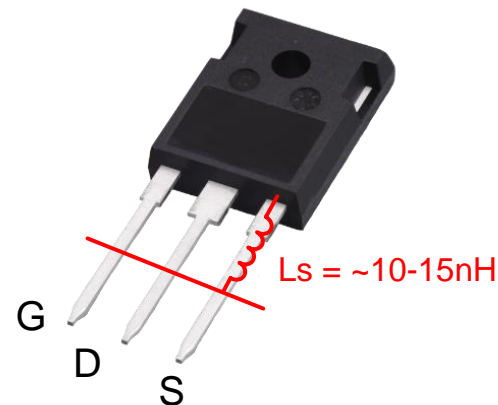


- Dual gate reduces the total gate drive loop in paralleling design
- Easier to make symmetric gate drive layout
- Reduce total layout footprint area

2x TO-247 Parallel layout

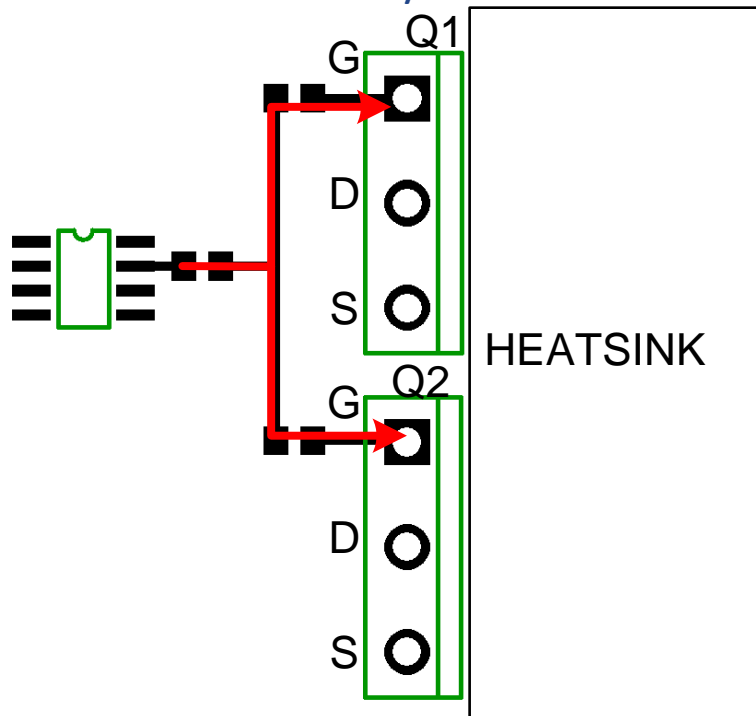

2x GS66516T Parallel layout

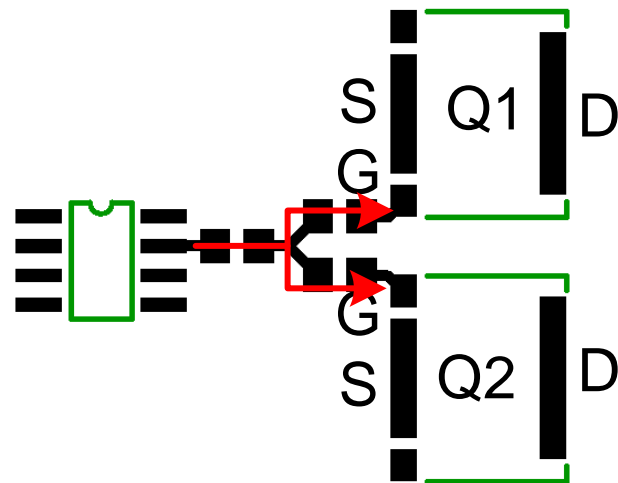

Compared to other technologies:

- GaN Systems E-HEMT characteristic is inherently good fit for paralleling as discussed.
 - The $R_{DS(on)}$ and GaN transfer characteristics provide strong negative feedback to self balance and compensate device and circuit mismatch
- *Circuit layout is most critical to GaN: Ensure successful paralleling and optimum dynamic performance.*
- Therefore, this presentation will focus on gate drive and circuit layout discussion for dynamic performance of paralleling GaN:
 - The impact of circuit parasitics on paralleling was analyzed
 - A half bridge power stage with 4x paralleled GaN 650V/160A HEMTs was designed and validated by experimental test

- ☐ Paralleling design considerations
- ☒ Layout considerations for paralleling GaN
- ☐ Design example of 4x paralleled GaN power stage
- ☐ Experimental results



Unbalanced L_G/L_S increases the gate ringing and risk of oscillation



- L_{CS1-4} : Common source inductance**


- Defined as any inductance that couples power loop switching noise ($L \cdot di/dt$) into the gate drive circuit
- Including the shared/common source inductance and mutual inductance between power and drive loops
- **Feedback switching di/dt to V_{GS} , impact gate drive stability and performance**
- **Minimize as much as possible.**

- ## ISOLATION



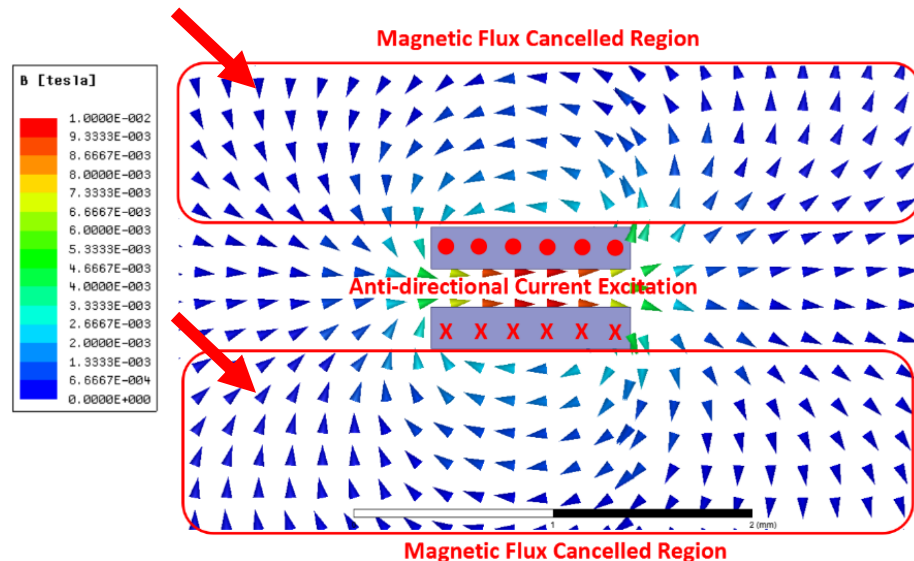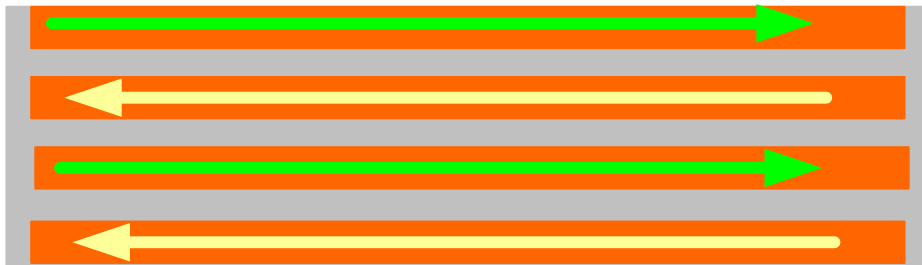- ❑ When two adjacent conductors are located close with opposite current direction, magnetic flux generated by two current flows will cancel each other in the region highlighted.
- ❑ This magnetic flux canceling effect can lower the parasitic inductance.
- Arrange the layout so that high-frequency current flows in opposite direction on two adjacent PCB layers



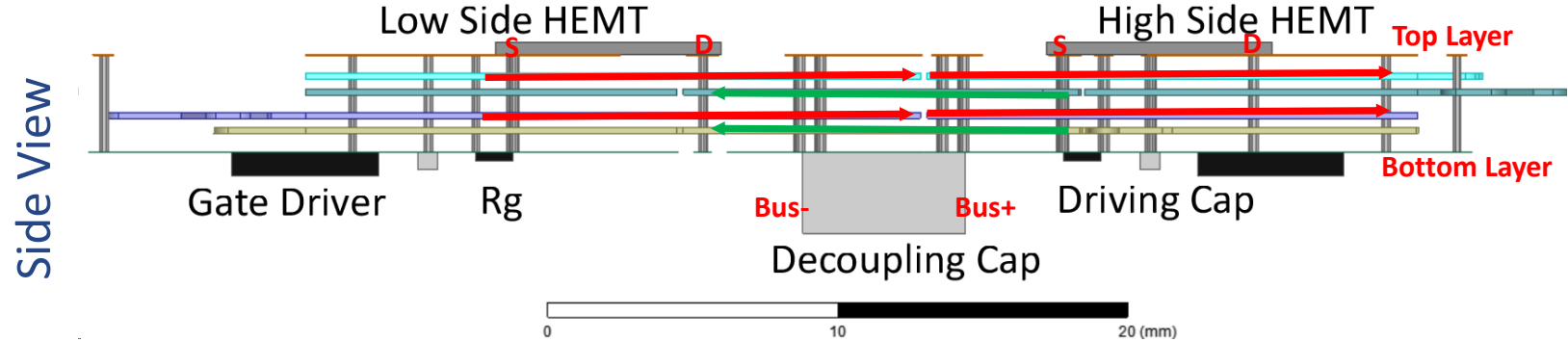

High Frequency Current alternates direction on Each Layer to provide flux canceling effect

Top Layer: place GaN HEMTs


Mid_L1: BUS+ -> Drain_High ; Source_Low -> BUS-


Mid_L2: Source_High -> Drain_Low

Mid_L3: BUS+ -> Drain_High ; Source_Low -> BUS-

Mid_L4: Source_High -> Drain_Low

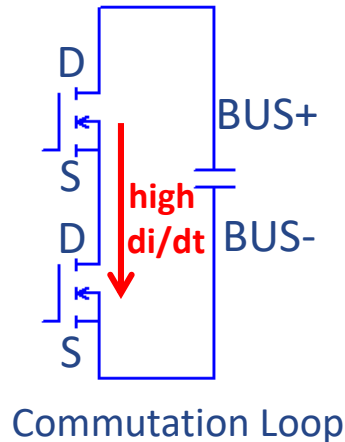
Bottom Layer: place Gate Driver Circuit and Decoupling Caps



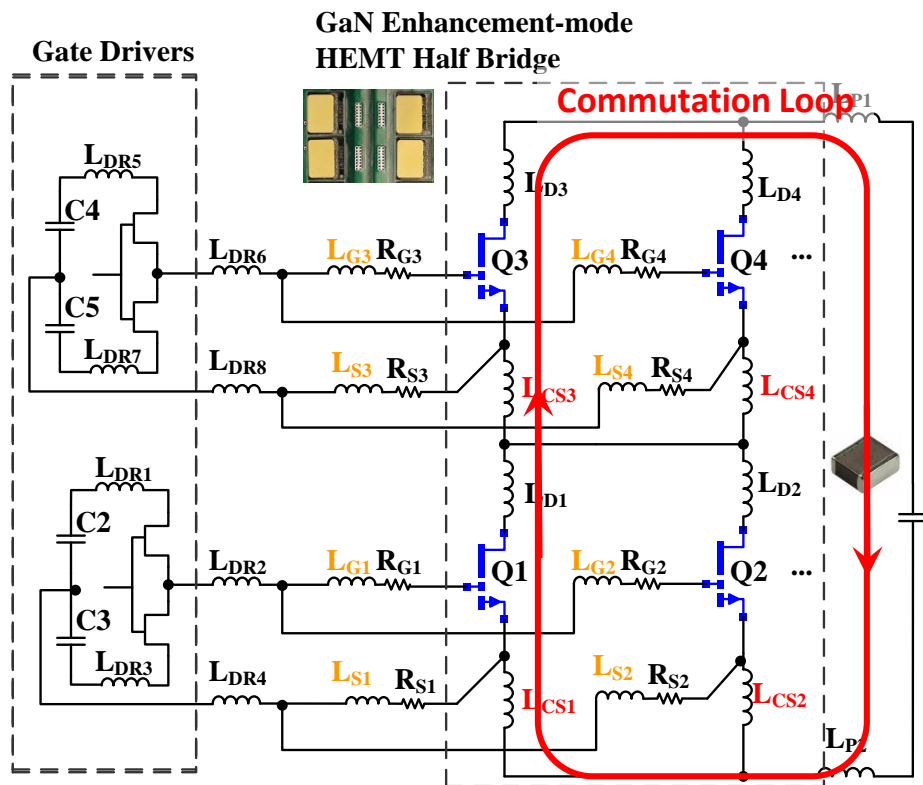

GaN Systems Solution: only 25% L_{Loop} of the Best Counterparts:

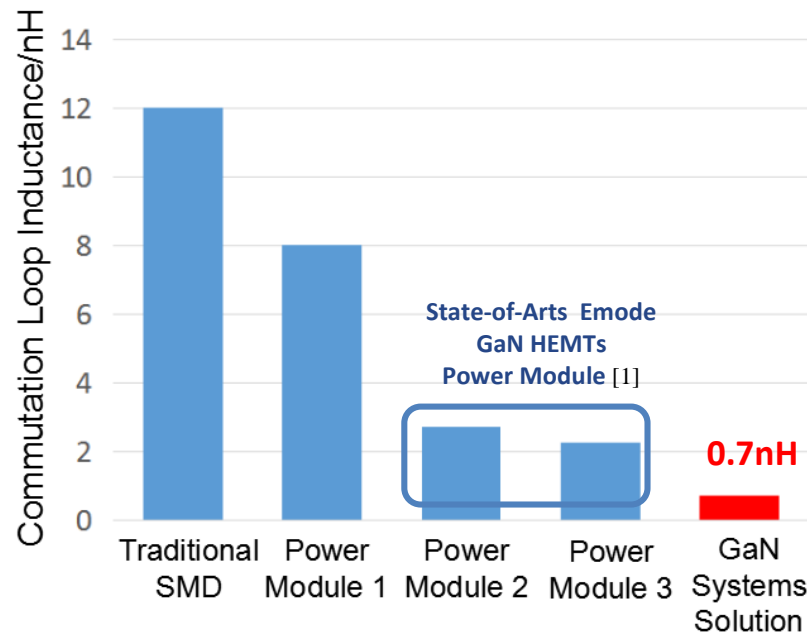- Low inductance GaN_{px} Packaging
- Flux cancelling PCB design





[1] F.Luo, Z.Chen, L.Xue, P.Mattavelli, D.Boroyevich, B.Hughes, "Design Considerations for GaN HEMT Multichip Half- bridge Module for High-Frequency Power Converters"

- ❑ Paralleling design considerations
- ❑ Layout considerations for paralleling GaN
- ❑ Design example of 4x paralleled GaN power stage
- ❑ Experimental results


4x GS66516T Paralleling Test Board – Top View

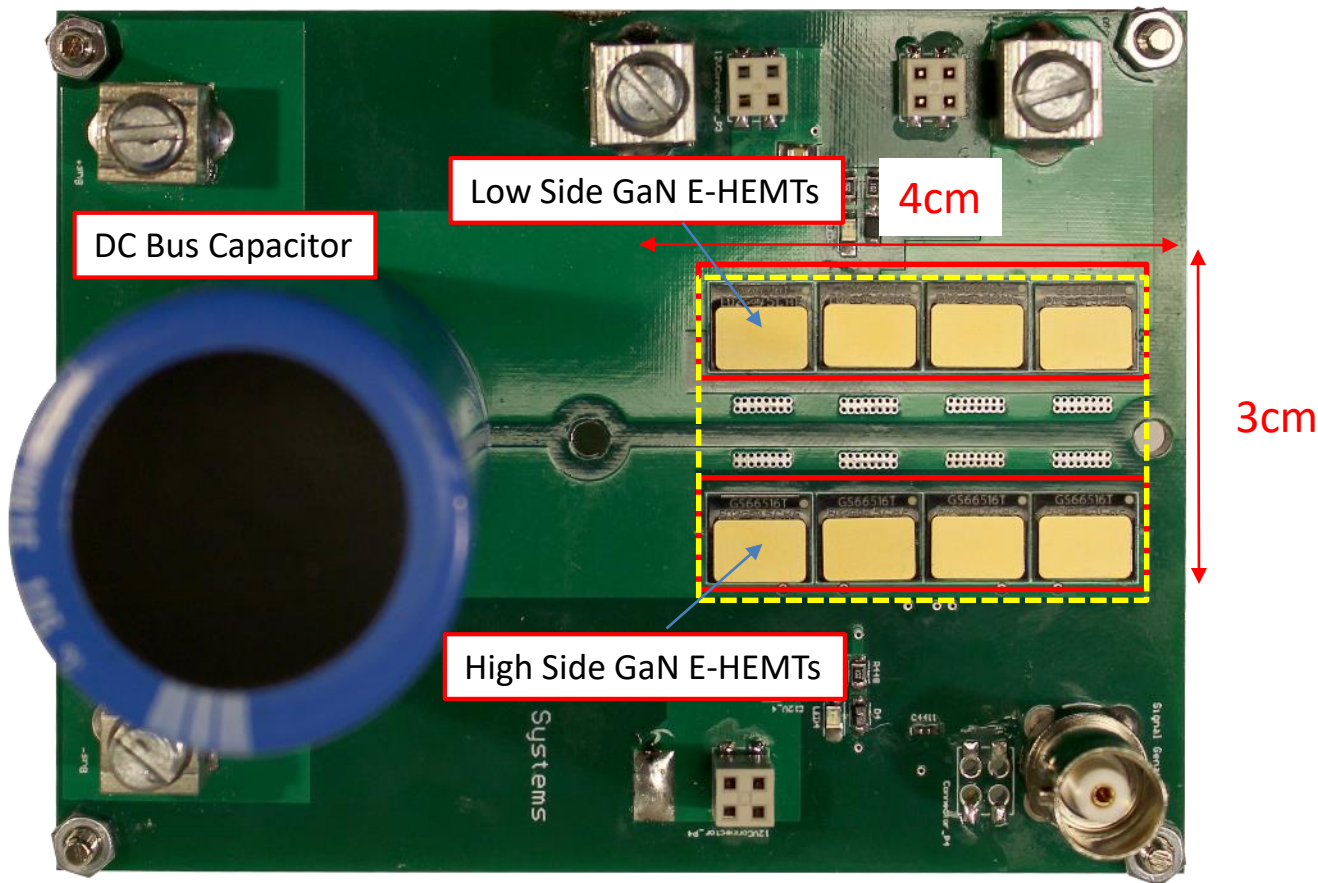650V/240A high Power stage design using discrete GaN EHEMTs




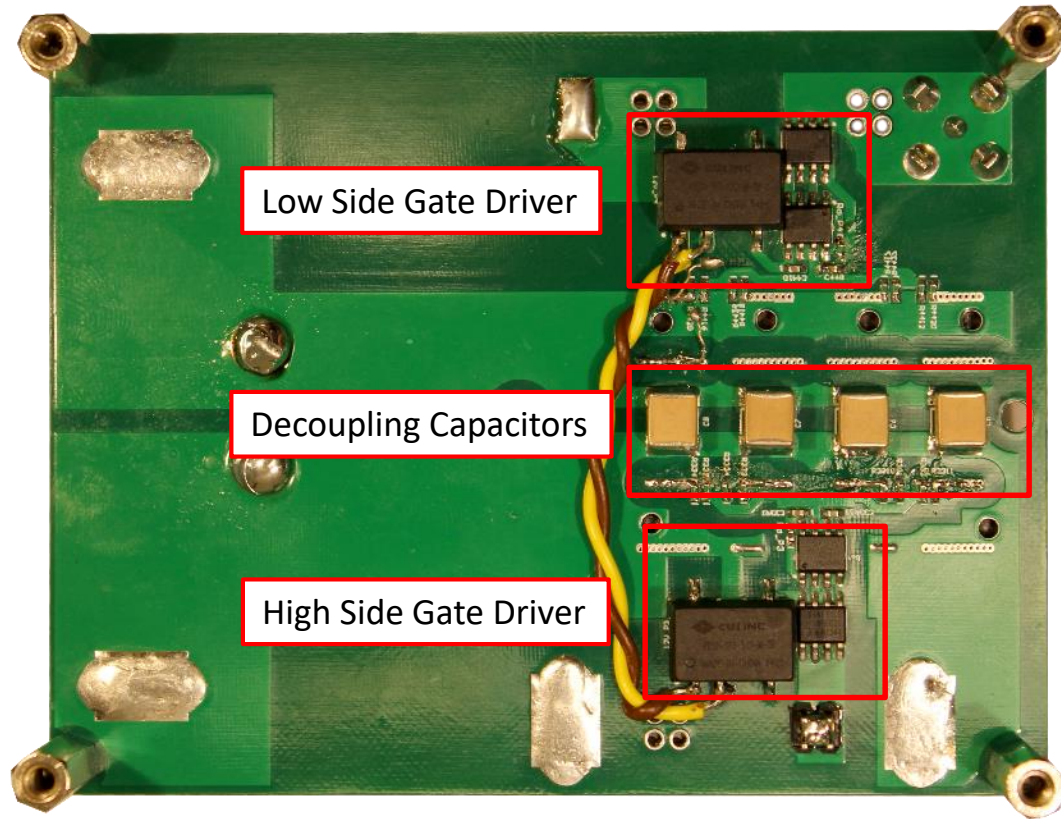


Layout of 4x paralleled GaN power stage

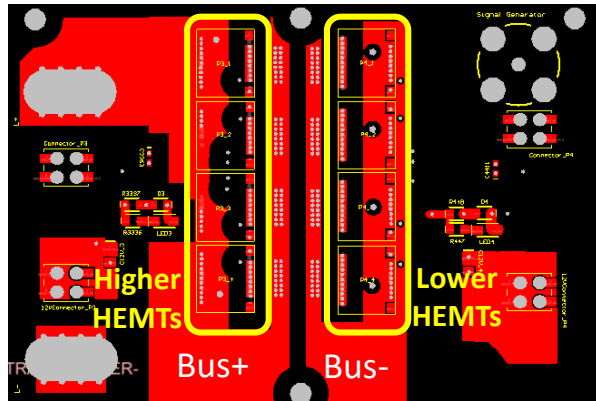


Top Layer

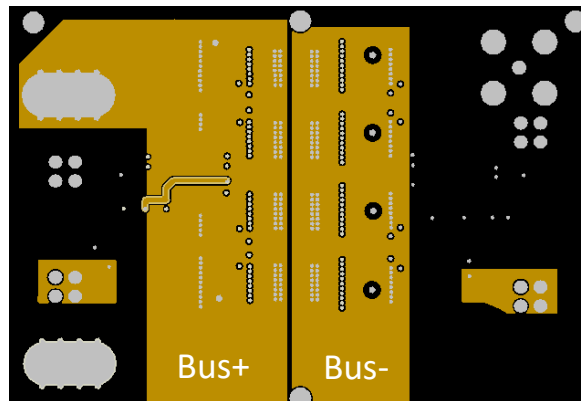


Mid_L1

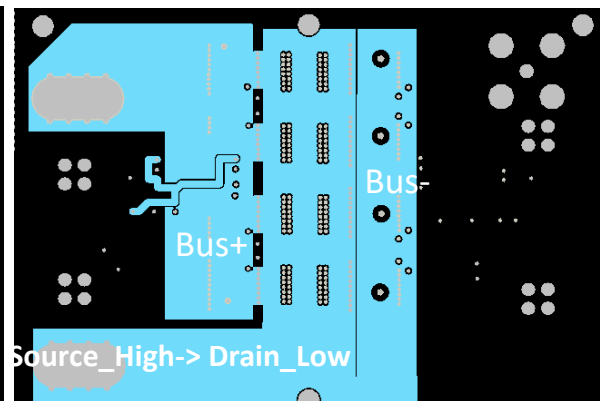


Mid_L2

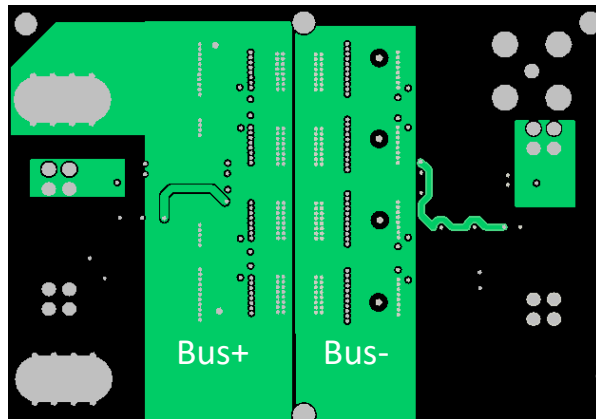

Mid_L3

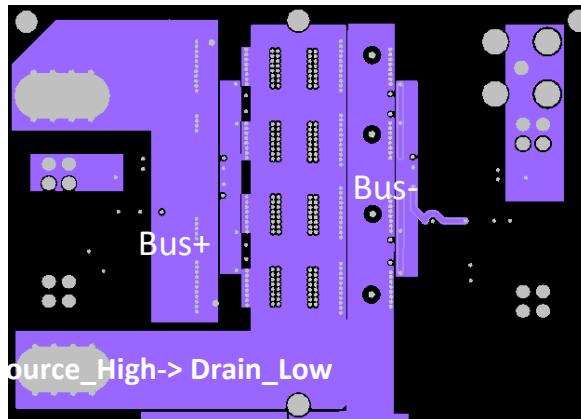

Mid_L4


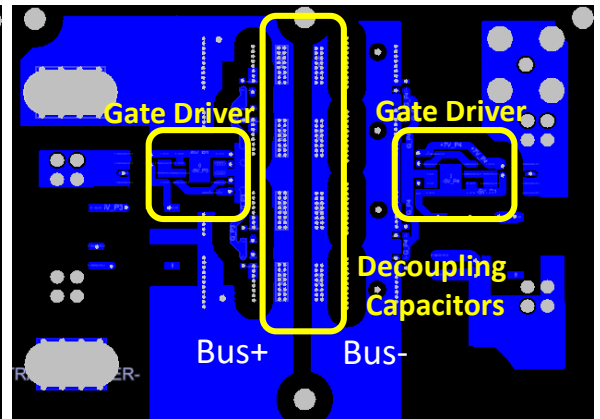


Bottom Layer

Optimum Paralleling Layout for GaN HEMT (4x GS66516T)

Top side with 4x GS66516T in half bridge

Bot side with gate driver

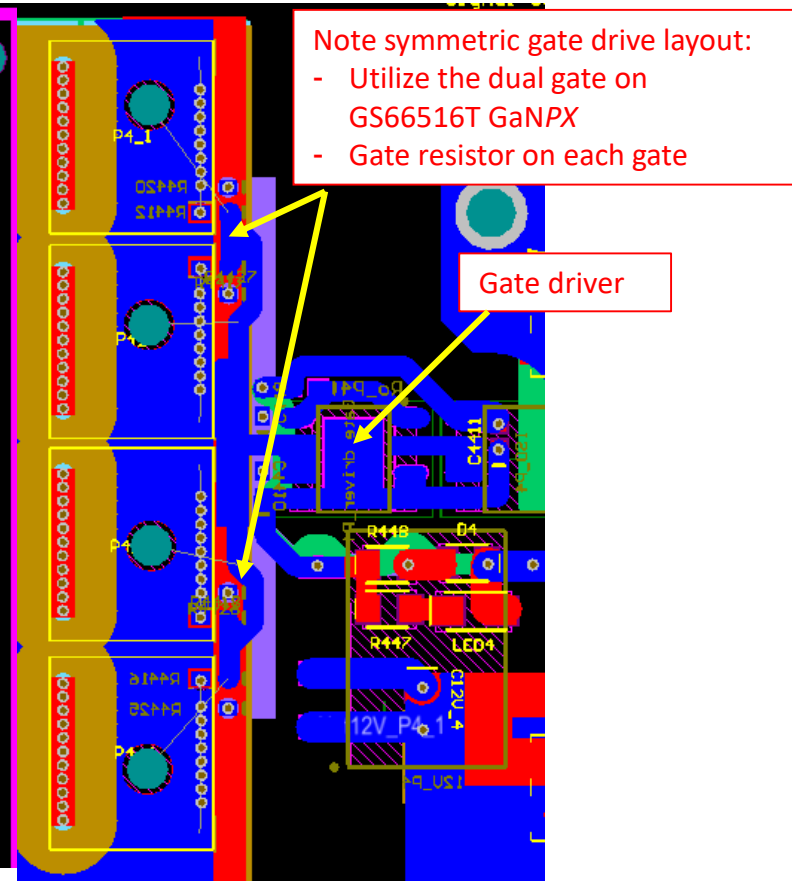
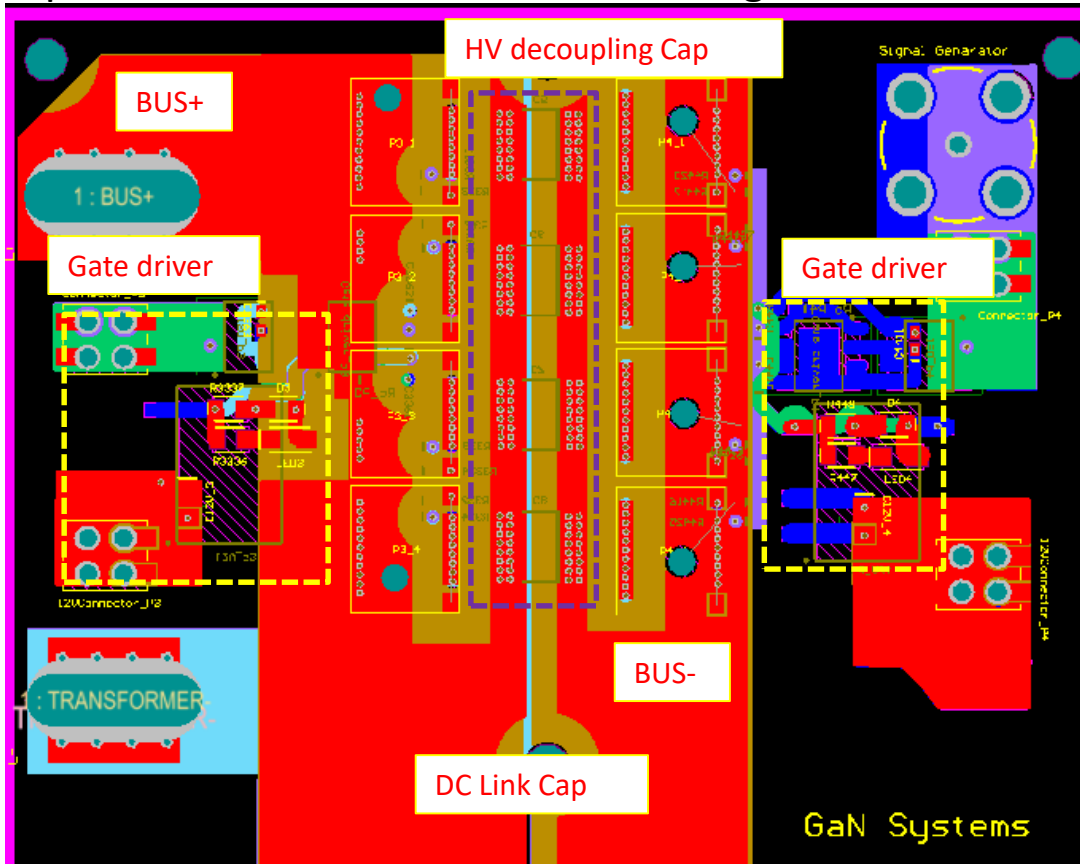


- ❑ Paralleling design considerations
- ❑ Layout considerations for paralleling GaN
- ❑ Design example of 4x paralleled GaN power stage
- ❑ Experimental results

400V/240A double pulse hard Switching test waveforms

DUT: 4x GS66516T in parallel; Freewheeling: 4x GS66516T in parallel

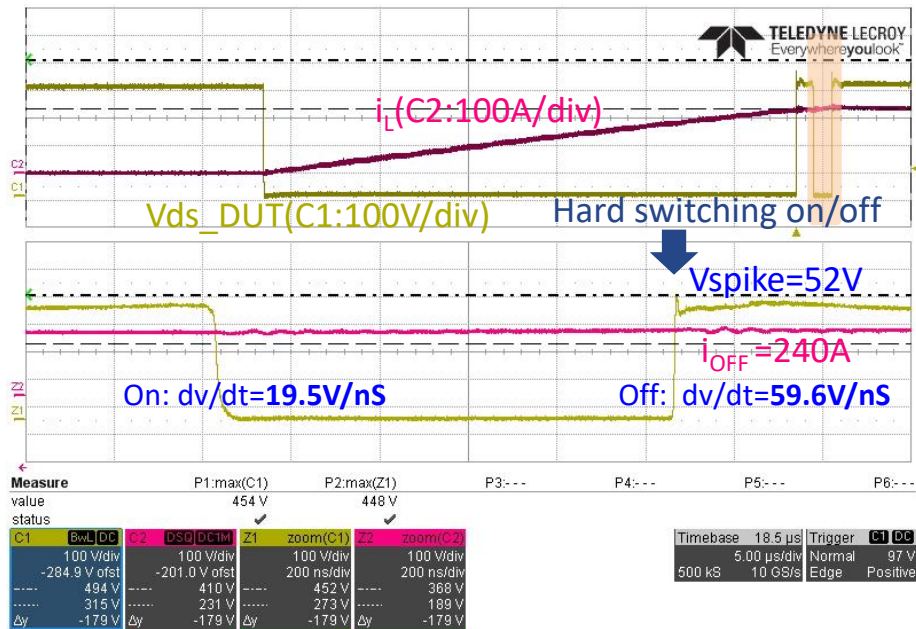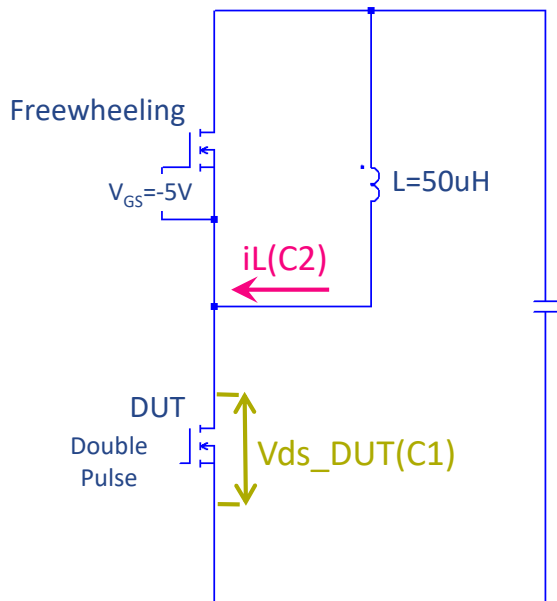Condition: $V_{BUS}=400V$, $I_{DS_ON}=231A$, $I_{DS_OFF}=240A$, $V_{GS}=+6.8V/-5V$, $R_{G_ON}=4.55\Omega$, $R_{G_OFF}=1.25\Omega$.



Measurement Setup: Lecroy WaveSurfer 10M Oscilloscope, HVD3106 Differential Probe (C1), CWT-3LFB mini Rogowski Coil (C2)

Experimental Waveform

- No-Derating Paralleling of GaN HEMTs. Hard switched up to full rated current with clean waveform.**
- 400V/240A Hard Switching Capability with $\sim 200V$ V_{DS} Margin**

- Paralleling discrete GaN is desired to achieve higher power output
- GaN Systems E-HEMT device characteristics are inherently fit for paralleling:
 - Positive $R_{DS(ON)}$ temperature coefficient
 - Stable gate threshold over the temperature range
 - Negative tempco of g_m
 - Low inductance GaNpX package for minimum circuit mismatch
- Layout is critical for paralleling high speed GaN HEMT:
 - Low and balanced parasitic inductance on the power and gate drive loop. Equal length of gate drive layout and optimum gate driver circuit
- Summary
 - Provided practical design guide on how to parallel high speed GaN HEMT devices
 - Showed a design layout example of 4x paralleled GaN E-HEMT half bridge power stage
 - Hardware was built and GaN E-HEMT paralleled operation has been validated up to the rated current under hard switching test (400V/240A)