



# Design considerations of Paralleled GaN HEMT-based Half Bridge Power Stage

*Last update: May 18, 2018*


- ❑ Paralleling design considerations
- ❑ Layout considerations for paralleling GaN
- ❑ Design example of 4x paralleled GaN power stage
- ❑ Experimental results

What are key considerations when paralleling power switches:

Design parameters	Effect on paralleling	Desired
$R_{DS(on)}$	Affect static current sharing.	Positive temperature co-efficient for self-balancing
Gate threshold, $V_{GS(th)}$	Impact dynamic current sharing during turn-on and off. Lower $V_{th}$ results in earlier turn-on and higher switching current/loss which creates positive feedback	Tight distribution, temperature independent or positive temperature co-efficient
Trans-conductance, $g_m$	Impact dynamic current sharing during turn-on and off.	Tight distribution, temperature independent or negative temperature co-efficient
Circuit design and layout	Balanced circuit layout are important for dynamic current sharing and stability of the paralleling operation. <b>This is particularly critical for high speed power switches such as GaN/SiC</b>	Minimize and equalize all layout parasitics to reduce circuit mismatch
Thermal	Affect the device temperature difference. $T_j$ variation may cause dynamic or static current sharing issues depending on device characteristics.	All paralleled devices should have similar thermal resistance and installed on same heatsink for good thermal balance.

- GaN E-HEMT has positive temperature co-efficient  $R_{DS(on)}$
- Compared to SiC, strong temperature dependency of  $R_{DS(on)}$  of GaN helps the current sharing in parallel operation

### GaN E-HEMT $R_{DS(on)}$ vs $T_J$

 

### SiC $R_{DS(on)}$ vs $T_J$


 


Figure 6. On-Resistance vs. Temperature For Various Gate Voltage

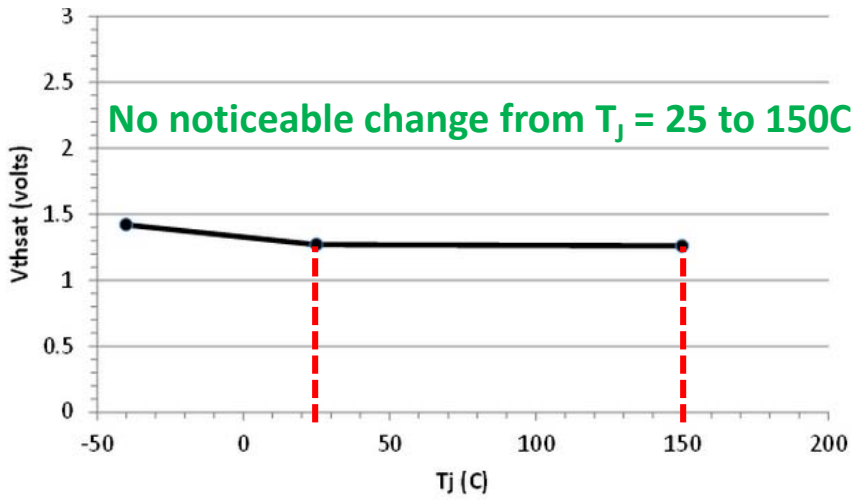
# $V_{GS(th)}$ vs $T_J$

- GaN E-HEMT has stable gate threshold over the temperature range
- Si/SiC MOSFET  $V_{GS(th)}$  decreases with temperature:
  - *Hotter drive turn-on earlier – positive feedback*

GaN E-HEMT  $V_{GS(th)}$  is stable over  $T_J$  range



SiC  $V_{GS(th)}$  decreases with  $T_J$

 

# Trans-conductance, $g_m$ vs $T_j$

- GaN E-HEMT Trans-conductance  $g_m$  decreases with temperature, good for paralleling
- This characteristics, together with stable  $V_{GS(th)}$ , helps with dynamic current sharing and self-balancing

## GaN HEMT


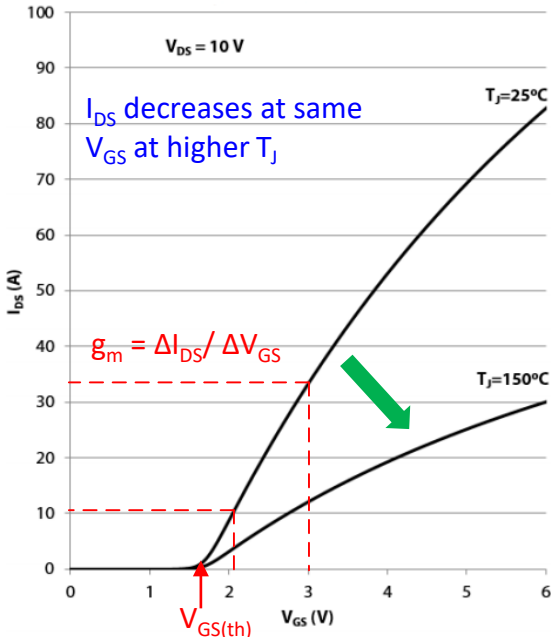


Figure 10 : Typical  $I_{DS}$  vs.  $V_{GS}$


## SiC MOSFET

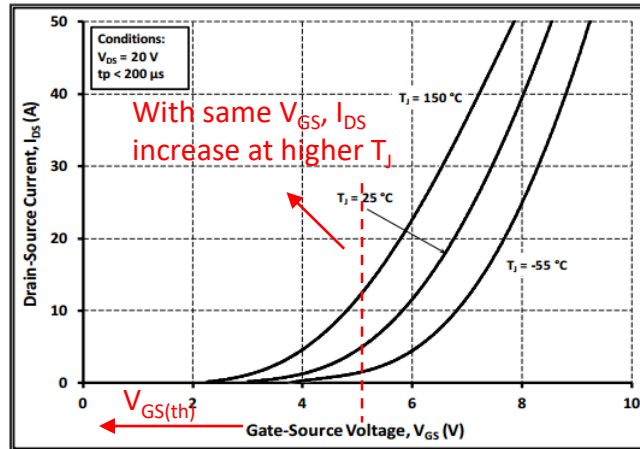

**SiC:**  $V_{GS(th)}$  drops and  $g_m$  slightly increases:

- Hotter device tends to have higher switching current -> higher switching loss
- Positive feedback, potential thermal runaway if not designed properly

## SJ MOSFET

 

**Si:**  $V_{th}$  decreases and  $g_m$  remain constant:


- Slightly positive feedback with  $T_j$

# Effect of $g_m$ on switching transient

- Negative feedback for self balancing in parallel:

- $T_J \uparrow - g_m \downarrow - I_{D@switching} \downarrow - E_{on} \downarrow - T_J \downarrow$

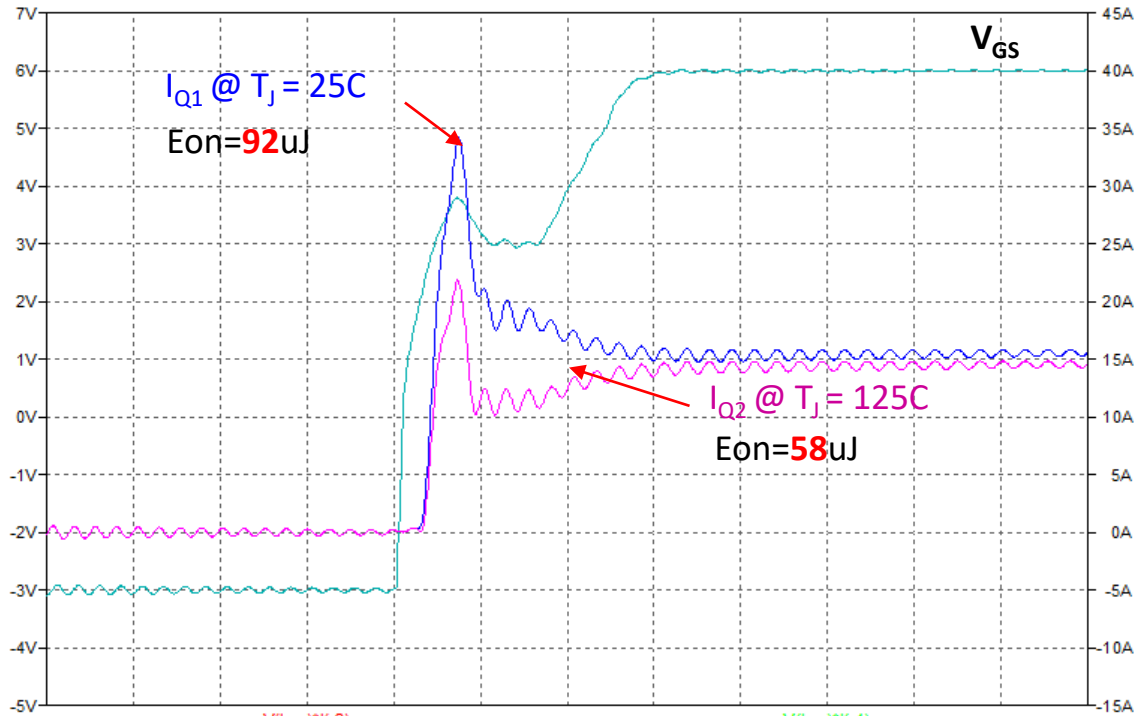2x GS66508T paralleled 400V/30A turn-on waveforms with different  $T_J$




# Circuit layout - Low inductance of GaNPX<sup>®</sup> package


GaNPX<sup>®</sup> package improves the paralleling performance and stability

- Traditional package has high source inductance that impacts paralleling performance
- GaNPX<sup>®</sup> package has ultra low Ls compared to traditional package
- Top-cooled T package features symmetric dual gate pads for easier layout

 
GaNPX<sup>®</sup> T Package  
GS66516T (650V/25mΩ)



Ansys Q3D 3D modeling of GS66516T

 


TO-247 Package inductance

 




- Dual gate reduces the total gate drive loop in paralleling design
- Easier to make symmetric gate drive layout
- Reduce total layout footprint area

2x TO-247 Parallel layout

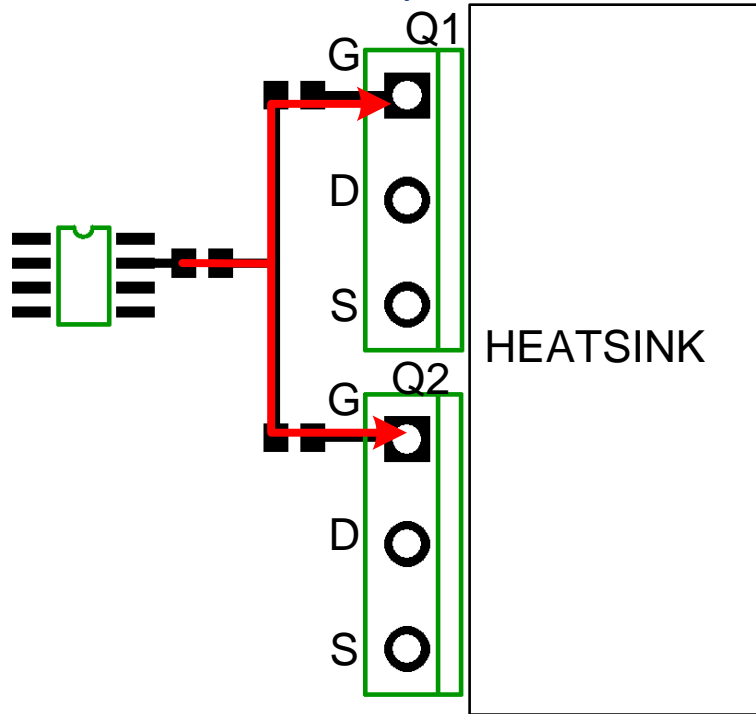

2x GS66516T Parallel layout

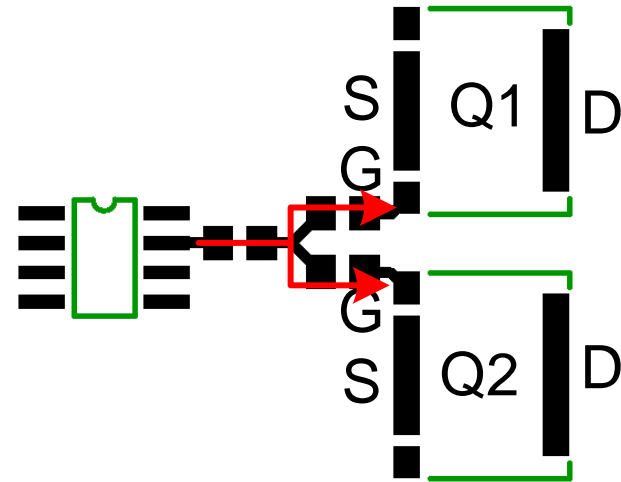


## Compared to other technologies:

- GaN Systems E-HEMT characteristic is inherently good fit for paralleling as discussed.
  - The  $R_{DS(on)}$  and GaN transfer characteristics provide strong negative feedback to self balance and compensate device and circuit mismatch
- ***Circuit layout is most critical to GaN: Ensure successful paralleling and optimum dynamic performance.***
- Therefore, this presentation will focus on gate drive and circuit layout discussion for dynamic performance of paralleling GaN:
  - The impact of circuit parasitics on paralleling was analyzed
  - A half bridge power stage with 4x paralleled GaN 650V/160A HEMTs was designed and validated by experimental test

- Paralleling design considerations
- Layout considerations for paralleling GaN
- Design example of 4x paralleled GaN power stage
- Experimental results

## GaN Enhancement-mode HEMT Half Bridge

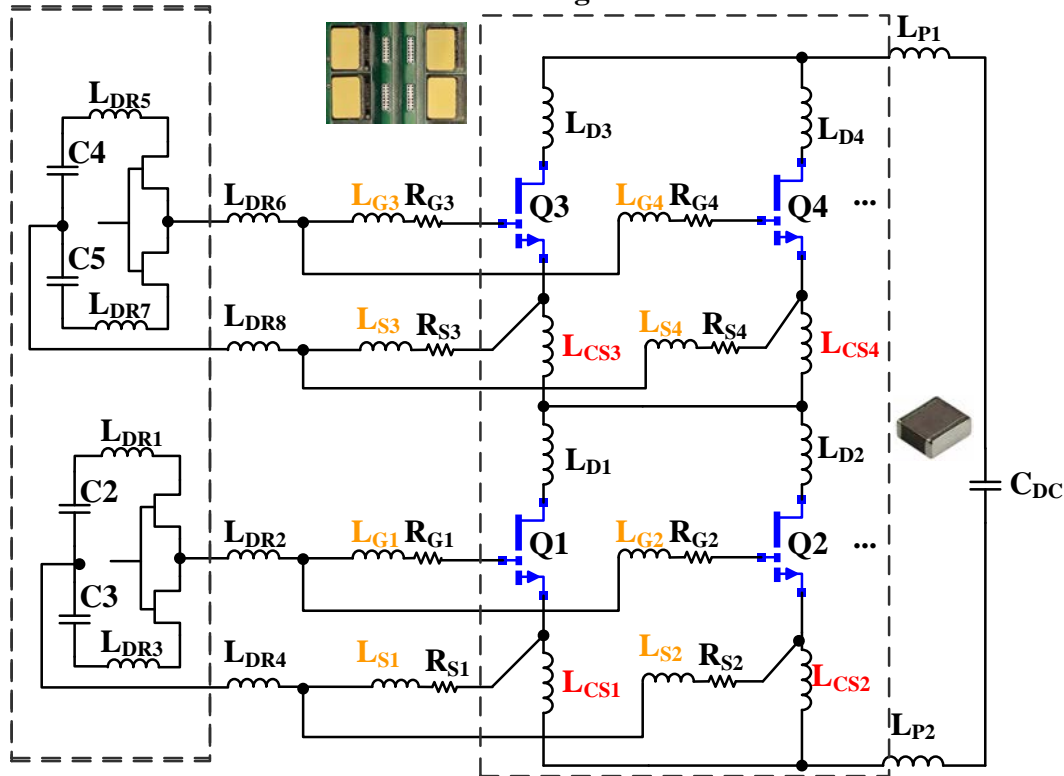

## Critical parasitic parameters that have high impact on GaN paralleling:

### $L_{G1-4}$ & $L_{S1-4}$ : gate/source inductance


Unbalanced  $L_G/L_S$  increases the gate ringing and risk of oscillation

- Equalize  $L_G/L_S$  using star connection and keep as low as possible
- **Individual  $R_G/R_S$  is recommended to reduce gate ringing among paralleled devices**


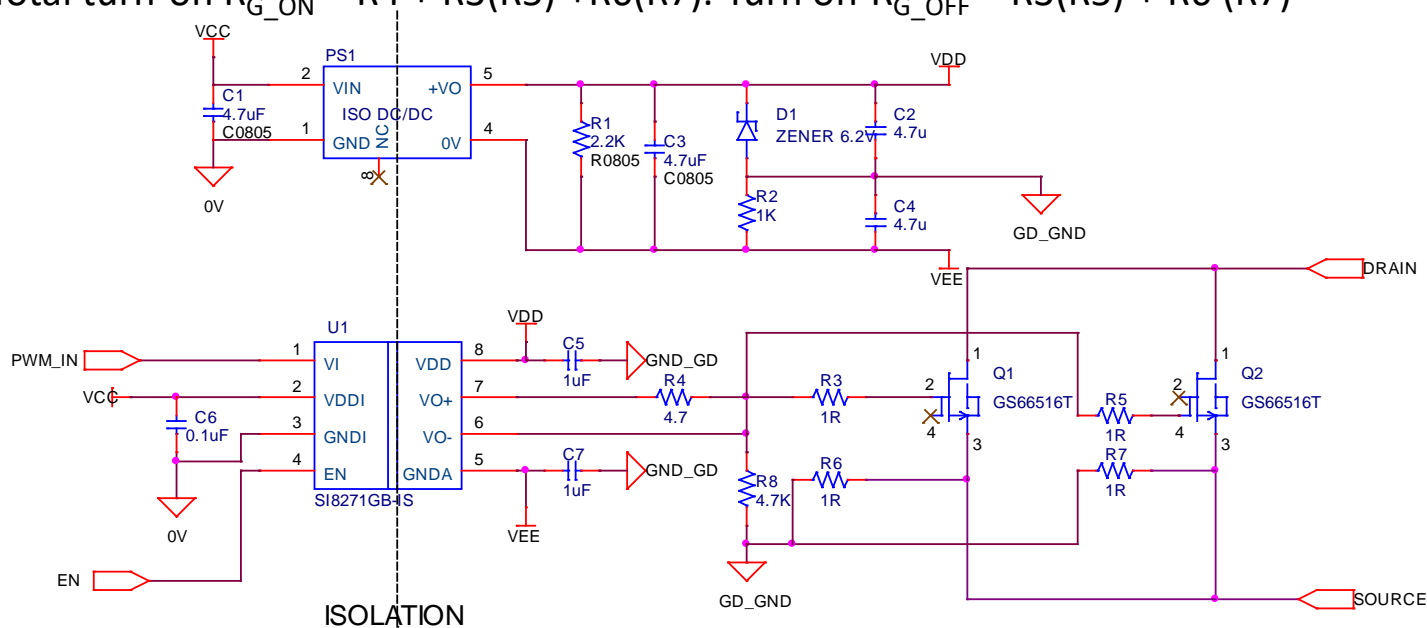
### $L_{CS1-4}$ : Common source inductance


- Defined as any inductance that couples power loop switching noise ( $L \cdot di/dt$ ) into the gate drive circuit
- Including the shared/common source inductance and mutual inductance between power and drive loops
- **Feedback switching  $di/dt$  to  $V_{GS}$ , impact gate drive stability and performance**
- **Minimize as much as possible.**

- For high current paralleling design, a small negative gate drive turn-off bias is recommended for lower turn-off loss and more robust gate drive. Recommend to use -3V to -5V with synchronous driving for optimum efficiency.
- Create bipolar gate drive from single power supply using a 6.2V Zener. Negative gate drive bias (VEE) is defined by PS1 output – Vzener(6V)
- Use small values (1-2Ω) for distributed gate and source resistance: R3/R5 and R6/R7
- Total turn-on  $R_{G\_ON} = R4 + R3(R5) + R6(R7)$ . Turn off  $R_{G\_OFF} = R3(R5) + R6(R7)$



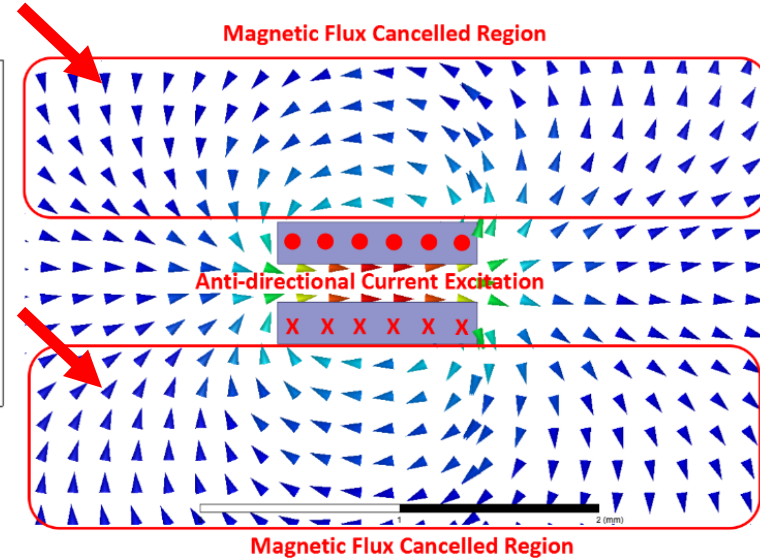 - When two adjacent conductors are located close with opposite current direction, magnetic flux generated by two current flows will cancel each other in the region highlighted.
- This magnetic flux canceling effect can lower the parasitic inductance.
- Arrange the layout so that high-frequency current flows in opposite direction on two adjacent PCB layers



 

**High Frequency Current alternates direction on Each Layer to provide flux canceling effect**

Top Layer: place GaN HEMTs


Mid\_L1: BUS+  $\rightarrow$  Drain\_High ; Source\_Low  $\rightarrow$  BUS-


Mid\_L2: Source\_High  $\rightarrow$  Drain\_Low

Mid\_L3: BUS+  $\rightarrow$  Drain\_High ; Source\_Low  $\rightarrow$  BUS-

Mid\_L4: Source\_High  $\rightarrow$  Drain\_Low

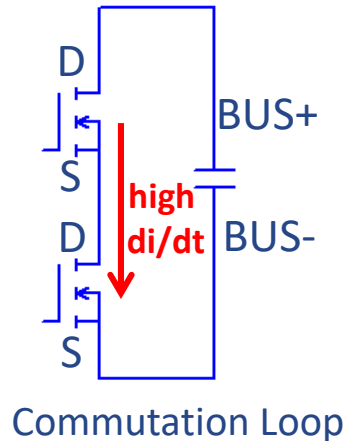
Bottom Layer: place Gate Driver Circuit and Decoupling Caps



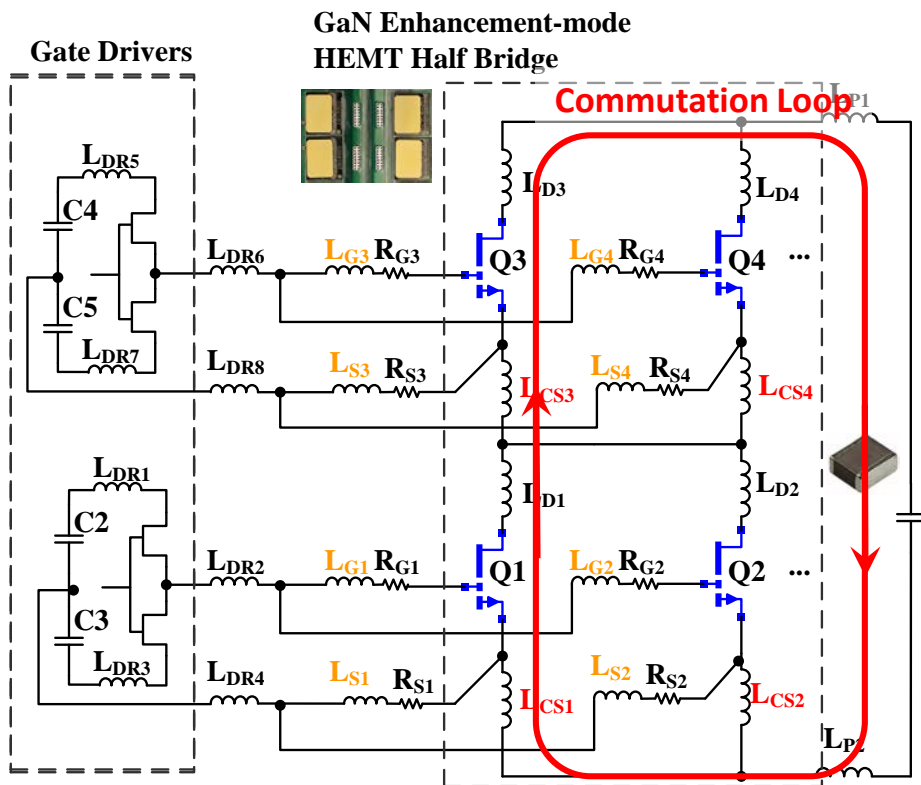

GaN Systems Solution: only 25%  $L_{Loop}$  of the Best Counterparts:

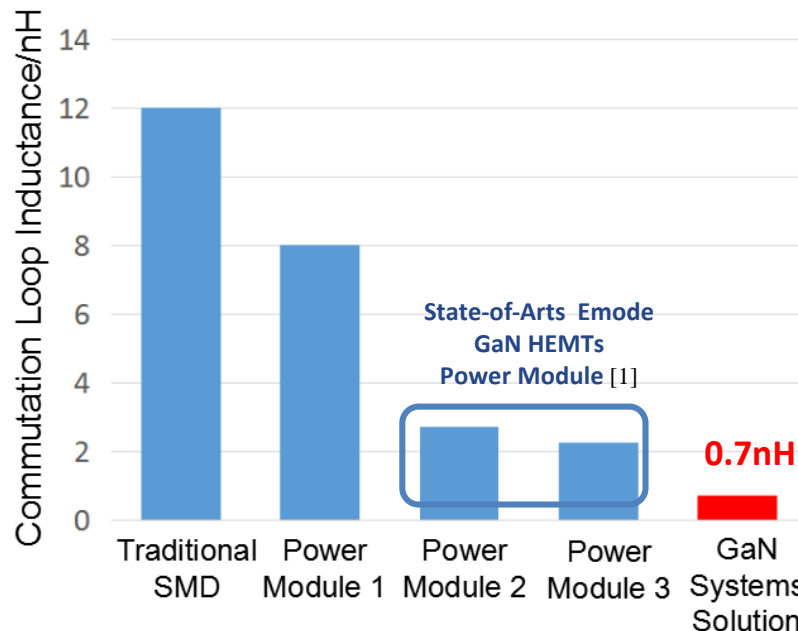- Low inductance GaN<sub>PIX</sub>® package
- Flux cancelling PCB design




[1] F.Luo, Z.Chen, L.Xue, P.Mattavelli, D.Boroyevich, B.Hughes, "Design Considerations for GaN HEMT Multichip Half- bridge Module for High-Frequency Power Converters"




- Paralleling design considerations
- Layout considerations for paralleling GaN
- Design example of 4x paralleled GaN power stage
- Experimental results
 
# 4x GS66516T Paralleling Test Board – Top View


650V/240A high Power stage design using discrete GaN EHEMTs



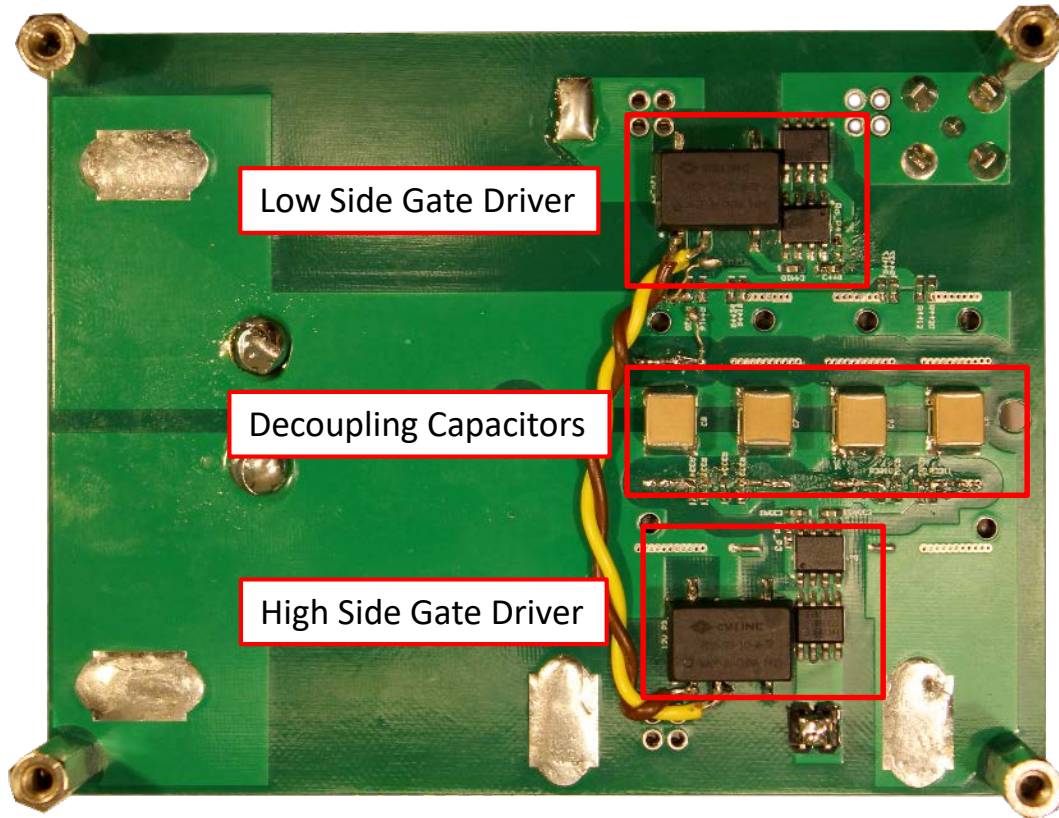

 
# Layout of 4x paralleled GaN power stage


\* Un-plated holes, for thermal measurement. Avoid routing electrical signals under the device.




Top Layer

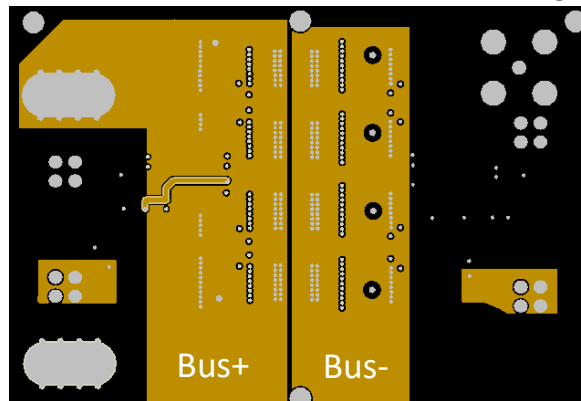


Mid\_L1

 


Mid\_L2

 

Mid\_L3

 

Mid\_L4


 


Bottom Layer

# Optimum Paralleling Layout for GaN HEMT (4x GS66516T)

Top side with 4x GS66516T in half bridge

Bot side with gate driver

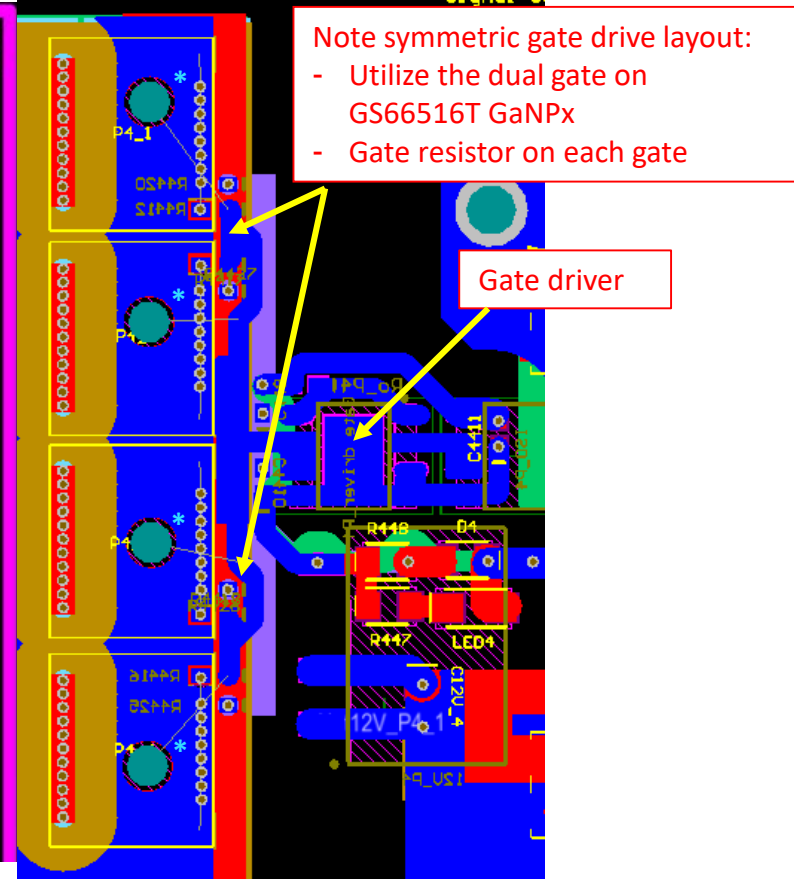
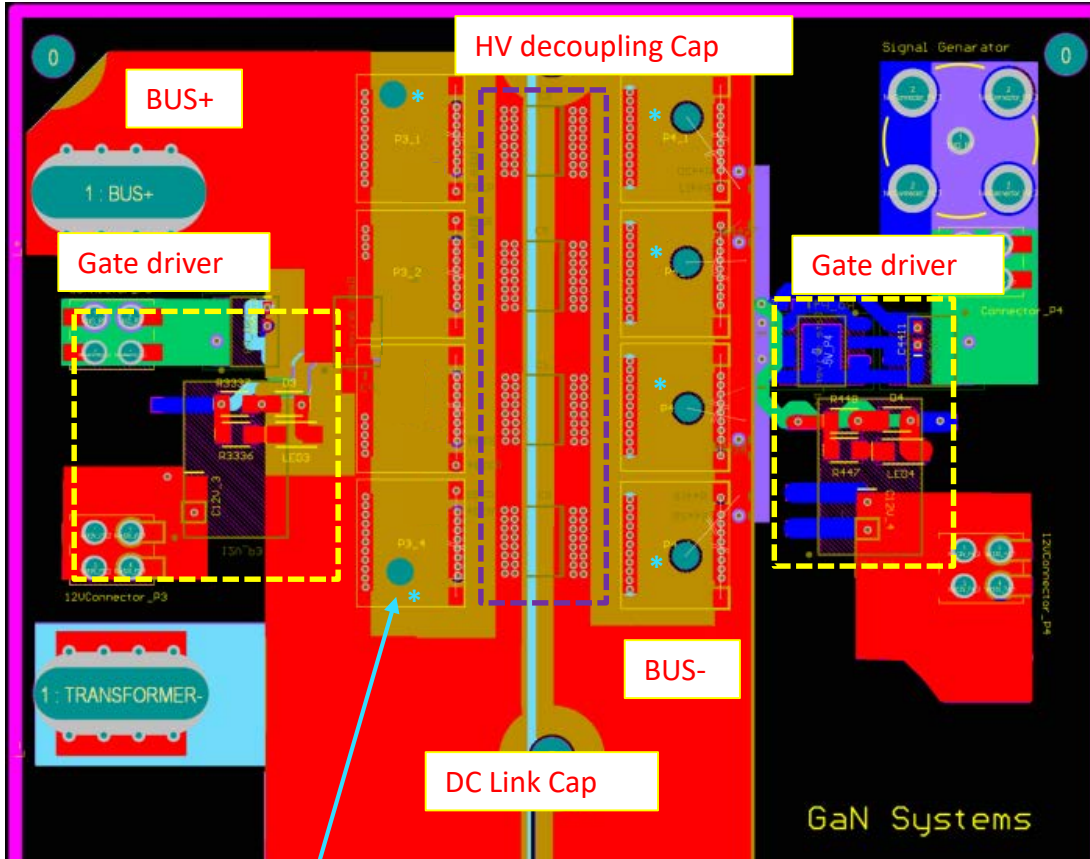


\* Un-plated holes, for thermal measurement. Avoid routing electrical signals under the device.

- ❑ Paralleling design considerations
- ❑ Layout considerations for paralleling GaN
- ❑ Design example of 4x paralleled GaN power stage
- ❑ Experimental results
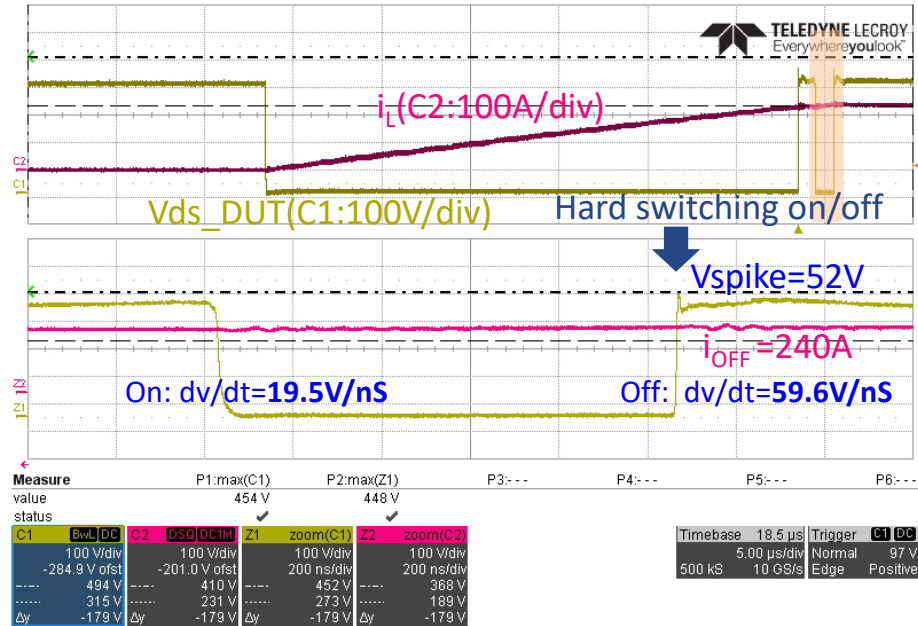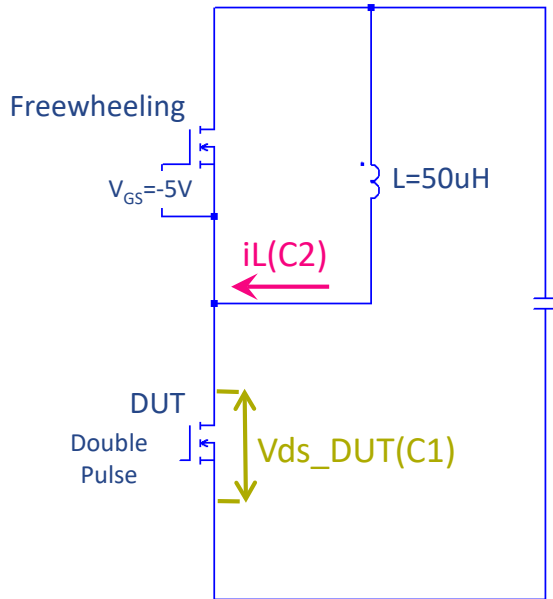
# 400V/240A double pulse hard Switching test waveforms

DUT: 4x GS66516T in parallel;      Freewheeling: 4x GS66516T in parallel  
Condition:  $V_{BUS}=400V$ ,  $I_{DS\_ON}=231A$ ,  $I_{DS\_OFF}=240A$ ,  $V_{GS}=+6.8V/-5V$ ,  $R_{G\_ON}=4.55ohm$ ,  $R_{G\_OFF}=1.25 ohm$ .



Measurement Setup: Lecroy WaveSurfer 10M Oscilloscope, HVD3106 Differential Probe(C1), CWT-3LFB mini Rogowski Coil(C2)

## Experimental Waveform

- **No-Derating Paralleling of GaN HEMTs. Hard switched up to full rated current with clean waveform.**
- **400V/240A Hard Switching Capability with  $\sim 200V$   $V_{DS}$  Margin**

- Paralleling discrete GaN is desired to achieve higher power output
- GaN Systems E-HEMT device characteristics are inherently fit for paralleling:
  - Positive  $R_{DS(ON)}$  temperature coefficient
  - Stable gate threshold over the temperature range
  - Negative tempco of  $g_m$
  - Low inductance GaN $PX^{\circledR}$  package for minimum circuit mismatch
- Layout is critical for paralleling high speed GaN HEMT:
  - Low and balanced parasitic inductance on the power and gate drive loop. Equal length of gate drive layout and optimum gate driver circuit
- Summary
  - Provided practical design guide on how to parallel high speed GaN HEMT devices
  - Showed a design layout example of 4x paralleled GaN E-HEMT half bridge power stage
  - Hardware was built and GaN E-HEMT paralleled operation has been validated up to the rated current under hard switching test (400V/240A)