



# GN004 Application Note

## Design Considerations of Paralleled GaN HEMTs

GaN Systems Inc.

March 08, 2022



Paralleling of switches is necessary in high power applications such as traction inverters, renewable energy systems etc. This application note provides details on the design considerations of GaN FETs in parallel so that designers can release optimized designs and achieve the best system performance.

The benefits of paralleling GaN are discussed. The characteristics of GaN are analyzed and show that GaN is inherently fit for paralleling.

For higher overall system performance, improvements in the design must take place to reduce the impact of parasitics in paralleling layout applications and this is illustrated in this application.

A design example of 4 x paralleled GaN HEMTs is presented and the test results show that the thermal balance of GaN HEMTs is achieved.

## 1 Paralleling GaN **Benefits**

## 2 Essential GaN Characteristics – **Good for Paralleling**

Essential GaN Characteristics

Conduction Loss Distribution:  $R_{DS(on)}$  vs  $T_J$

Switching Loss Distribution:  $V_{GS(th)}$  vs  $T_J$

Switching Loss Distribution:  $g_m$  vs  $T_J$

## 3 Layout & **Design Considerations** of Paralleled GaN

## 4 Real Example of **Paralleling 4 x GaN FETs**

## 5 Summary

## 1 Paralleling GaN **Benefits**

## 2 Essential GaN Characteristics – **Good for Paralleling**

Essential GaN Characteristics

Conduction Loss Distribution:  $R_{DS(on)}$  vs  $T_J$

Switching Loss Distribution:  $V_{GS(th)}$  vs  $T_J$

Switching Loss Distribution:  $g_m$  vs  $T_J$

## 3 Layout & **Design Considerations** of Paralleled GaN

## 4 Real Example of **Paralleling 4 x GaN FETs**

## 5 Summary

## **Purpose of Paralleling GaN Transistors**

- ▶ Paralleling of switches is necessary in high-power handling, high-output current, high-efficiency applications.
- ▶ Examples: Traction inverters, renewable energy systems, and uninterruptible power supplies.

## **Benefits of Paralleling GaN Power Devices**

- ▶ Improved thermal management
- ▶ Redundancy
- ▶ Expandability of output power
- ▶ Ease in standardization

## **Characteristics fit for Paralleling**

- ▶ GaN Systems E-HEMT device characteristics are inherently fit for paralleling
- ▶ Loss distributions (conduction & switching losses) of paralleled GaN HEMTs show superior paralleling capability.

## 1 Paralleling GaN **Benefits**

## 2 Essential GaN Characteristics – **Good for Paralleling**

Essential GaN Characteristics

Conduction Loss Distribution:  $R_{DS(on)}$  vs  $T_J$

Switching Loss Distribution:  $V_{GS(th)}$  vs  $T_J$

Switching Loss Distribution:  $g_m$  vs  $T_J$

## 3 Layout & **Design Considerations** of Paralleled GaN

## 4 Real Example of **Paralleling 4 x GaN FETs**

## 5 Summary

GaN has positive temperature coefficient of  $R_{DS(on)}$



GaN has stable gate-source threshold voltage  $V_{GS(th)}$  over temperature

GaN E-HEMT trans-conductance  $g_m$  decreases with temperature


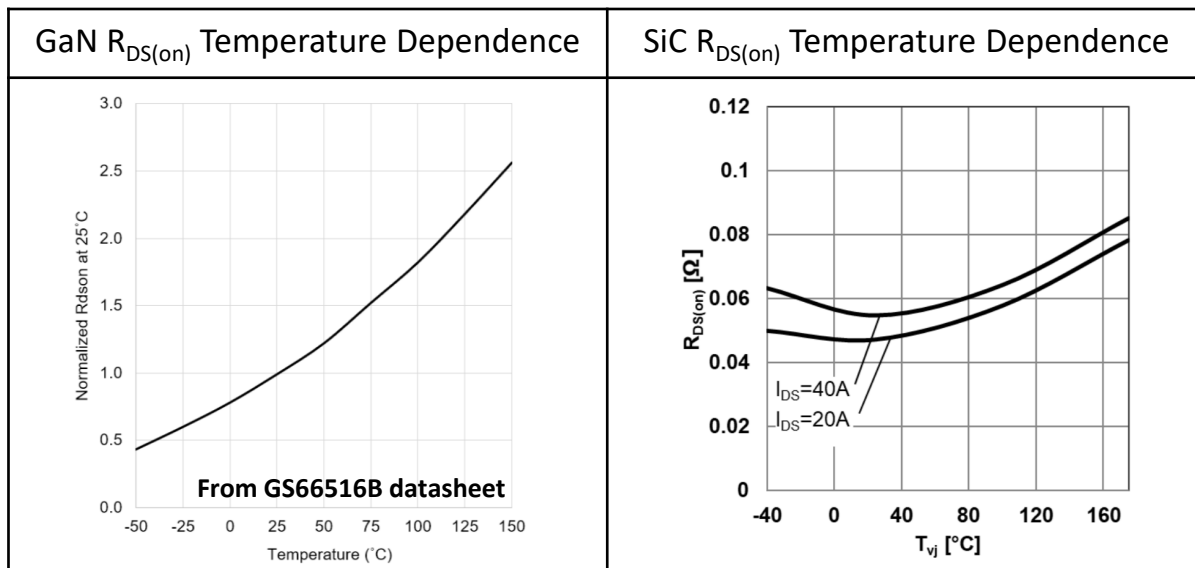 
# 2 Conduction Loss Distribution: $R_{DS(on)}$ vs $T_j$

- ❑ GaN has **positive** temperature coefficient of  $R_{DS(on)}$
- ❑ **Positive temperature coefficient** of  $R_{DS(on)}$  **helps** the thermal balance in parallel applications:




- ❑ Compared to SiC, strong  $R_{DS(on)}$  temperature dependence of GaN **helps** the current sharing in parallel applications



 
# 2 Switching Loss Distribution: $V_{GS(th)}$ vs $T_J$

- ❑ In parallel applications, current sharing heavily relies on stable gate-source threshold voltage  $V_{GS(th)}$
- ❑ GaN has stable gate-source threshold voltage  $V_{GS(th)}$  over temperature as compared to SiC
- ❑ GaN has superior paralleling capability

GaN Gate-Source Threshold  $V_{GS(th)}$  Temperature Dependence



 SiC Gate-Source Threshold  $V_{GS(th)}$  Temperature Dependence




# 2 Switching Loss Distribution: $g_m$ vs $T_j$

- ❑ GaN E-HEMT trans-conductance  $g_m$  decreases with temperature, **good for paralleling**
- ❑ **Negative** temperature coefficient of  $g_m$  helps the thermal balance in parallel applications:




GaN  $g_m$  Temperature Dependence

 


- $I_{DS}$  decreases at same  $V_{GS}$  at higher  $T_j$
- $V_{GS(th)}$  remains constant at higher  $T_j$

SiC  $g_m$  Temperature Dependence

 

- $I_{DS}$  increases at same  $V_{GS}$  at higher  $T_j$
- $V_{GS(th)}$  decreases at higher  $T_j$

Si  $g_m$  Temperature Dependence

 

- $g_m$  remains constant at higher  $T_j$
- $V_{GS(th)}$  decreases at higher  $T_j$

## 1 Paralleling GaN **Benefits**

## 2 Essential GaN Characteristics – **Good for Paralleling**

Essential GaN Characteristics

Conduction Loss Distribution:  $R_{DS(on)}$  vs  $T_J$

Switching Loss Distribution:  $V_{GS(th)}$  vs  $T_J$

Switching Loss Distribution:  $g_m$  vs  $T_J$

## 3 Layout & **Design Considerations** of Paralleled GaN

## 4 Real Example of **Paralleling 4 x GaN FETs**

## 5 Summary

# 3 Key Layout Parameters in Paralleling Applications


Here are the key layout parasitic parameters, minimize as much as possible to have the optimized system performance:

## $L_{G1-4}$ & $L_{S1-4}$ : Gate/Source inductance

- Equalize  $L_G/L_S$  using star connection and keep as low as possible
- Individual  $R_G/R_S$  is recommended to reduce gate ringing among paralleled devices

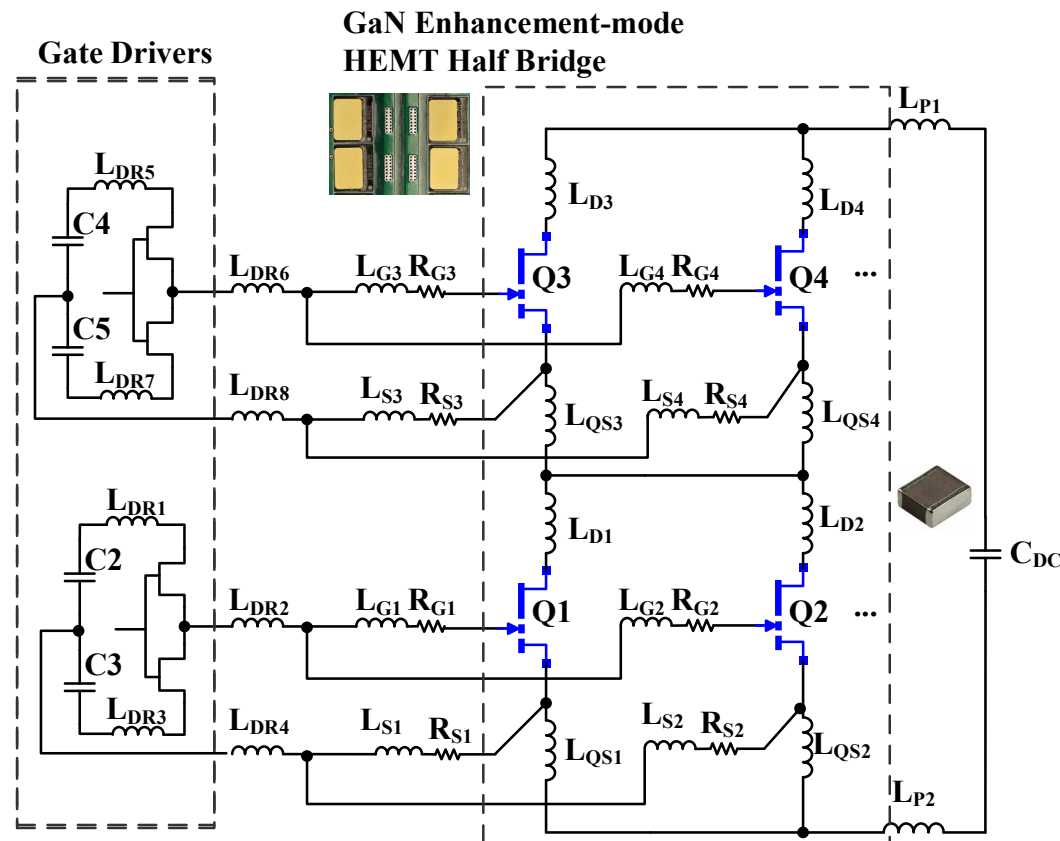
## $L_{QS1-4}$ : Common source inductance

- Defined as any inductance that couples power loop switching noise ( $L \cdot di/dt$ ) into the gate drive circuit, feedback switching  $di/dt$  to  $V_{GS}$
- Including the shared/common source inductance and mutual inductance between power and drive loops


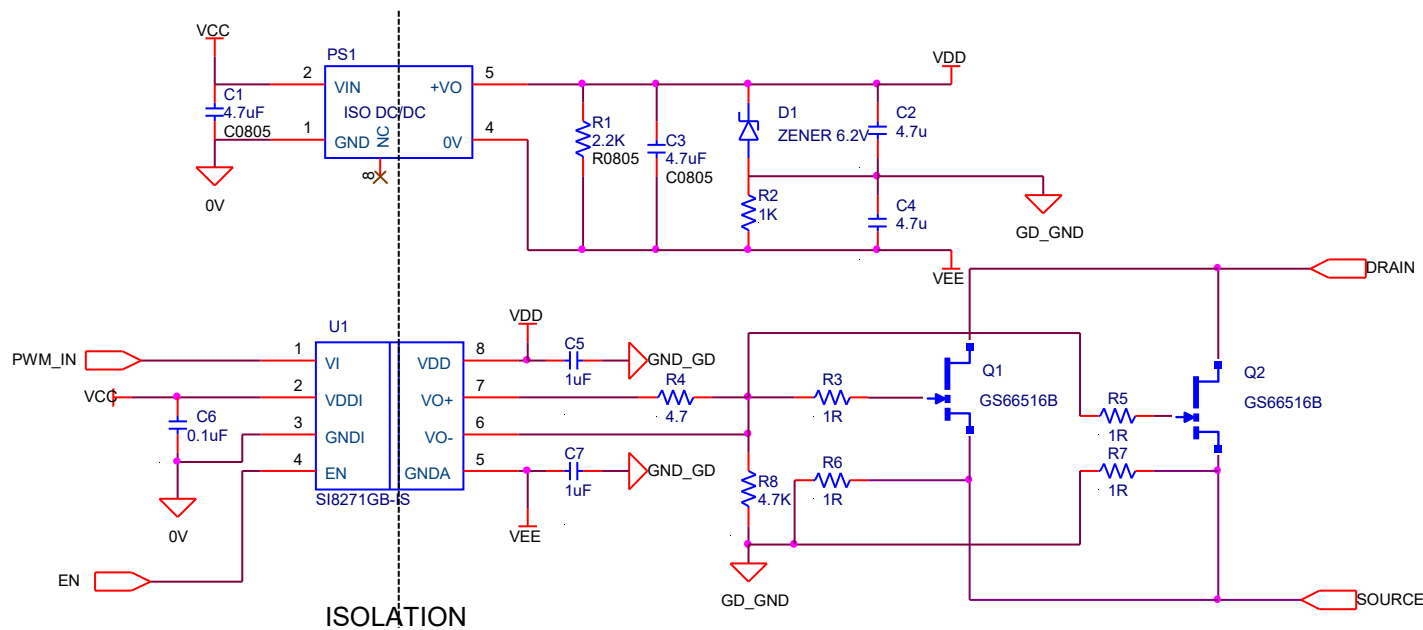
## Design considerations of gate driver circuit:


- ❑ For high current paralleling design, negative gate drive turn-off bias (-3V to -6V) is recommended for **lower turn-off loss** and **more robust** gate drive
- ❑ Create bipolar gate drive from single power supply using a 6.2V Zener (VDD = 6.2V and VEE = 6.2V - PS1 output)
- ❑ Distributed gate resistors ( $R3/R5 = 1\text{-}2\Omega$ ) and source resistors ( $R6/R7 = 1\text{-}2\Omega$ ) are added to **reduce gate ringing** among paralleled devices
- ❑ **Minimize** the gate driver loop to reduce its impact on paralleled devices current sharing




*\*Refer to  
**application note**  
**GN009**  
(PCB Layout  
Considerations  
with GaN E-HEMTs)  
for more  
information about  
optimizing the gate  
driver loop*
 
## Design considerations of power commutation loop:

- ❑ Minimize the power loop length (including the GaN FETs and decoupling capacitors)
- ❑ To reduce the power commutation loop inductance, it is important to use **magnetic flux cancellation approach**: when two adjacent conductors are located close with opposite current direction, magnetic flux generated by two current flows will cancel each other




Top View

 


Side View

 Example: Bottom-side cooled devices  
(gate driver/GaN HEMT/caps on the same side of PCB)



Top view

 


Side view
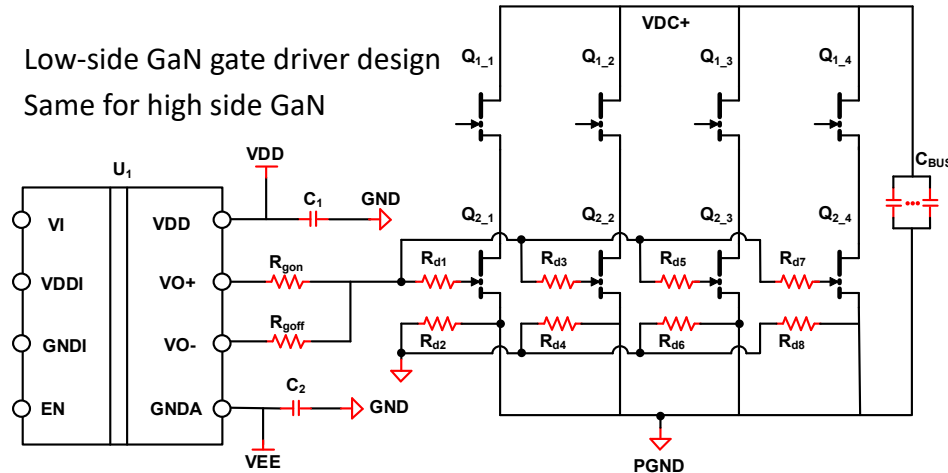
## Design example of 4x top cooled GaN FETs in parallel:



It is presented to show how the key components are placed on the PCB

- Low-side GaN gate driver design
- Same for high side GaN



Design rules of important loops

Important Loops	Components	Design Rule
Power Commutation Loop	$Q_{1\_1,2,3,4}, Q_{2\_1,2,3,4}, C_{BUS}$	1. As small as possible 2. Identical loop length for each paralleled device
Gate Driver Loop (turn-on)	$R_{gon}, R_{d1,3,5,7}, Q_{2\_1,2,3,4}, R_{d2,4,6,8}, C_1, U_1$	
Gate Driver Loop (turn-off)	$R_{goff}, R_{d1,3,5,7}, Q_{2\_1,2,3,4}, R_{d2,4,6,8}, C_2, U_1$	

  



## 1 Paralleling GaN **Benefits**

## 2 Essential GaN Characteristics – **Good for Paralleling**

Essential GaN Characteristics

Conduction Loss Distribution:  $R_{DS(on)}$  vs  $T_J$

Switching Loss Distribution:  $V_{GS(th)}$  vs  $T_J$

Switching Loss Distribution:  $g_m$  vs  $T_J$



## 3 Layout & **Design Considerations** of Paralleled GaN

## 4 Real Example of **Paralleling 4 x GaN FETs**


## 5 Summary
  
# 4 Real Example of Paralleling 4xGS66516B

- An example of **4x GS66516B in parallel** (650V 240A) IMS GaN module design is presented to illustrate how its gate driver and power stage layouts are designed




① Gate Driver Board


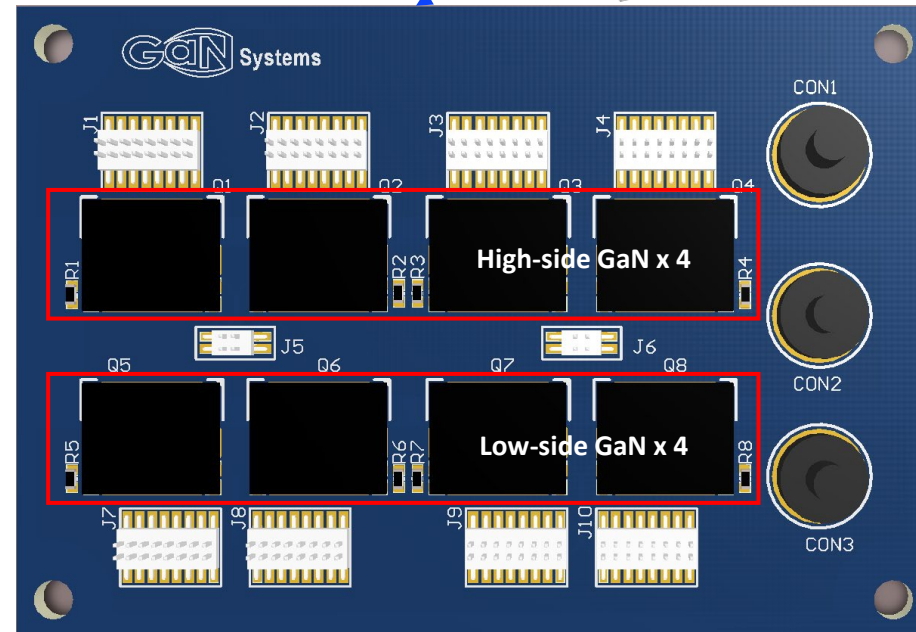


② IMS Power Board

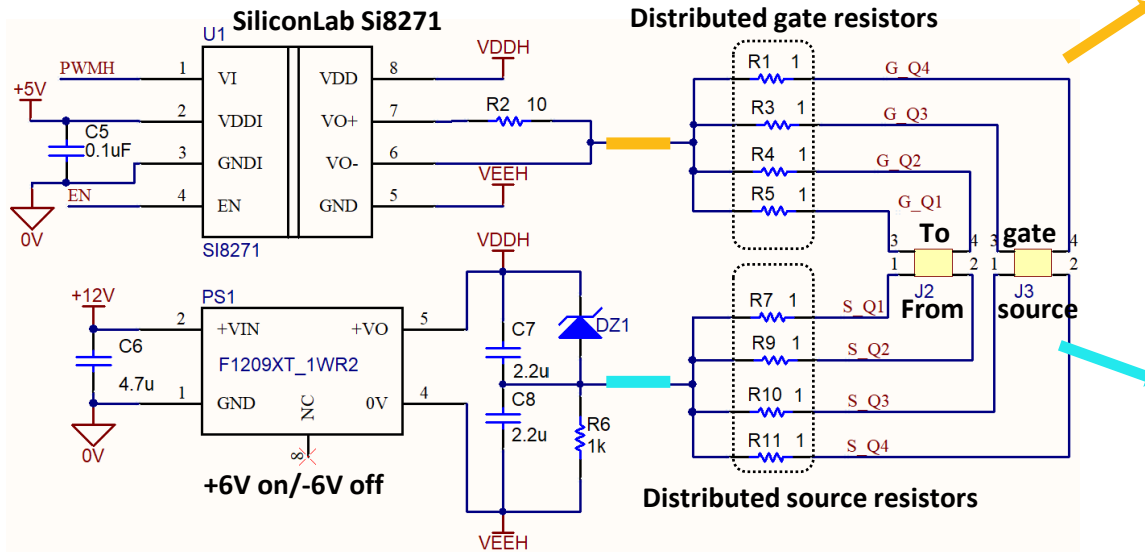- For gate driver loops, symmetric gate traces are observed







Schematic of Gate Driver Circuit

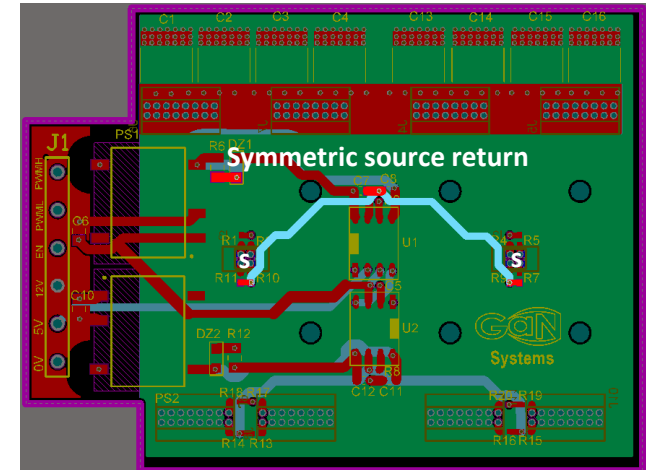 

  
 
 
# 4 Paralleling 4xGS66516B: Power Stage Layout Design

- Power commutation loop inductance is **effectively reduced** by flux cancellation


  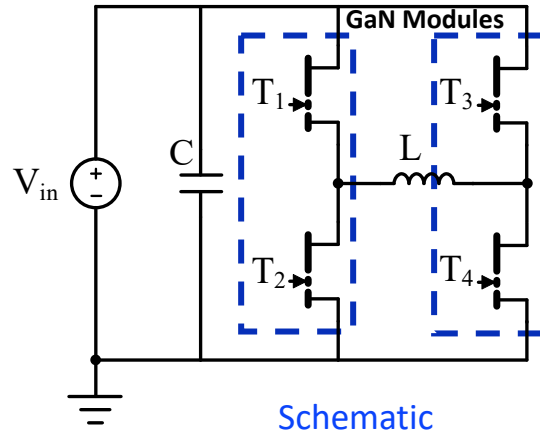
# 4 Paralleling 4xGS66516B: Full Power Emulation Test Setup GaN Systems


- ❑ A full power emulation test bench is built to test the 650V 240A GaN IMS module under high power conditions




Experiment Bench



 
- GaN HEMTs **randomly** selected for paralleling



GaN power modules under test

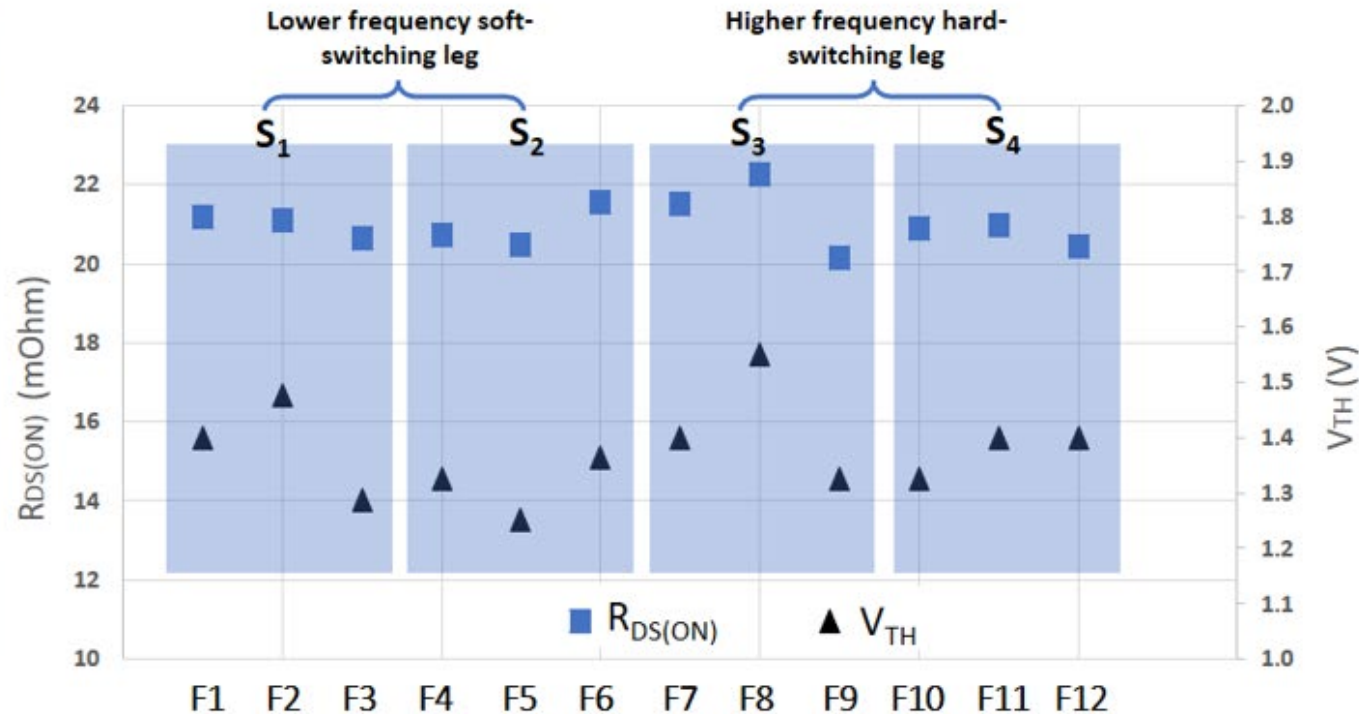

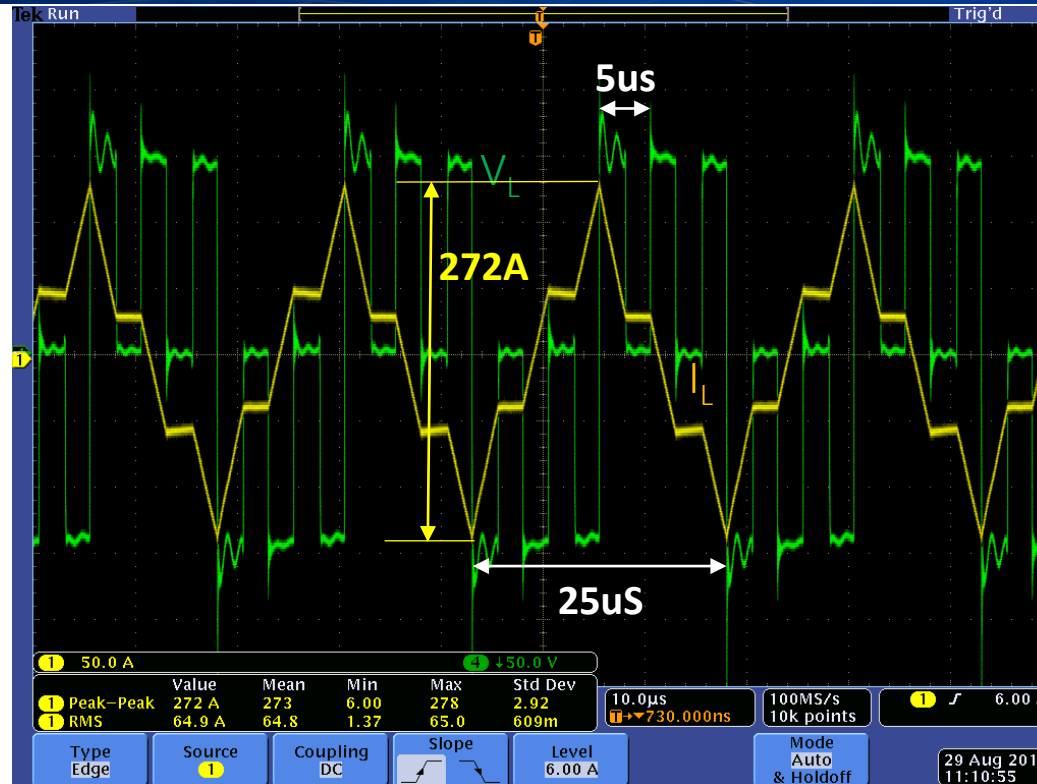
# 4 Paralleling 4xGS66516B: Experimental Waveforms



- ❑ Full power emulation test @  $I_{\max} = 136\text{A}$ ,  $I_{\text{RMS}} = 65\text{A}$ ,  $F_{\text{SW}} = 200\text{kHz}$  is performed
- ❑ Current and voltage switching waveforms are good



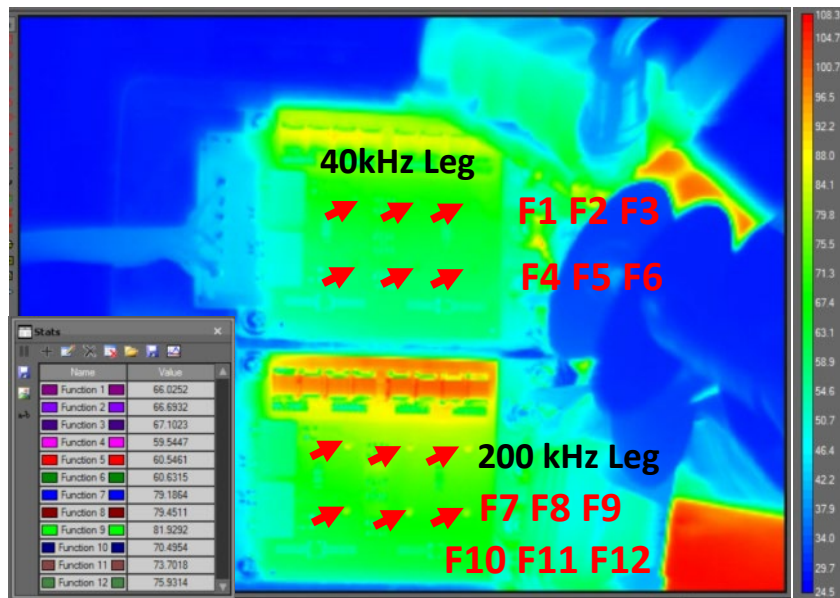
# 4 Paralleling 4xGS66516B: Temperature Distribution



Temperature Distribution@  $I_{\max}=136A$

$T_j/^\circ C$

 

Temperature Distribution in All Operation Range

- ❑ Thermal **Balance is achieved** between un-pre-selected transistors – **no thermal runaway**
- ❑ **Good** thermal balance performance: the junction temperature difference is  $< 6^\circ C$  for the worst case,  $< 3^\circ C$  for the best case

## 1 Paralleling GaN **Benefits**

## 2 Essential GaN Characteristics – **Good for Paralleling**

Essential GaN Characteristics

Conduction Loss Distribution:  $R_{DS(on)}$  vs  $T_J$

Switching Loss Distribution:  $V_{GS(th)}$  vs  $T_J$

Switching Loss Distribution:  $g_m$  vs  $T_J$

## 3 Layout & **Design Considerations** of Paralleled GaN

## 4 Real Example of **Paralleling 4 x GaN FETs**

## 5 Summary

❑ GaN Systems E-HEMT device characteristics are **inherently fit for paralleling:**

- **Positive**  $R_{DS(on)}$  temperature coefficient
- **Stable** gate threshold over the temperature range
- **Negative transconductance**  $g_m$  temperature coefficient

❑ Layout is important for paralleling high speed GaN HEMT:

- Low and balanced parasitic inductance on the power and gate drive loop
- Equal length of gate drive layout and optimum gate driver circuit

❑ A design example of 4 x paralleled GaN HEMTs is presented and the test results show that the **thermal balance of GaN HEMTs is achieved**



## Power Semiconductors

### 650 V



5.0 x 6.0 mm

**GS-065-004-1-L** 4 A, 450 mΩ

**GS-065-008-1-L** 8 A, 225 mΩ

**GS-065-011-1-L** 11 A, 150 mΩ



8.0 x 8.0 mm

**GS-065-011-2-L** 11 A, 150 mΩ

**GS-065-018-2-L** 18 A, 78 mΩ

**GS-065-030-2-L** 30 A, 50 mΩ



6.6 x 5.0 mm

**GS66502B** 7.5 A, 200 mΩ

**GS66504B** 15 A, 100 mΩ



6.6 x 5.0 mm

**GS66506T** 22.5 A, 67 mΩ

5.6 x 4.5 mm



6.6 x 5.0 mm

**GS66508T** 30 A, 50 mΩ

7.0 x 4.5 mm



6.6 x 5.0 mm

**GS66508B** 30 A, 50 mΩ

8.4 x 7.0 mm



**GS-065-060-3-T** 60 A, 25 mΩ

**GS66516T** 9.0 x 7.6 mm




**GS-065-060-3-B** 60 A, 25 mΩ

**GS66516B** 11.0 x 9.0 mm

### 650 V

AutoQual+

 

**GS-065-060-5-T-A**

60 A, 25 mΩ

9.0 x 7.6 mm



**GS-065-060-5-B-A**

60 A, 25 mΩ

11.0 x 9.0 mm



**GS-065-150-1-D2**

150 A, 10 mΩ

12.7 x 5.6 mm

### 100 V



**GS61004B**

38 A, 16 mΩ

4.6 x 4.4 mm



**GS61008P**

90 A, 7 mΩ

7.6 x 4.6 mm



**GS61008T**

90 A, 7 mΩ

7.0 x 4.0 mm



View All Products



## Power Semiconductors

### RESOURCES



Products & Datasheets



Evaluation Kits & Reference Designs



Application Notes



Featured Developments



We're Hiring



Newsroom



Video Content



Where to Buy



Product and application support at  
[gansystems.com](http://gansystems.com)